

## TUTORIAL – SINGLE PHASE IMPEDANCE AND POWER

### EXERCISE 1: FLUORESCENT TUBE

Philips Lighting  
Master TL5 HE Eco 32=35W/840 UNP/40

$P = 31,7 \text{ W} - I = 0,17 \text{ A} - V = 230 \text{ V}$

A fluorescent tube is a capacitive load



- 1) **Calculate :**
  - the apparent power required by the tube
  - the tube power factor and the phase angle between the line current  $I$  and the supply voltage
  - the reactive power required by the tube
- 2) **Draw** the power triangle.

#### Equivalent “parallel” tube model

- 3) **Draw** a diagram of the equivalent “parallel” model of the tube as a resistor and a reactance connected in parallel. **Indicate** the supply voltage  $V$ , the line current  $I$ , the active current  $I_P$  and the reactive current  $I_Q$  on the diagram
- 4) **Plot** the Fresnel diagram by taking the supply voltage  $V$  as a reference
- 5) **Calculate:**
  - the active current flowing through the tube
  - the reactive current flowing through the tube
  - the equivalent tube impedance
  - the equivalent tube resistance
  - the equivalent tube reactance
  - the capacitance of the tube equivalent capacitor.

#### Equivalent “series” tube model

- 6) **Draw** a diagram of the equivalent “series” model of the tube as a resistor and a reactance connected in series. On the diagram, indicate the supply voltage  $V$ , the line current  $I$ , the voltage across the resistor  $V_R$  and the voltage across the reactor  $V_C$
- 7) **Plot** the Fresnel diagram by using the line current  $I$  as a reference
- 8) **Calculate:**
  - the voltage across the resistor
  - the voltage across the reactance
  - the equivalent tube impedance
  - the equivalent tube resistance
  - the equivalent tube reactance
  - the capacitance of the tube equivalent capacitor

*Additional documentation: GIE 2017 p N38*


## EXERCISE 2: SINGLE-PHASE MOTOR

**Motor SEW - DRK 71 M4 - 0,25 kW**

**$P_U = 0,250 \text{ kW} - I = 2,05 \text{ A} - V = 230 \text{ V}$**

**$\eta = 66.3\%$**

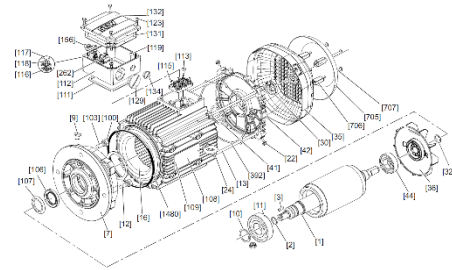**A single-phase motor is an inductive load**



9) **Calculate:**

- the apparent power required by the motor
- the motor power factor and the phase angle between the line current  $I$  and the supply voltage  $V$
- the reactive power required by the motor

10) **Draw** the power triangle.

**Equivalent “parallel” motor model**

11) **Draw** a diagram of the equivalent “parallel” model of the motor as a resistor and a reactance connected in parallel. **Indicate** the supply voltage  $V$ , the line current  $I$ , the active current  $I_P$  and the reactive current  $I_Q$  on the diagram.

12) **Plot** the Fresnel diagram by taking the supply voltage  $V$  as a reference.

13) **Calculate:**

- the active current flowing through the motor,
- the reactive current flowing through the motor,
- the equivalent motor impedance,
- the equivalent motor resistance,
- the equivalent motor reactance,
- the equivalent motor inductance.