


## II – Power in sinusoidal regime

### Sine-wave: definitions


- A sinusoidal quantity  $s(t)$  (voltage, current, flux or magnetic field) is written:

$$s(t) = \hat{S} \cdot \cos(\omega t + / - \varphi)$$
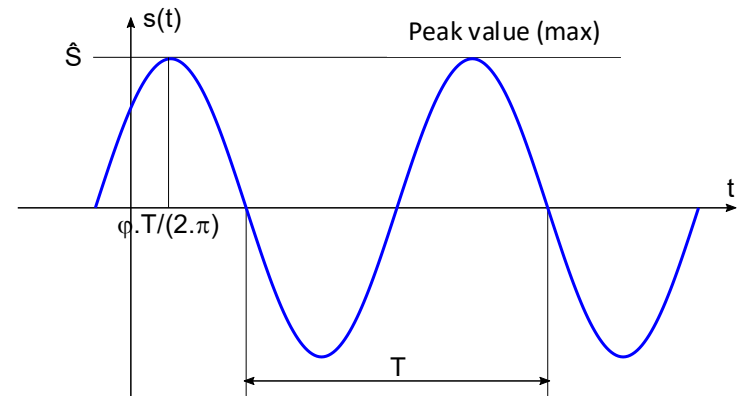
$$s(t) = S\sqrt{2} \cdot \cos(\omega t + / - \varphi)$$




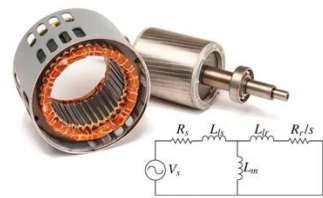
- $s(t)$ : quantity which evolves with time in sinusoidal form
- $S$ : RMS value of the quantity,
- $\hat{S}$ : maximum value reached by the quantity  $s(t) \Rightarrow \hat{S} = S\sqrt{2}$ ,
- $\omega$ : electrical pulsation in rad/s of the magnitude,  $\omega = 2\pi \cdot f = 2\pi/T$ ,
- $f$ : signal frequency and  $T$ : signal period,
- $\varphi$ : phase at origin (at  $t = 0$ ).



## II – Power in sinusoidal regime

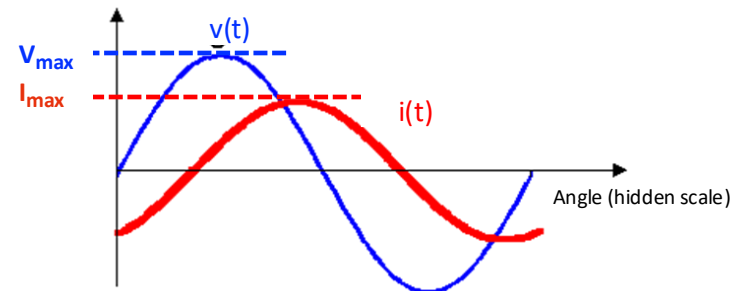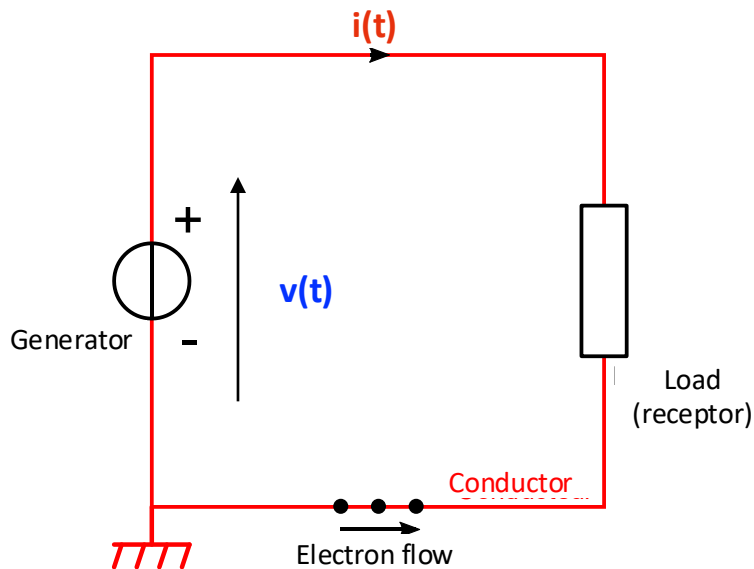
### Single-phase

- Most of the world's electrical energy is generated, transmitted and distributed in the form of sinusoidal voltages.
- Any periodic signal can be studied by decomposing it down into sinusoidal signals using a Fourier transform.



$$v(t) = \hat{V} \cdot \sin(\omega t)$$
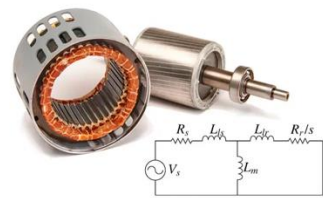
$$i(t) = \hat{I} \cdot \sin(\omega t - \varphi)$$




## II – Power in sinusoidal regime
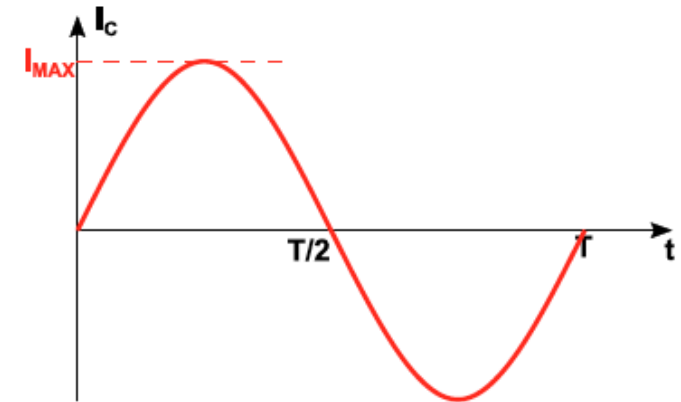
### Single-phase – Average and RMS values


- The **AVERAGE VALUE** of any current (same for the voltage) is the value that a direct current carrying the same amount of electricity would have.


$$I_{MOY} = \frac{1}{T} \int i(t) dt \quad I_{MOY} = 0$$



- The **RMS** (Root Mean square) **VALUE** of any current is the value that a direct current carrying the same amount of energy would have.
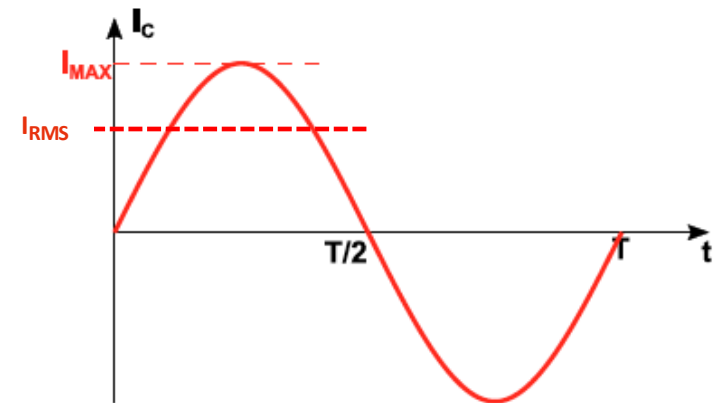
$$I_{RMS} = \sqrt{\frac{1}{T} \int i^2(t) dt} \quad I_{RMS} = \frac{I_{MAX}}{\sqrt{2}}$$



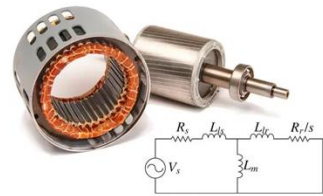

## II – Power in sinusoidal regime

### Single-phase – Average and RMS values

- **Exercise:** demonstrate the expression of  $I_{\text{moy}}$  and  $I_{\text{RMS}}$


#### Average value

- $I_{\text{MOY}} = \frac{1}{T} \int_0^T i(t) dt$
- $I_{\text{MOY}} = \frac{1}{T} \int_0^T I_{\text{MAX}} \cdot \sin(\omega t) dt$
- $I_{\text{MOY}} = \frac{1}{T} \left[ I_{\text{MAX}} \cdot \frac{-\cos(\omega t)}{\omega} \right]_0^T$
- $I_{\text{MOY}} = \frac{I_{\text{MAX}}}{\omega T} \cdot [-\cos(\omega T) + \cos(0)]$
- $I_{\text{MOY}} = \frac{I_{\text{MAX}}}{\omega T} \cdot (-1 + 1)$
- $I_{\text{MOY}} = 0$

$$\cos 2a = 1 - 2\sin^2 a \text{ et } \sin^2 a = \frac{1 - \cos 2a}{2}$$
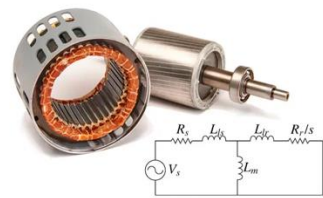
#### RMS value


- $I_{\text{EFF}} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$
- $I_{\text{EFF}}^2 = \frac{1}{T} \int_0^T i^2(t) dt$
- $I_{\text{EFF}}^2 = \frac{1}{T} \int_0^T (I_{\text{MAX}} \cdot \sin(\omega t))^2 dt$
- $I_{\text{EFF}}^2 = \frac{1}{T} \int_0^T (I_{\text{MAX}})^2 \cdot (\sin(\omega t))^2 dt$
- $I_{\text{EFF}}^2 = \frac{1}{T} \int_0^T (I_{\text{MAX}})^2 \frac{(1 - \cos 2\omega t)}{2} dt$
- $I_{\text{EFF}}^2 = \frac{I_{\text{MAX}}^2}{2 \cdot T} \int_0^T (1 - \cos 2\omega t) dt$
- $I_{\text{EFF}}^2 = \frac{I_{\text{MAX}}^2}{2 \cdot T} \left[ t - \frac{\sin(2\omega t)}{2\omega} \right]_0^T$
- $I_{\text{EFF}}^2 = \frac{I_{\text{MAX}}^2}{2} \left[ \frac{T-0}{T} - \frac{\sin(2\omega T) - \sin(0)}{2\omega T} \right]$
- $I_{\text{EFF}}^2 = \frac{I_{\text{MAX}}^2}{2} \left[ 1 - \frac{0-0}{4\pi} \right]$
- $I_{\text{EFF}}^2 = \frac{I_{\text{MAX}}^2}{2}$
- $I_{\text{EFF}} = \frac{I_{\text{MAX}}}{\sqrt{2}}$




## II – Power in sinusoidal regime
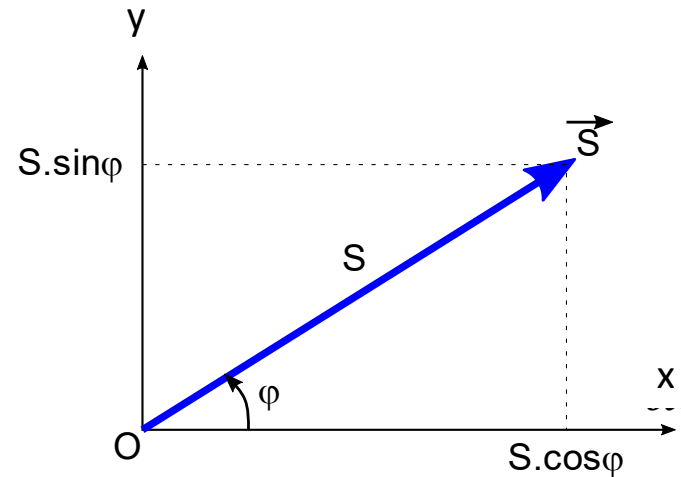
### Single-phase – Fresnel vector representation

- Associated with  $s(t)$  is a **vector**  $\vec{S}$  known as the **Fresnel vector**, of norm  $S$  (RMS value) rotating around the origin point  $O$  at an angular frequency  $\omega$ .



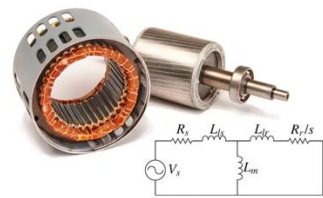- Since all signals have the same angular frequency  $\omega$ , vectors in the same Fresnel diagram rotate at the same speed. Therefore, they are represented at  $t = 0$ .



## II – Power in sinusoidal regime


### Single-phase – Complex representation

- Complex representation:

- Reminder: Euler's formula

$$e^{ix} = \cos x + i \cdot \sin x$$
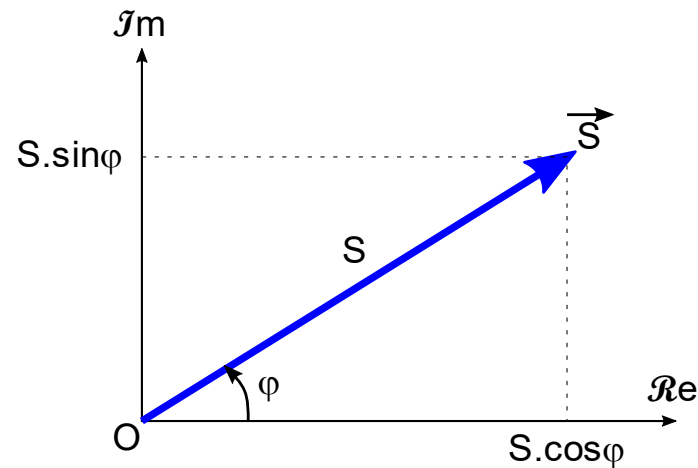
$$S \cdot \cos \varphi + j \cdot S \cdot \sin \varphi = S \cdot e^{j\varphi} = \underline{S}$$




- Complex quantity

- Complex amplitude

$$\begin{cases} \underline{s}(t) = S\sqrt{2} \cdot e^{j(\omega t + \varphi)} \\ s(t) = \Re(\underline{s}(t)) \end{cases}$$

$$\underline{s} = \underline{S}\sqrt{2} \cdot e^{j\omega t}$$

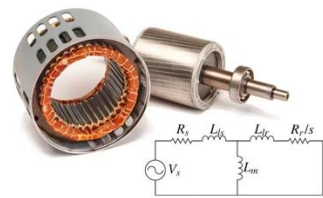
where  $\underline{S} = S \cdot e^{j\varphi} = [S; \varphi]$



## II – Power in sinusoidal regime


### Single-phase – Complex representation

- Sum:

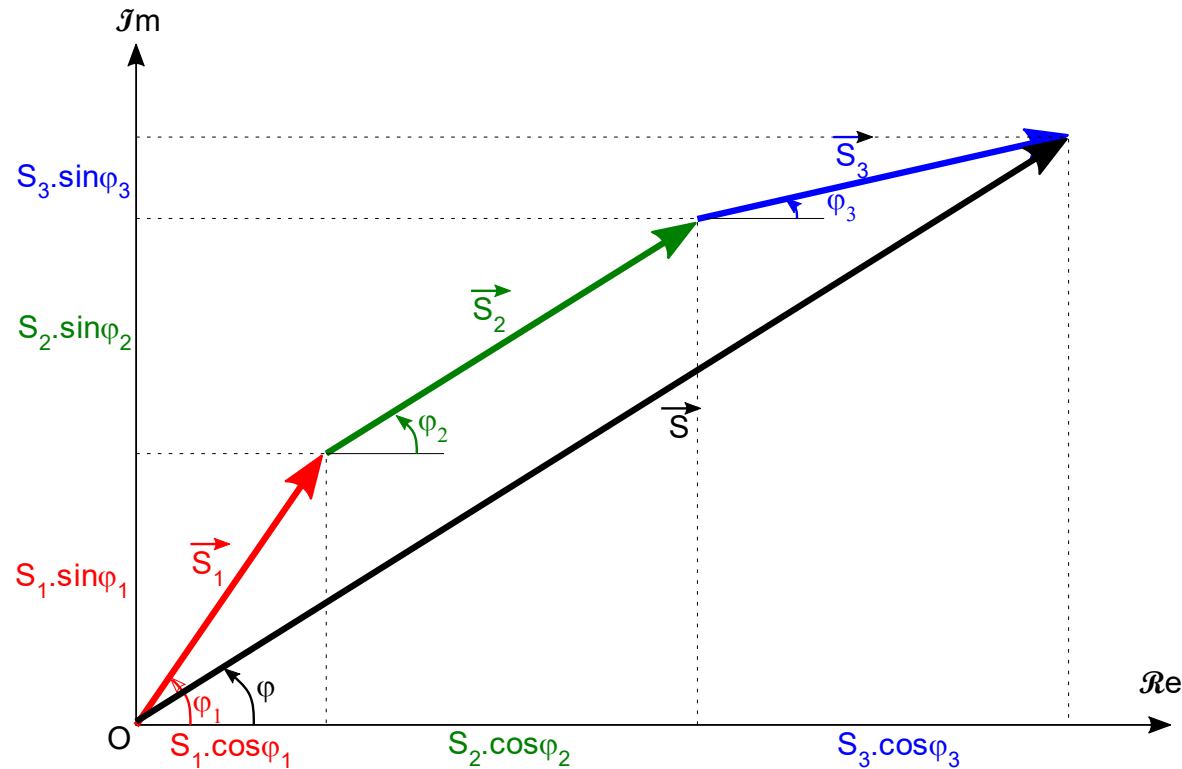

$$S = \sqrt{(\sum S_i \cdot \cos \varphi_i)^2 + (\sum S_i \cdot \sin \varphi_i)^2}$$
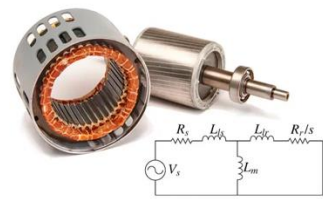
$$\tan \varphi = \frac{\sum S_i \cdot \sin \varphi_i}{\sum S_i \cdot \cos \varphi_i}$$




## II – Power in sinusoidal regime
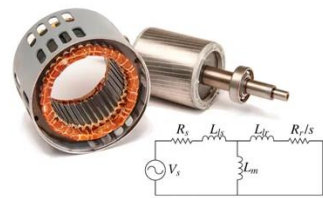
### Single-phase – Complex representation

- Derivate:  $\underline{s}(t) = \hat{S} \cdot e^{j(\omega t + \varphi)} = \hat{S} \cdot \cos(\omega t + \varphi) + j \cdot \hat{S} \cdot \sin(\omega t + \varphi)$

$$\frac{d\underline{s}(t)}{dt} = \frac{d(\hat{S} \cdot \cos(\omega t + \varphi) + j \cdot \hat{S} \cdot \sin(\omega t + \varphi))}{dt}$$



## II – Power in sinusoidal regime


### Single-phase – Complex representation

- Derivate:  $\underline{s}(t) = \hat{S} \cdot e^{j(\omega t + \varphi)} = \hat{S} \cdot \cos(\omega t + \varphi) + j \cdot \hat{S} \cdot \sin(\omega t + \varphi)$

$$\begin{aligned} \frac{d\underline{s}(t)}{dt} &= \frac{d(\hat{S} \cdot \cos(\omega t + \varphi) + j \cdot \hat{S} \cdot \sin(\omega t + \varphi))}{dt} \\ \frac{d\underline{s}(t)}{dt} &= \hat{S} \cdot [-\omega \cdot \sin(\omega t + \varphi) + j \cdot \omega \cdot \cos(\omega t + \varphi)] \\ \frac{d\underline{s}(t)}{dt} &= j \cdot \omega \cdot \hat{S} \cdot \left[ -\frac{\sin(\omega t + \varphi)}{j} + \cos(\omega t + \varphi) \right] \\ \frac{d\underline{s}(t)}{dt} &= j \cdot \omega \cdot \hat{S} \cdot [\cos(\omega t + \varphi) + j \sin(\omega t + \varphi)] \\ \frac{d\underline{s}(t)}{dt} &= j \cdot \omega \cdot \underline{s}(t) \end{aligned}$$

Derivative with respect to time: **rotation of  $+\pi/2$  rad** in the complex plane
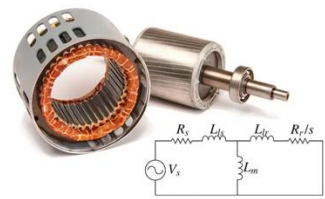
$$\frac{d\underline{s}(t)}{dt} = j \cdot \omega \cdot \underline{s}(t) = \left[ \underline{S} \cdot \omega; \varphi + \frac{\pi}{2} \right]$$




## ***II – Power in sinusoidal regime***

### **Single-phase – Complex representation**

- Integrate:

$$\underline{s}(t) = \hat{S} \cdot e^{j(\omega t + \varphi)} = \hat{S} \cdot \cos(\omega t + \varphi) + j \cdot \hat{S} \cdot \sin(\omega t + \varphi)$$
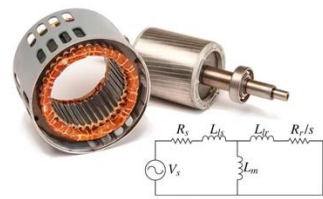
$$\int \underline{s}(t) \cdot dt = \int (\hat{S} \cdot \cos(\omega t + \varphi) + j \cdot \hat{S} \cdot \sin(\omega t + \varphi)) \cdot dt$$



## II – Power in sinusoidal regime

### Single-phase – Complex representation

- Integrate:

$$\int \underline{s}(t).dt = \int (\hat{S} \cdot \cos(\omega t + \varphi) + j \cdot \hat{S} \cdot \sin(\omega t + \varphi)).dt$$

$$\int \underline{s}(t).dt = \hat{S} \cdot \left[ \int (\cos(\omega t + \varphi)).dt + j \cdot \int (\sin(\omega t + \varphi)).dt \right] = \hat{S} \cdot \left[ \frac{\sin(\omega t + \varphi)}{\omega} + j \cdot \frac{-\cos(\omega t + \varphi)}{\omega} \right]$$

$$\int \underline{s}(t).dt = \frac{\hat{S}}{j\omega} \cdot [j \cdot \sin(\omega t + \varphi) + j \cdot j \cdot (-\cos(\omega t + \varphi))]$$


$$\int \underline{s}(t).dt = \frac{\hat{S}}{j\omega} \cdot [j \cdot \sin(\omega t + \varphi) + \cos(\omega t + \varphi)]$$

$$\int \underline{s}(t).dt = \frac{1}{j\omega} \cdot \hat{S} \cdot [\cos(\omega t + \varphi) + j \cdot \sin(\omega t + \varphi)]$$

$$\int \underline{s}(t).dt = \frac{\underline{s}(t)}{j \cdot \omega}$$

Time integration: **rotation of  $-\pi/2$  rad** in the complex plane

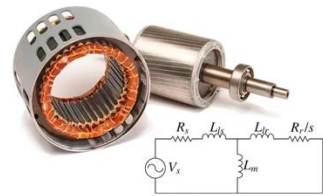
$$\int \underline{s}(t).dt = \frac{\underline{s}(t)}{j \cdot \omega} = \left[ \frac{\underline{S}}{\omega}; \varphi - \frac{\pi}{2} \right]$$



## II – Power in sinusoidal regime
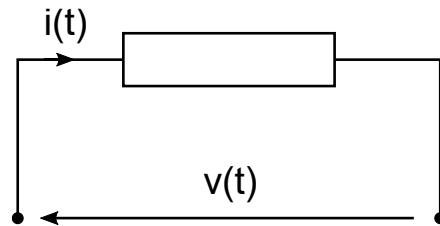
### Single-phase – Complex impedances


- Let us consider a passive linear dipole, in receptor convention, subjected to a sinusoidal voltage  $v(t)$  and flowed by a sinusoidal current  $i(t)$ :




- We write:

$$\begin{cases} v(t) = V\sqrt{2} \cdot \cos(\omega t + \varphi_V) \\ i(t) = I\sqrt{2} \cdot \cos(\omega t + \varphi_I) \end{cases}$$
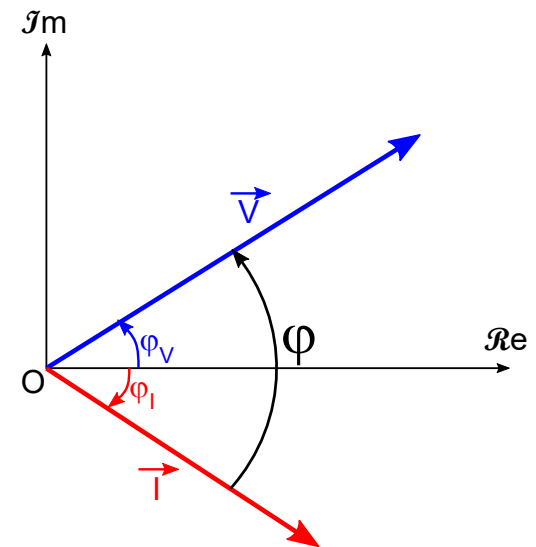
$$\begin{cases} \underline{V} = V \cdot e^{j\varphi_V} = [V; \varphi_V] \\ \underline{I} = I \cdot e^{j\varphi_I} = [I; \varphi_I] \end{cases}$$



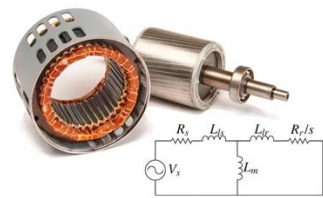

## II – Power in sinusoidal regime

### Single-phase – Complex impedances

- The complex impedance is defined as:

$$\underline{Z} = \frac{\underline{V}}{\underline{I}} = R + jX = \underline{Z} = Z \cdot e^{j\varphi}$$

- where:

-  $Z$  : dipole impedance  $Z = \|\underline{Z}\| = \frac{V}{I}$

-  $\varphi$  : phase shift angle of voltage with respect to current:



$$\varphi = \text{Arg} \underline{Z} = \varphi_V - \varphi_I$$


-  $R$ : resistance in Ohms of the dipole, real part of the complex impedance:

$$R = \Re(\underline{Z}) = Z \cdot \cos\varphi$$

-  $X$  : reactance in Ohms of the dipole, imaginary part of the complex impedance
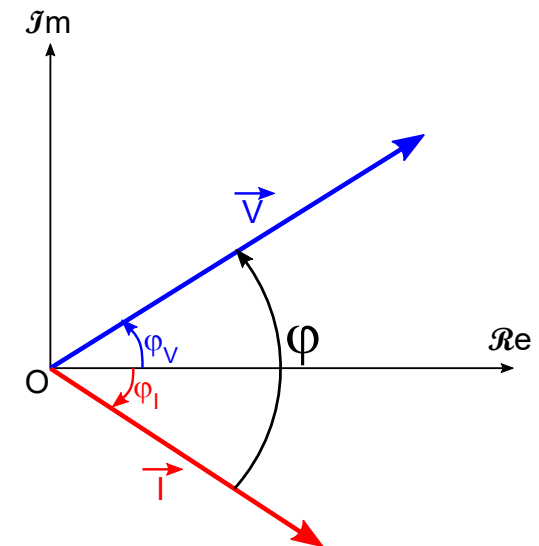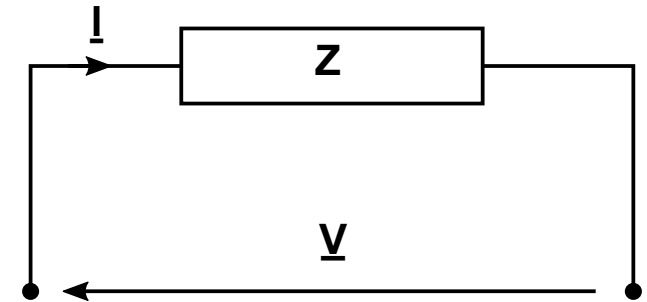
$$X = \Im(\underline{Z}) = Z \cdot \sin\varphi$$



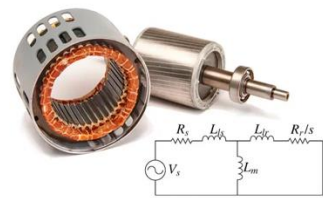

## II – Power in sinusoidal regime

### Single-phase – Complex impedances


$$\underline{Z} = \frac{\underline{V}}{\underline{I}} = R + jX = \underline{Z} = Z \cdot e^{j\varphi}$$

- where:

- Z : dipole impedance  $Z = \|\underline{Z}\| = \frac{V}{I}$

-  $\varphi$  : phase shift angle of voltage with respect to current:
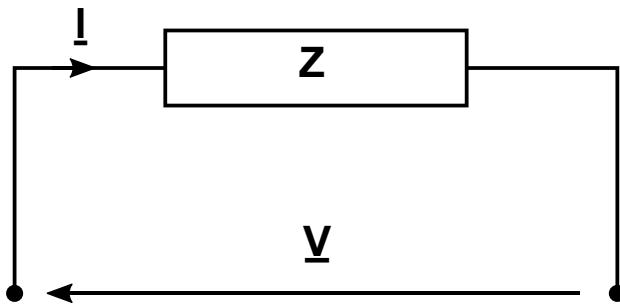
$$\varphi = \text{Arg} \underline{Z} = \varphi_V - \varphi_I$$



- If  $\varphi > 0$ , the voltage leads the current, impedance or load is said to be **inductive**.


(Motors, Transformers, Electromagnets)

- If  $\varphi = 0$ , the voltage is in phase with the current, impedance or load is said to be **resistive**.

(Resistors, Furnaces, Regulated baths)

- If  $\varphi < 0$ , the voltage lags the current, impedance or load is said to be **capacitive**.


(Capacitors)

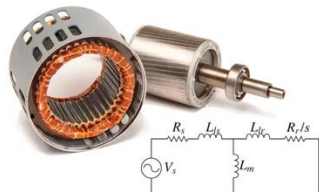

## II – Power in sinusoidal regime

### Single-phase – linear dipoles

	Resistor	Ideal coil	Ideal capacitor
Definition	An electrical resistor is an electrical dipole that opposes the flow of current	A “coil” is an electrical dipole that opposes the variation of electric current and can store energy in electromagnetic form.	A “capacitor” is an electrical dipole that resists variation in the voltage to which it is subjected, and can store energy in electrostatic form.
Characteristics	$R$ : resistance in $\Omega$ (Ohm)	$L$ : Coil inductance in H (Henry)	$C$ : Capacitance in F (Farad)
AC regime	$V_R(t) = R \cdot i(t)$	$V_L(t) = L \cdot \frac{di(t)}{dt}$	$V_C(t) = \frac{1}{C} \cdot \int i(t) \cdot dt$
Symbolic representation in receptor convention			
Sinusoidal regime	$\underline{V_R} = R \cdot \underline{I}$	$\underline{V_L} = jL\omega \cdot \underline{I}$	$\underline{V_C} = \frac{1}{jC\omega} \cdot \underline{I}$
Impedance	$\underline{Z} = R = [R; 0]$	$\underline{Z} = jL\omega = [L\omega; \frac{\pi}{2}]$	$\underline{Z} = \frac{1}{jC\omega} = [\frac{1}{jC\omega}; -\frac{\pi}{2}]$

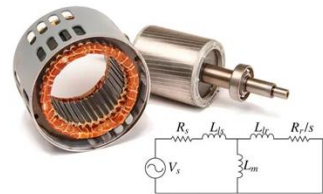

## II – Power in sinusoidal regime

### Single-phase – Fresnel (vector) representation

$$\underline{V_R} = [R \cdot I; 0]$$


$V_R$  and  $I$  are in phase


$$\underline{V_L} = [L\omega \cdot I; \frac{\pi}{2}]$$

$V_L$  leads  $I$  in quadrature

$$\underline{V_C} = [\frac{I}{C\omega}; -\frac{\pi}{2}]$$

$V_C$  lags  $I$  in quadrature

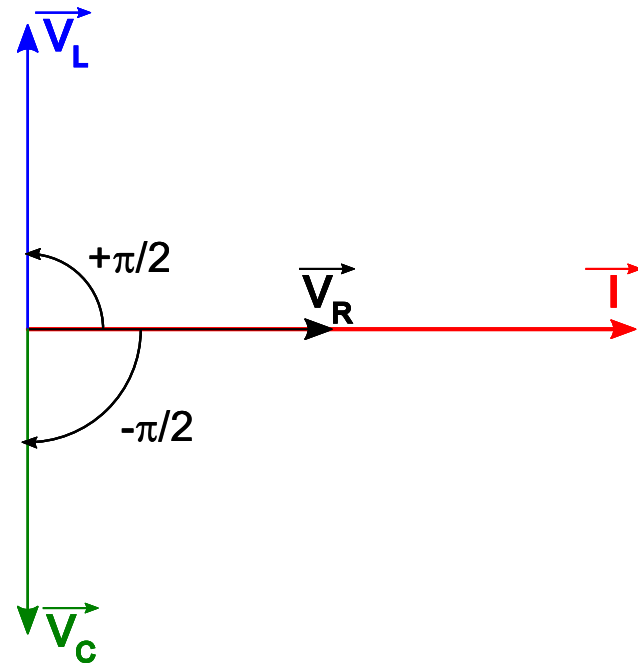

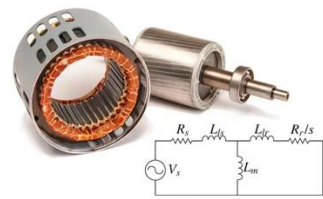

## II – Power in sinusoidal regime

### Single-phase – Expressions of powers

- Instantaneous power (in W):  $p(t) = v(t) \times i(t)$

=> exchange of energy, heat or work, between the network and the dipole at each instant


- Active power or average power (in W) – General expression:

$$P = \langle p(t) \rangle = \frac{1}{T} \int_0^T p(t) \cdot dt = \frac{1}{T} \int_0^T v(t) \cdot i(t) \cdot dt$$

=> Balance of energy exchanged between the network and the dipole over a period T

=> If  $P > 0$ , the dipole consumes energy, it operates a receptor

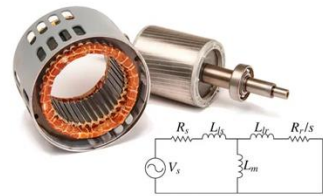=> If  $P < 0$ , the dipole supplies energy, it operates a generator



## II – Power in sinusoidal regime

### Single-phase – Expressions of powers

- Linear receptor in sinusoidal regime

- Through which a current  $i(t)$  flows

$$i(t) = I\sqrt{2} \times \sin(\omega t)$$

- Subjected to a voltage  $v(t)$



$$v(t) = V\sqrt{2} \times \sin(\omega t + \varphi)$$


$\varphi$  positive, voltage ahead of current, inductive receiver

$\varphi$  zero, voltage in phase with current, resistive receiver

$\varphi$  negative, voltage lagging current, capacitive receiver

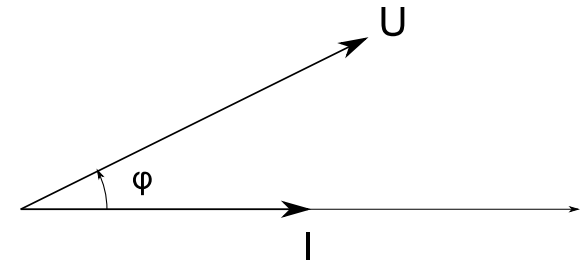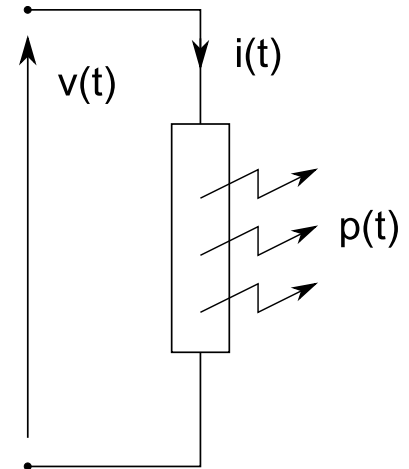- Instantaneous power  $p(t) = v(t) \times i(t)$




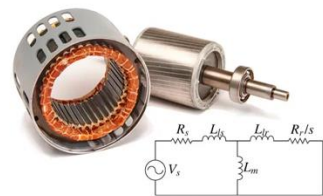


## II – Power in sinusoidal regime
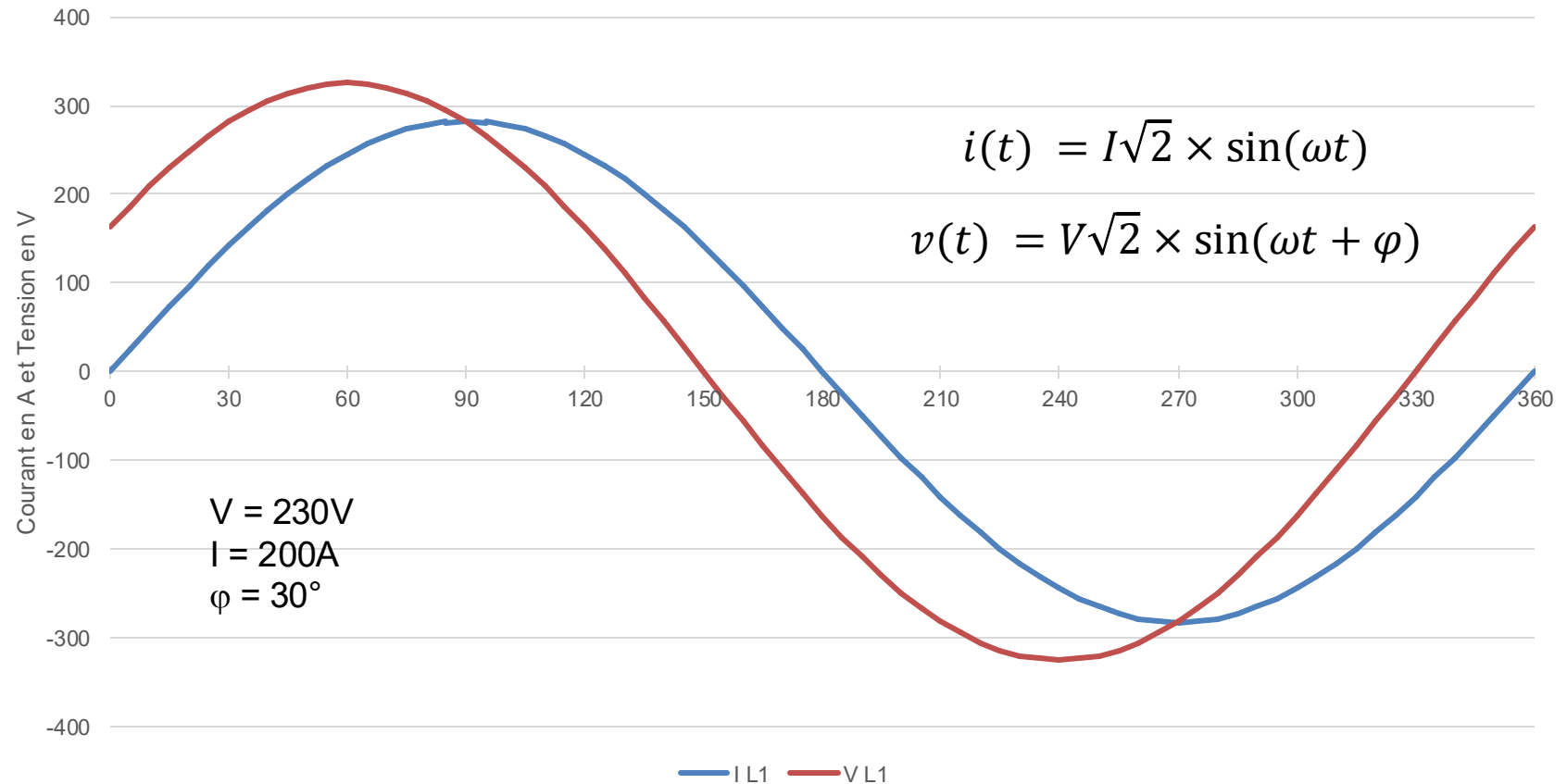
### Single-phase – Expressions of powers

- Linear receptor in sinusoidal regime: current and voltages



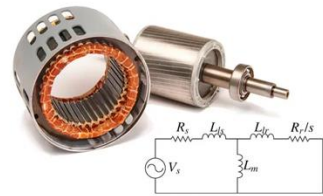

## II – Power in sinusoidal regime

### Single-phase – Expressions of powers

- Linear receptor in sinusoidal regime
- Instantaneous power:

$$p(t) = v(t) \times i(t)$$


$$p(t) = V\sqrt{2} \times \sin(\omega t + \varphi) \times I\sqrt{2} \times \sin(\omega t)$$

$$p(t) = 2 \times V \times I \times \sin(\omega t + \varphi) \times \sin(\omega t)$$

$$\sin a \times \sin b = \frac{1}{2} (\cos(a - b) + \cos(a + b))$$

$$p(t) = 2 \times V \times I \times \frac{1}{2} (\cos(\omega t + \varphi - \omega t) + \cos(\omega t + \varphi + \omega t))$$

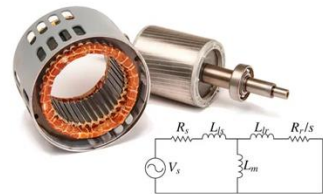
$$p(t) = V I \cos(\varphi) + V I \cos(2 \omega t + \varphi)$$




## II – Power in sinusoidal regime
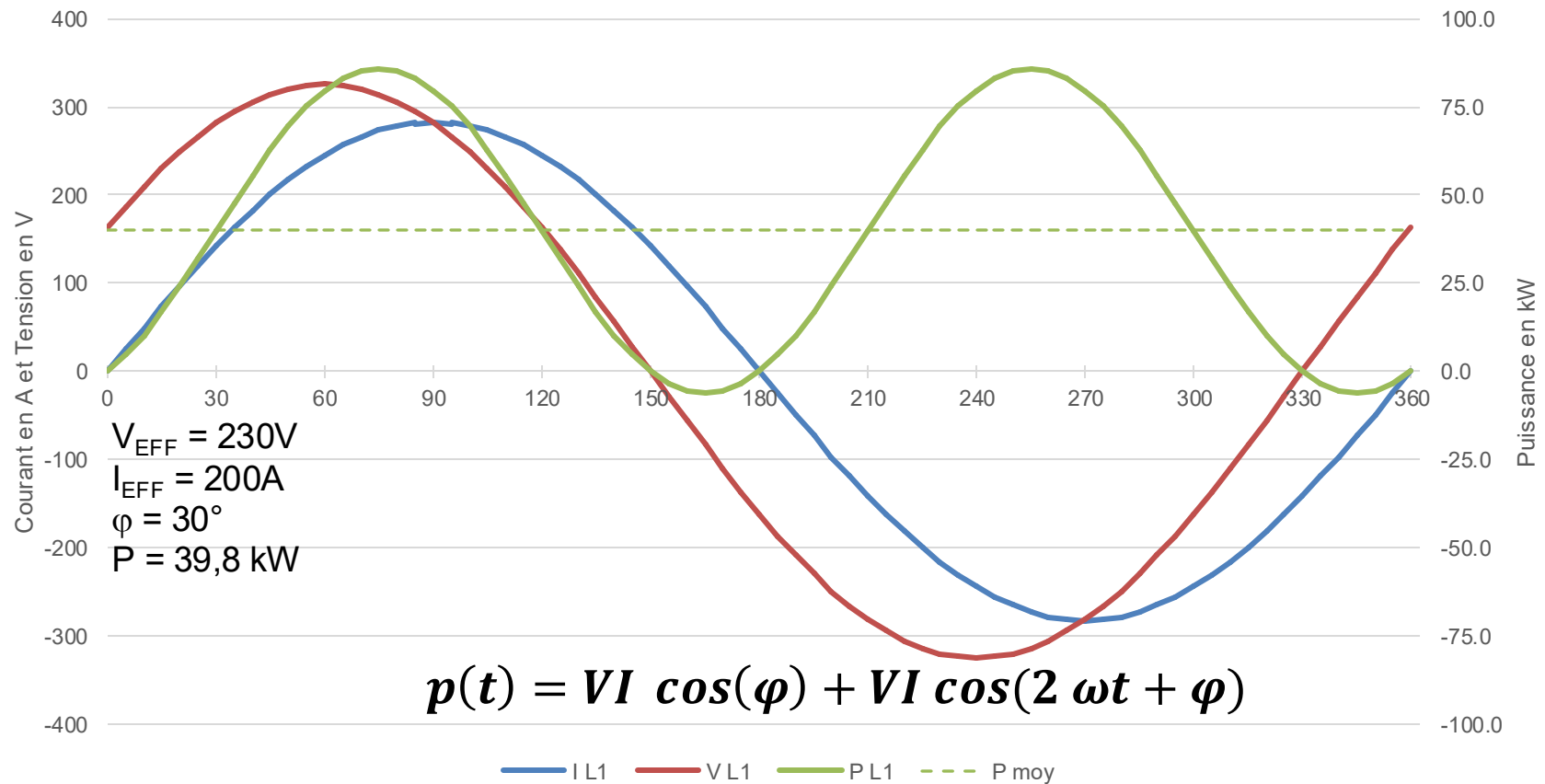
### Single-phase – Expressions of powers

- Linear receptor in sinusoidal regime: current, voltage and power



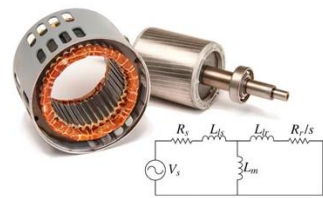

## II – Power in sinusoidal regime

### Single-phase – Expressions of powers

- Instantaneous power (in W):  $p(t) = v(t) \times i(t)$

=> exchange of energy, heat or work, between the network and the dipole at each instant

- Active power or average power (in W):  $P = \langle p(t) \rangle = V I \cos(\varphi)$


=> Balance of energy exchanged between the network and the dipole over a period T

- Apparent power (in VA):  $S = V \cdot I$

=> Design value (voltage for insulation, current for conductor cross-section)

- Power factor (general expression):
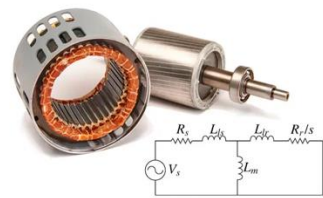
$$FP = \frac{P}{S} \quad FP = \cos(\varphi) \quad \Rightarrow \text{Sinusoidal regime only}$$



## II – Power in sinusoidal regime

### Single-phase – Expressions of powers

- **Reactive power:**

- Projection of  $I$  on the axes:  $\vec{I} = \vec{I}_A + \vec{I}_R$

=> Active current:  $I_A = I \cdot \cos(\varphi)$



=> Reactive current:  $I_R = I \cdot \sin(\varphi)$


- Reminder of the active power (W):

$$P = V \cdot I \cdot \cos(\varphi) = V \cdot I_A$$

- By analogy, the reactive power (given in VAR) can be written:
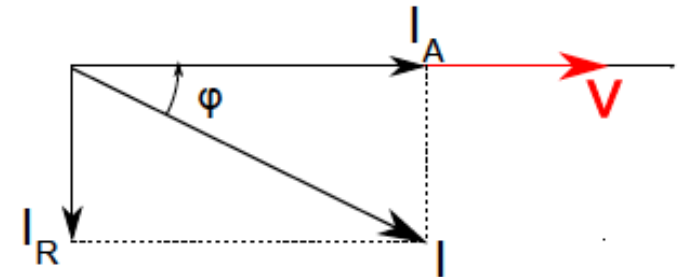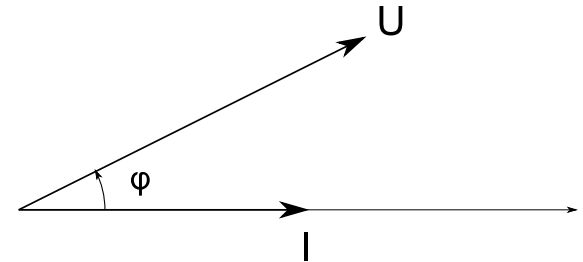
$$Q = V \cdot I \cdot \sin(\varphi) = V \cdot I_R$$



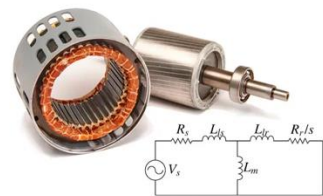

## II – Power in sinusoidal regime

### Single-phase – Expressions of powers

- Relation between powers  $S$ ,  $P$  and  $Q$ :



$$P = V \cdot I \cdot \cos(\varphi)$$


$$Q = V \cdot I \cdot \sin(\varphi) = P \cdot \tan(\varphi)$$

$$S^2 = P^2 + Q^2$$

- Note that:  $S \neq P + Q$

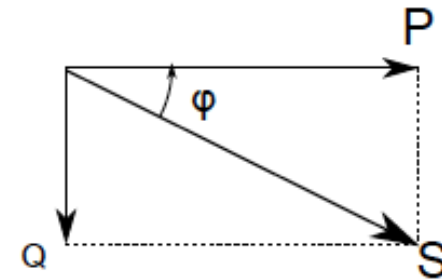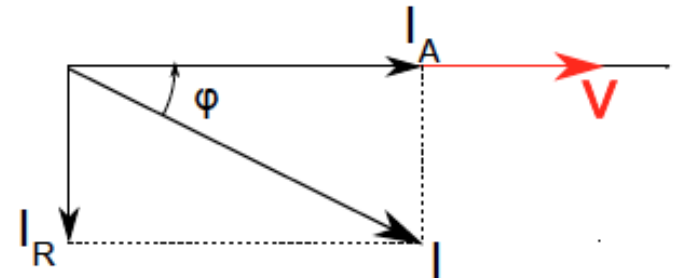- But:  $\underline{S} = \underline{V} \underline{I}^* = P + jQ$



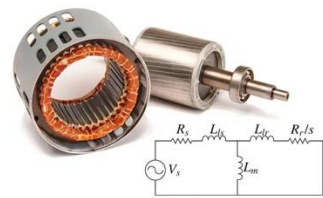

## II – Power in sinusoidal regime

### Single-phase – Expressions of powers


- The **resistive load** (e.g. a furnace)

=>  $\varphi = 0$ , voltage in phase with current.

=>  $\cos(\varphi) = 1$ ,  $\sin(\varphi) = 0$

=>  $P = V \cdot I$  and  $Q = 0$

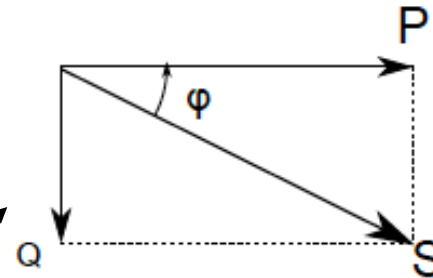A resistive dipole consumes no reactive power



- The **inductive load** (e.g. a motor)

=> The voltage leads the current,  $\varphi > 0$

=>  $\sin(\varphi) > 0$ ,  $Q > 0$


An inductive dipole consumes reactive power

- The **capacitive load** (e.g. a capacitor)

=> The voltage lags the current,  $\varphi < 0$

=>  $\sin(\varphi) < 0$ ,  $Q < 0$


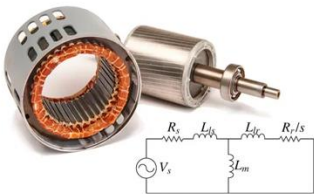
An inductive dipole supplies reactive power




## II – Power in sinusoidal regime

### Single-phase

- Measurement of powers

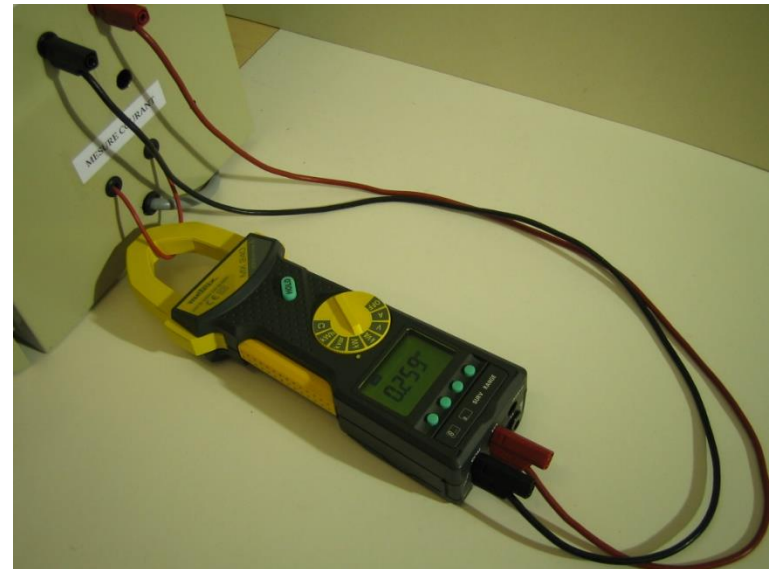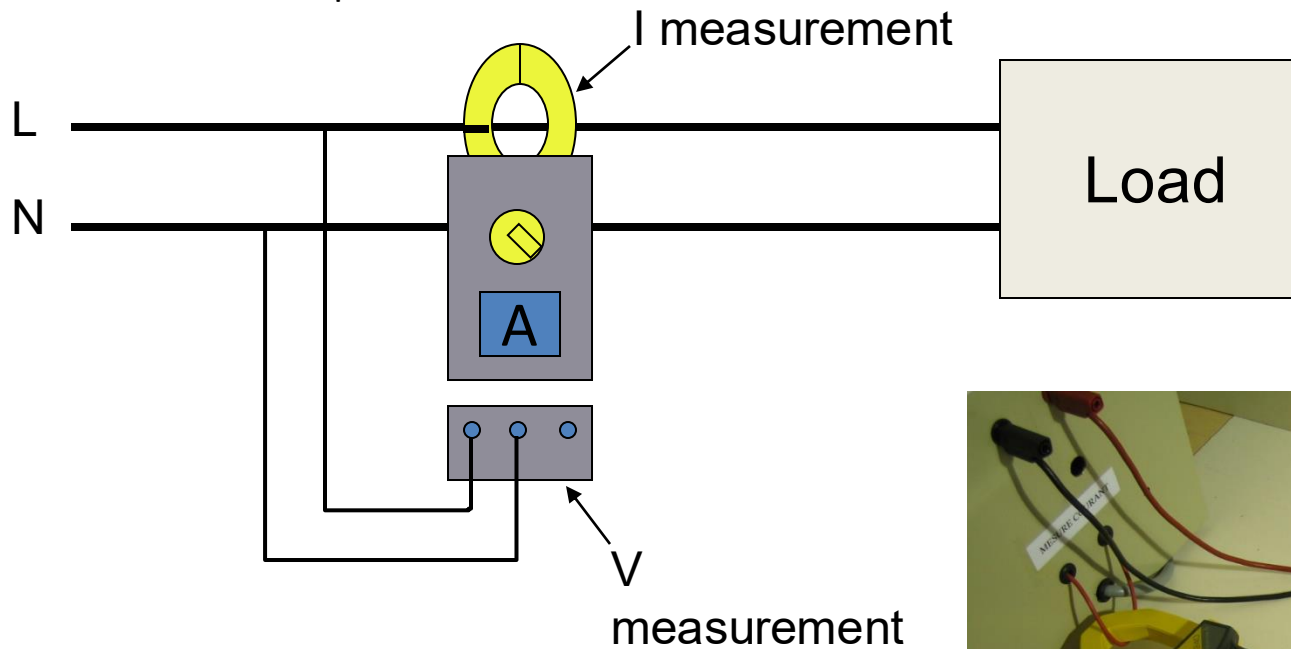

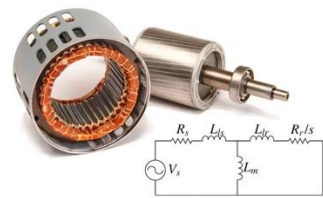

## II – Power in sinusoidal regime

### Single-phase

- Measurement of powers

