


II – Power in sinusoidal regime

Sine-wave: definitions


- A sinusoidal quantity $s(t)$ (voltage, current, flux or magnetic field) is written:

$$s(t) = \widehat{S} \cdot \cos(\omega t + / - \varphi)$$
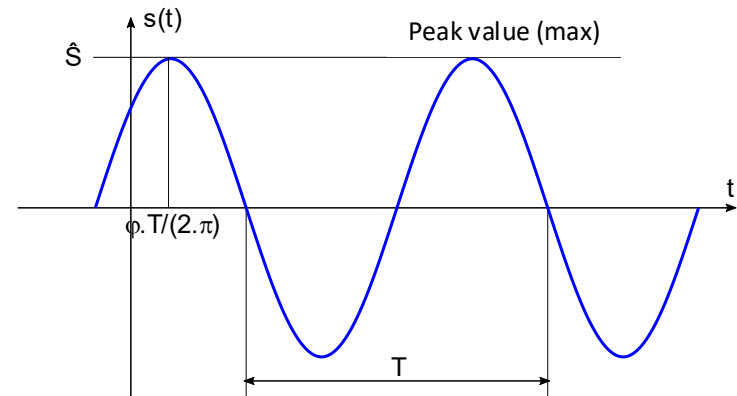
$$s(t) = S\sqrt{2} \cdot \cos(\omega t + / - \varphi)$$




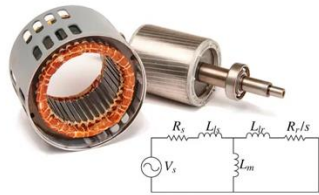
- $s(t)$: quantity which evolves with time in sinusoidal form
- S : RMS value of the quantity,
- \widehat{S} : maximum value reached by the quantity $s(t) \Rightarrow \widehat{S} = S \cdot \sqrt{2}$,
- ω : electrical pulsation in rad/s of the magnitude, $\omega = 2 \cdot \pi \cdot f = 2 \cdot \pi / T$,
- f : signal frequency and T : signal period,
- φ : phase at origin (at $t = 0$).



II – Power in sinusoidal regime


Single-phase

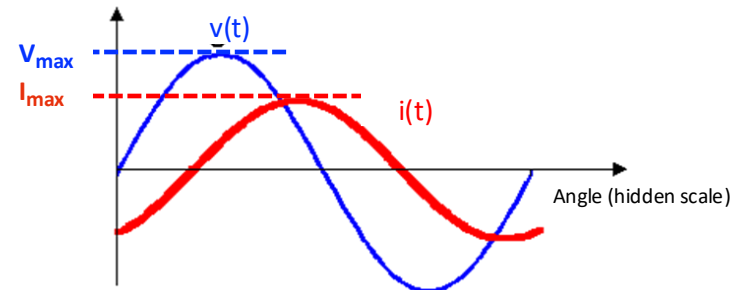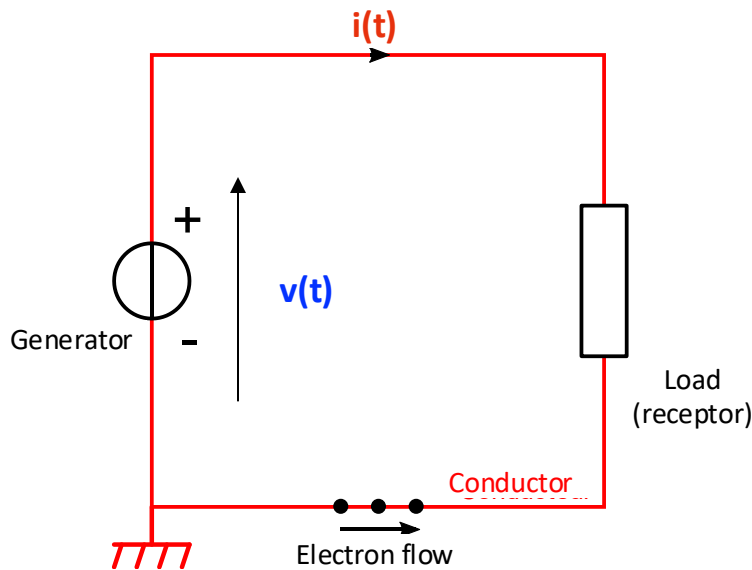- Most of the world's electrical energy is generated, transmitted and distributed in the form of sinusoidal voltages.
- Any periodic signal can be studied by decomposing it down into sinusoidal signals using a Fourier transform.



$$v(t) = \hat{V} \cdot \sin(\omega t)$$
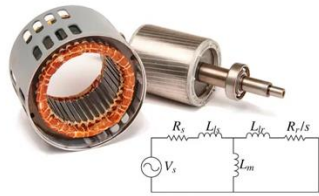
$$i(t) = \hat{I} \cdot \sin(\omega t - \varphi)$$




II – Power in sinusoidal regime

Single-phase – Average and RMS values


- The **AVERAGE VALUE** of any current (same for the voltage) is the value that a direct current carrying the same amount of electricity would have.

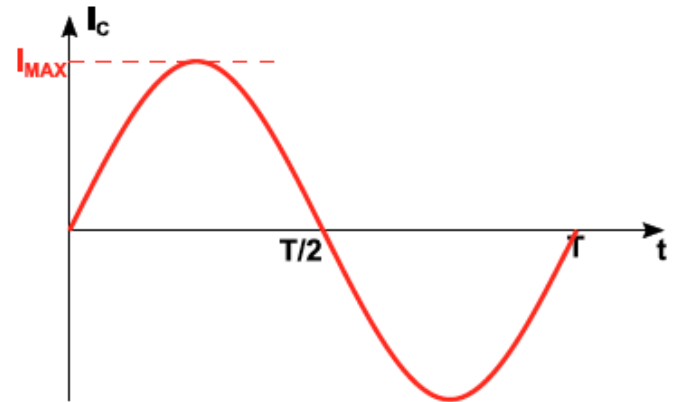
$$I_{MOY} = \frac{1}{T} \int i(t) dt \quad I_{MOY} = 0$$



- The **RMS** (Root Mean square) **VALUE** of any current is the value that a direct current carrying the same amount of energy would have.
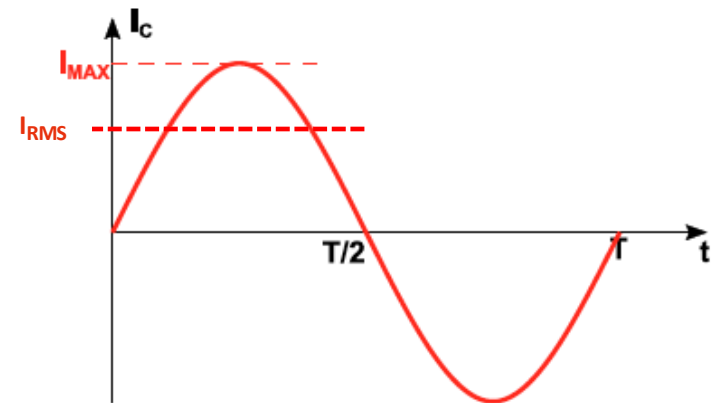
$$I_{RMS} = \sqrt{\frac{1}{T} \int i^2(t) dt} \quad I_{RMS} = \frac{I_{MAX}}{\sqrt{2}}$$



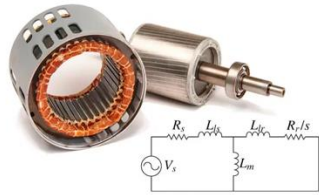

II – Power in sinusoidal regime

Single-phase – Average and RMS values

- **Exercise:** demonstrate the expression of I_{moy} and I_{RMS}


Average value

- $I_{\text{MOY}} = \frac{1}{T} \int_0^T i(t) dt$
- $I_{\text{MOY}} = \frac{1}{T} \int_0^T I_{\text{MAX}} \cdot \sin(\omega t) dt$
- $I_{\text{MOY}} = \frac{1}{T} \left[I_{\text{MAX}} \cdot \frac{-\cos(\omega t)}{\omega} \right]_0^T$
- $I_{\text{MOY}} = \frac{I_{\text{MAX}}}{\omega T} \cdot [-\cos(\omega T) + \cos(0)]$
- $I_{\text{MOY}} = \frac{I_{\text{MAX}}}{\omega T} \cdot (-1 + 1)$
- $I_{\text{MOY}} = 0$

$$\cos 2a = 1 - 2\sin^2 a \text{ et } \sin^2 a = \frac{1 - \cos 2a}{2}$$

RMS value


- $I_{\text{EFF}} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$
- $I_{\text{EFF}}^2 = \frac{1}{T} \int_0^T i^2(t) dt$
- $I_{\text{EFF}}^2 = \frac{1}{T} \int_0^T (I_{\text{MAX}} \cdot \sin(\omega t))^2 dt$
- $I_{\text{EFF}}^2 = \frac{1}{T} \int_0^T (I_{\text{MAX}})^2 \cdot (\sin(\omega t))^2 dt$
- $I_{\text{EFF}}^2 = \frac{1}{T} \int_0^T (I_{\text{MAX}})^2 \frac{(1 - \cos 2\omega t)}{2} dt$
- $I_{\text{EFF}}^2 = \frac{I_{\text{MAX}}^2}{2 \cdot T} \int_0^T (1 - \cos 2\omega t) dt$
- $I_{\text{EFF}}^2 = \frac{I_{\text{MAX}}^2}{2 \cdot T} \left[t - \frac{\sin(2\omega t)}{2\omega} \right]_0^T$
- $I_{\text{EFF}}^2 = \frac{I_{\text{MAX}}^2}{2} \left[\frac{T-0}{T} - \frac{\sin(2\omega T) - \sin(0)}{2\omega T} \right]$
- $I_{\text{EFF}}^2 = \frac{I_{\text{MAX}}^2}{2} \left[1 - \frac{0-0}{4\pi} \right]$
- $I_{\text{EFF}}^2 = \frac{I_{\text{MAX}}^2}{2}$
- $I_{\text{EFF}} = \frac{I_{\text{MAX}}}{\sqrt{2}}$

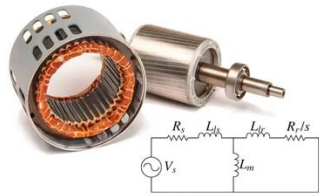


II – Power in sinusoidal regime

Single-phase – Fresnel vector representation

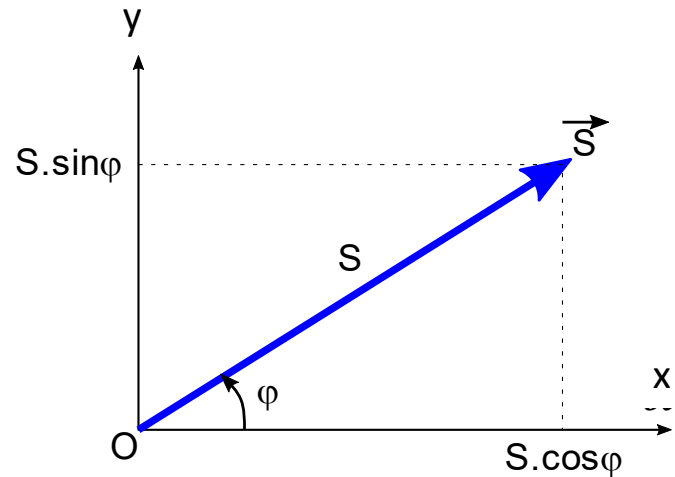- Associated with $s(t)$ is a **vector** \vec{S} known as the **Fresnel vector**, of norm S (RMS value) rotating around the origin point O at an angular frequency ω .



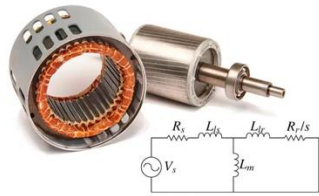- Since all signals have the same angular frequency ω , vectors in the same Fresnel diagram rotate at the same speed. Therefore, they are represented at $t = 0$.



II – Power in sinusoidal regime


Single-phase – Complex representation

- Complex representation:

- Reminder: Euler's formula

$$e^{ix} = \cos x + i \cdot \sin x$$
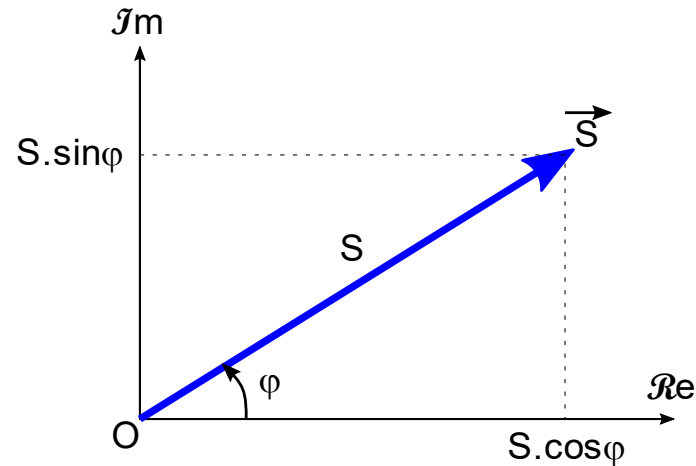
$$S \cdot \cos \varphi + j \cdot S \cdot \sin \varphi = S \cdot e^{j\varphi} = \underline{S}$$




- Complex quantity

- Complex amplitude

$$\begin{cases} \underline{s}(t) = S\sqrt{2} \cdot e^{j(\omega t + \varphi)} \\ s(t) = \Re(\underline{s}(t)) \end{cases}$$

$$\underline{s} = \underline{S}\sqrt{2} \cdot e^{j\omega t}$$

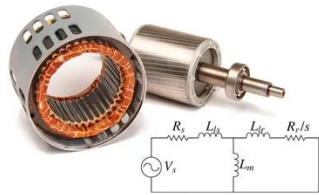
where $\underline{S} = S \cdot e^{j\varphi} = [S; \varphi]$



II – Power in sinusoidal regime


Single-phase – Complex representation

- Sum:

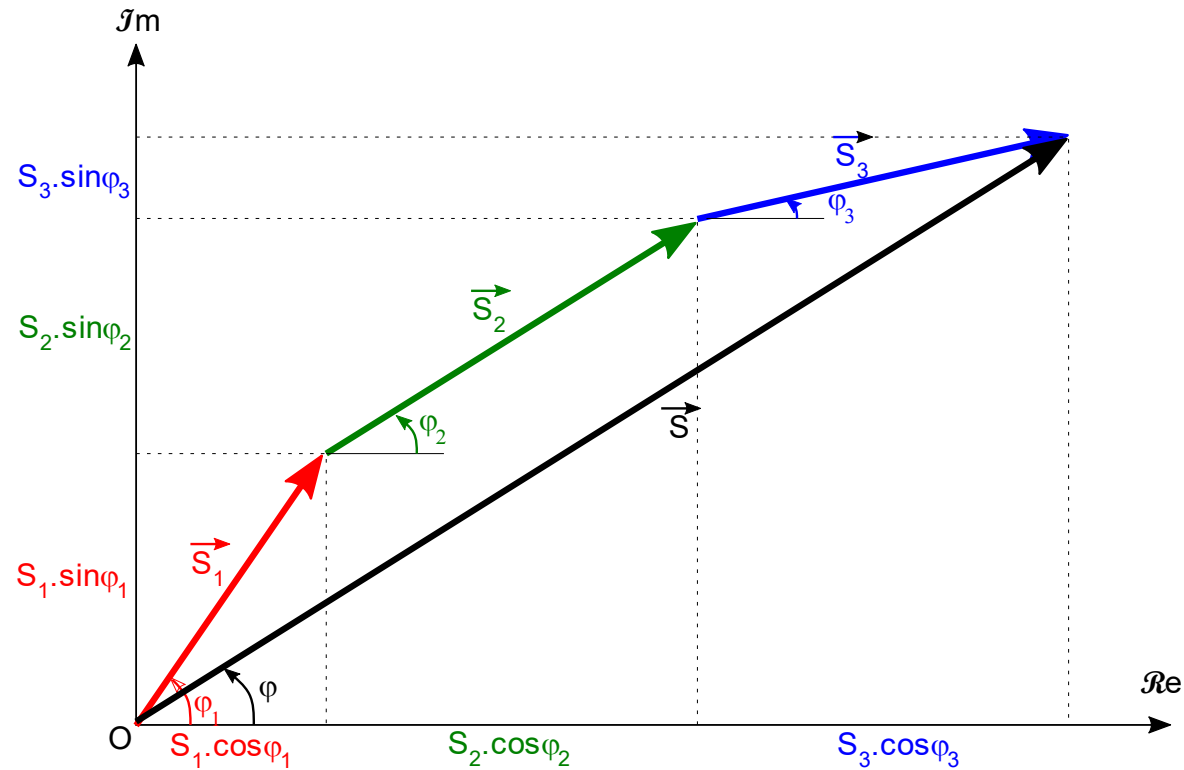

$$S = \sqrt{(\sum S_i \cdot \cos \varphi_i)^2 + (\sum S_i \cdot \sin \varphi_i)^2}$$
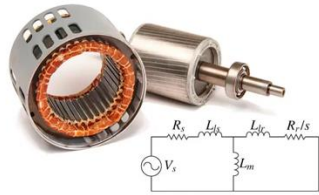
$$\tan \varphi = \frac{\sum S_i \cdot \sin \varphi_i}{\sum S_i \cdot \cos \varphi_i}$$




II – Power in sinusoidal regime

Single-phase – Complex representation

- Derivate: $\underline{s}(t) = \hat{S} \cdot e^{j(\omega t + \varphi)} = \hat{S} \cdot \cos(\omega t + \varphi) + j \cdot \hat{S} \cdot \sin(\omega t + \varphi)$
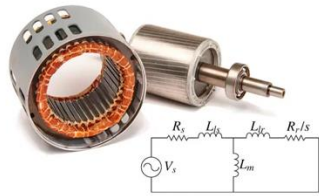
$$\frac{d\underline{s}(t)}{dt} = \frac{d(\hat{S} \cdot \cos(\omega t + \varphi) + j \cdot \hat{S} \cdot \sin(\omega t + \varphi))}{dt}$$



II – Power in sinusoidal regime


Single-phase – Complex representation

- Derivate: $\underline{s}(t) = \hat{S} \cdot e^{j(\omega t + \varphi)} = \hat{S} \cdot \cos(\omega t + \varphi) + j \cdot \hat{S} \cdot \sin(\omega t + \varphi)$

$$\begin{aligned} \frac{d\underline{s}(t)}{dt} &= \frac{d(\hat{S} \cdot \cos(\omega t + \varphi) + j \cdot \hat{S} \cdot \sin(\omega t + \varphi))}{dt} \\ \frac{d\underline{s}(t)}{dt} &= \hat{S} \cdot [-\omega \cdot \sin(\omega t + \varphi) + j \cdot \omega \cdot \cos(\omega t + \varphi)] \\ \frac{d\underline{s}(t)}{dt} &= j \cdot \omega \cdot \hat{S} \cdot \left[-\frac{\sin(\omega t + \varphi)}{j} + \cos(\omega t + \varphi) \right] \\ \frac{d\underline{s}(t)}{dt} &= j \cdot \omega \cdot \hat{S} \cdot [\cos(\omega t + \varphi) + j \sin(\omega t + \varphi)] \\ \frac{d\underline{s}(t)}{dt} &= j \cdot \omega \cdot \underline{s}(t) \end{aligned}$$

Derivative with respect to time: **rotation of $+\pi/2$ rad** in the complex plane
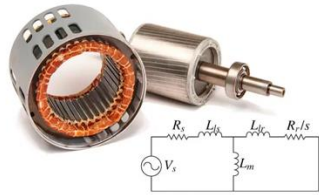
$$\frac{d\underline{s}(t)}{dt} = j \cdot \omega \cdot \underline{s}(t) = \left[\mathbf{S} \cdot \omega; \varphi + \frac{\pi}{2} \right]$$




II – Power in sinusoidal regime

Single-phase – Complex representation

- Integrate:

$$\underline{s}(t) = \hat{S} \cdot e^{j(\omega t + \varphi)} = \hat{S} \cdot \cos(\omega t + \varphi) + j \cdot \hat{S} \cdot \sin(\omega t + \varphi)$$
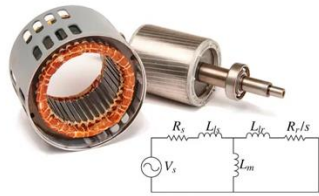
$$\int \underline{s}(t) \cdot dt = \int (\hat{S} \cdot \cos(\omega t + \varphi) + j \cdot \hat{S} \cdot \sin(\omega t + \varphi)) \cdot dt$$



II – Power in sinusoidal regime

Single-phase – Complex representation

- Integrate:
$$\int \underline{s}(t). dt = \int (\hat{S}. \cos(\omega t + \varphi) + j. \hat{S}. \sin(\omega t + \varphi)). dt$$

$$\int \underline{s}(t). dt = \hat{S}. \left[\int (\cos(\omega t + \varphi)). dt + j. \int (\sin(\omega t + \varphi)). dt \right] = \hat{S}. \left[\frac{\sin(\omega t + \varphi)}{\omega} + j. \frac{-\cos(\omega t + \varphi)}{\omega} \right]$$

$$\int \underline{s}(t). dt = \frac{\hat{S}}{j\omega}. [j. \sin(\omega t + \varphi) + j.j. (-\cos(\omega t + \varphi))]$$


$$\int \underline{s}(t). dt = \frac{\hat{S}}{j\omega}. [j. \sin(\omega t + \varphi) + \cos(\omega t + \varphi)]$$

$$\int \underline{s}(t). dt = \frac{1}{j\omega}. \hat{S}. [\cos(\omega t + \varphi) + j. \sin(\omega t + \varphi)]$$

$$\int \underline{s}(t). dt = \frac{\underline{s}(t)}{j. \omega}$$

Time integration: **rotation of $-\pi/2$ rad** in the complex plane

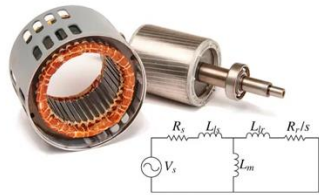
$$\int \underline{s}(t). dt = \frac{\underline{s}(t)}{j. \omega} = \left[\frac{\underline{S}}{\omega}; \varphi - \frac{\pi}{2} \right]$$



II – Power in sinusoidal regime

Single-phase – Complex impedances

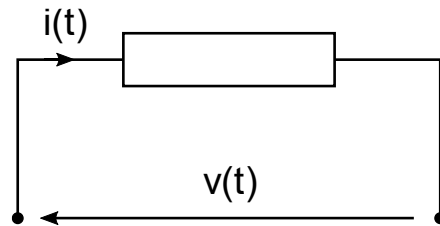
- Let us consider a passive linear dipole, in receptor convention, subjected to a sinusoidal voltage $v(t)$ and flowed by a sinusoidal current $i(t)$:




- We write:

$$\begin{cases} v(t) = V\sqrt{2} \cdot \cos(\omega t + \varphi_V) \\ i(t) = I\sqrt{2} \cdot \cos(\omega t + \varphi_I) \end{cases}$$
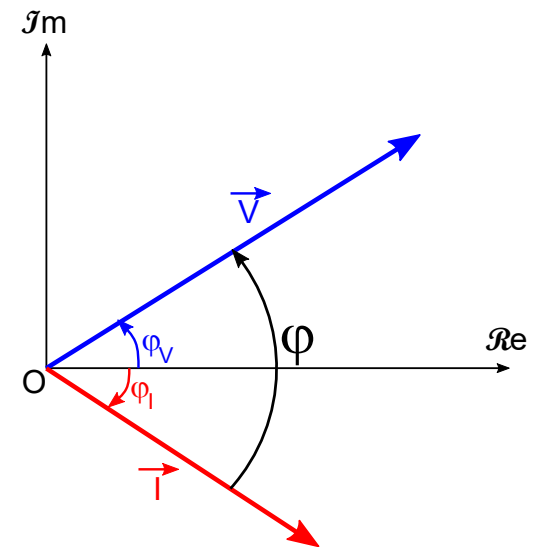
$$\begin{cases} \underline{V} = V \cdot e^{j\varphi_V} = [V; \varphi_V] \\ \underline{I} = I \cdot e^{j\varphi_I} = [I; \varphi_I] \end{cases}$$



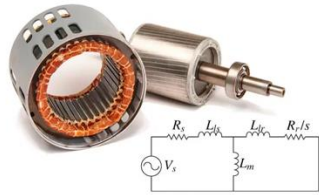

II – Power in sinusoidal regime

Single-phase – Complex impedances

- The complex impedance is defined as:

$$\underline{Z} = \frac{\underline{V}}{\underline{I}} = R + jX = \underline{Z} = Z \cdot e^{j\varphi}$$

- where:

- Z : dipole impedance $Z = \|\underline{Z}\| = \frac{V}{I}$

- φ : phase shift angle of voltage with respect to current:



$$\varphi = \text{Arg}\underline{Z} = \varphi_V - \varphi_I$$


- R : resistance in Ohms of the dipole, real part of the complex impedance:

$$R = \Re(\underline{Z}) = Z \cdot \cos\varphi$$

- X : reactance in Ohms of the dipole, imaginary part of the complex impedance
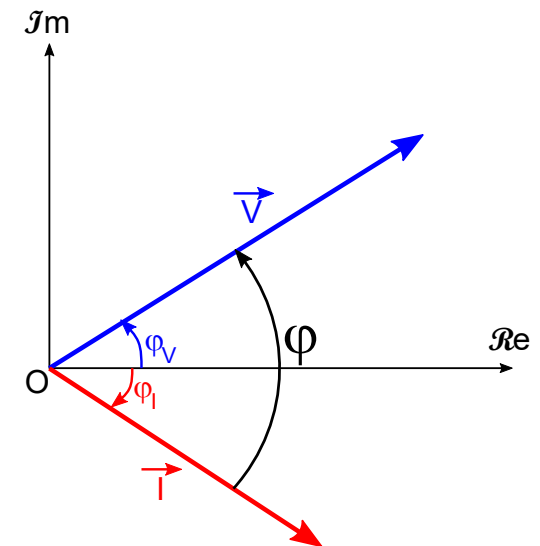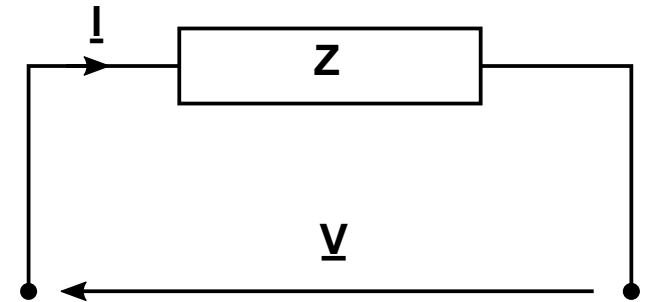
$$X = \Im(\underline{Z}) = Z \cdot \sin\varphi$$



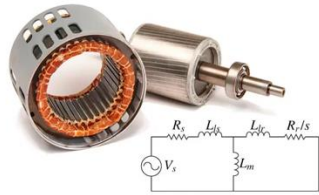

II – Power in sinusoidal regime

Single-phase – Complex impedances


$$\underline{Z} = \frac{\underline{V}}{\underline{I}} = R + jX = \underline{Z} = Z \cdot e^{j\varphi}$$

- where:

- Z : dipole impedance $Z = \|\underline{Z}\| = \frac{V}{I}$

- φ : phase shift angle of voltage with respect to current:
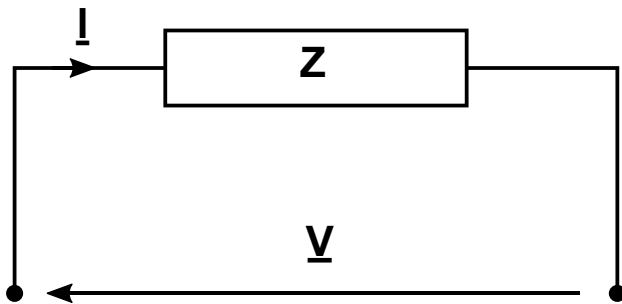
$$\varphi = \text{Arg}\underline{Z} = \varphi_V - \varphi_I$$



- If $\varphi > 0$, the voltage leads the current, impedance or load is said to be **inductive**.


(Motors, Transformers, Electromagnets)

- If $\varphi = 0$, the voltage is in phase with the current, impedance or load is said to be **resistive**.

(Resistors, Furnaces, Regulated baths)

- If $\varphi < 0$, the voltage lags the current, impedance or load is said to be **capacitive**.


(Capacitors)

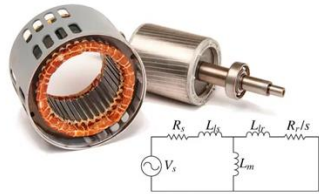

II – Power in sinusoidal regime

Single-phase – linear dipoles

	Resistor	Ideal coil	Ideal capacitor
Definition	An electrical resistor is an electrical dipole that opposes the flow of current	A “coil” is an electrical dipole that opposes the variation of electric current and can store energy in electromagnetic form.	A “capacitor” is an electrical dipole that resists variation in the voltage to which it is subjected, and can store energy in electrostatic form.
Characteristics	R : resistance in Ω (Ohm)	L : Coil inductance in H (Henry)	C : Capacitance in F (Farad)
AC regime	$V_R(t) = R \cdot i(t)$	$V_L(t) = L \cdot \frac{di(t)}{dt}$	$V_C(t) = \frac{1}{C} \cdot \int i(t) \cdot dt$
Symbolic representation in receptor convention			
Sinusoidal regime	$\underline{V}_R = R \cdot \underline{I}$	$\underline{V}_L = jL\omega \cdot \underline{I}$	$\underline{V}_C = \frac{1}{jC\omega} \cdot \underline{I}$
Impedance	$\underline{Z} = R = [R; 0]$	$\underline{Z} = jL\omega = [L\omega; \frac{\pi}{2}]$	$\underline{Z} = \frac{1}{jC\omega} = [\frac{1}{jC\omega}; -\frac{\pi}{2}]$

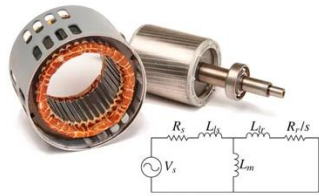

II – Power in sinusoidal regime

Single-phase – Fresnel (vector) representation

$$\underline{V}_R = [R \cdot I; 0]$$


V_R and I are in phase


$$\underline{V}_L = [L\omega \cdot I; \frac{\pi}{2}]$$

V_L leads I in quadrature

$$\underline{V}_C = [\frac{I}{C\omega}; -\frac{\pi}{2}]$$

V_C lags I in quadrature

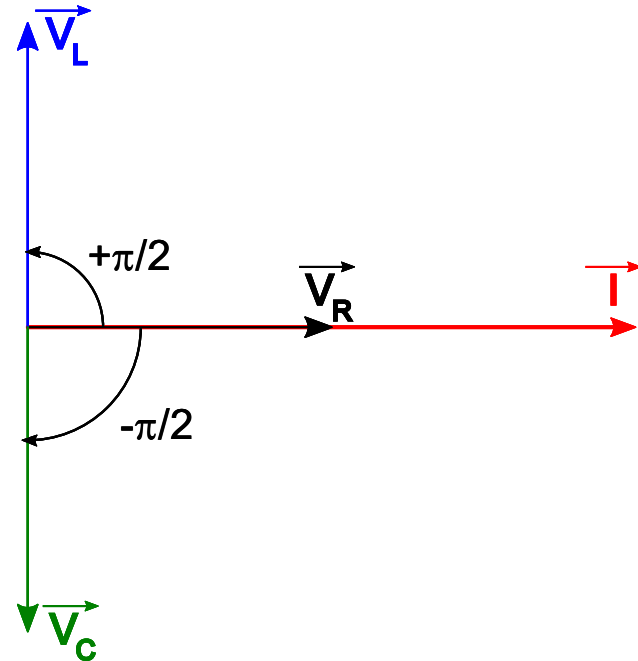

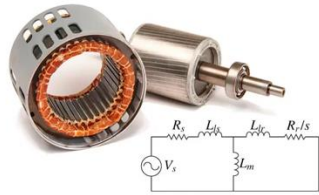

II – Power in sinusoidal regime

Single-phase – Expressions of powers

- Instantaneous power (in W): $p(t) = v(t) \times i(t)$

=> exchange of energy, heat or work, between the network and the dipole at each instant


- Active power or average power (in W) – General expression:

$$P = \langle p(t) \rangle = \frac{1}{T} \int_0^T p(t) \cdot dt = \frac{1}{T} \int_0^T v(t) \cdot i(t) \cdot dt$$

=> Balance of energy exchanged between the network and the dipole over a period T

=> If $P > 0$, the dipole consumes energy, it operates a receptor

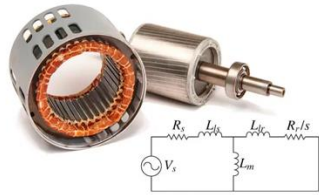=> If $P < 0$, the dipole supplies energy, it operates a generator



II – Power in sinusoidal regime

Single-phase – Expressions of powers

- Linear receptor in sinusoidal regime

- Through which a current $i(t)$ flows

$$i(t) = I\sqrt{2} \times \sin(\omega t)$$

- Subjected to a voltage $v(t)$



$$v(t) = V\sqrt{2} \times \sin(\omega t + \varphi)$$


φ positive, voltage ahead of current, inductive receiver

φ zero, voltage in phase with current, resistive receiver

φ negative, voltage lagging current, capacitive receiver

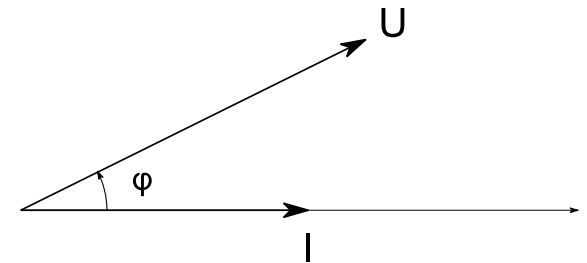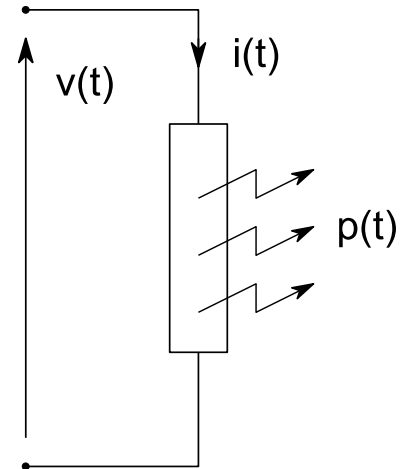- Instantaneous power $p(t) = v(t) \times i(t)$




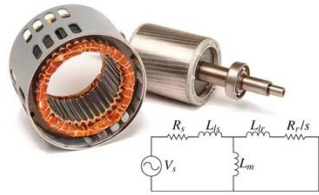


II – Power in sinusoidal regime

Single-phase – Expressions of powers

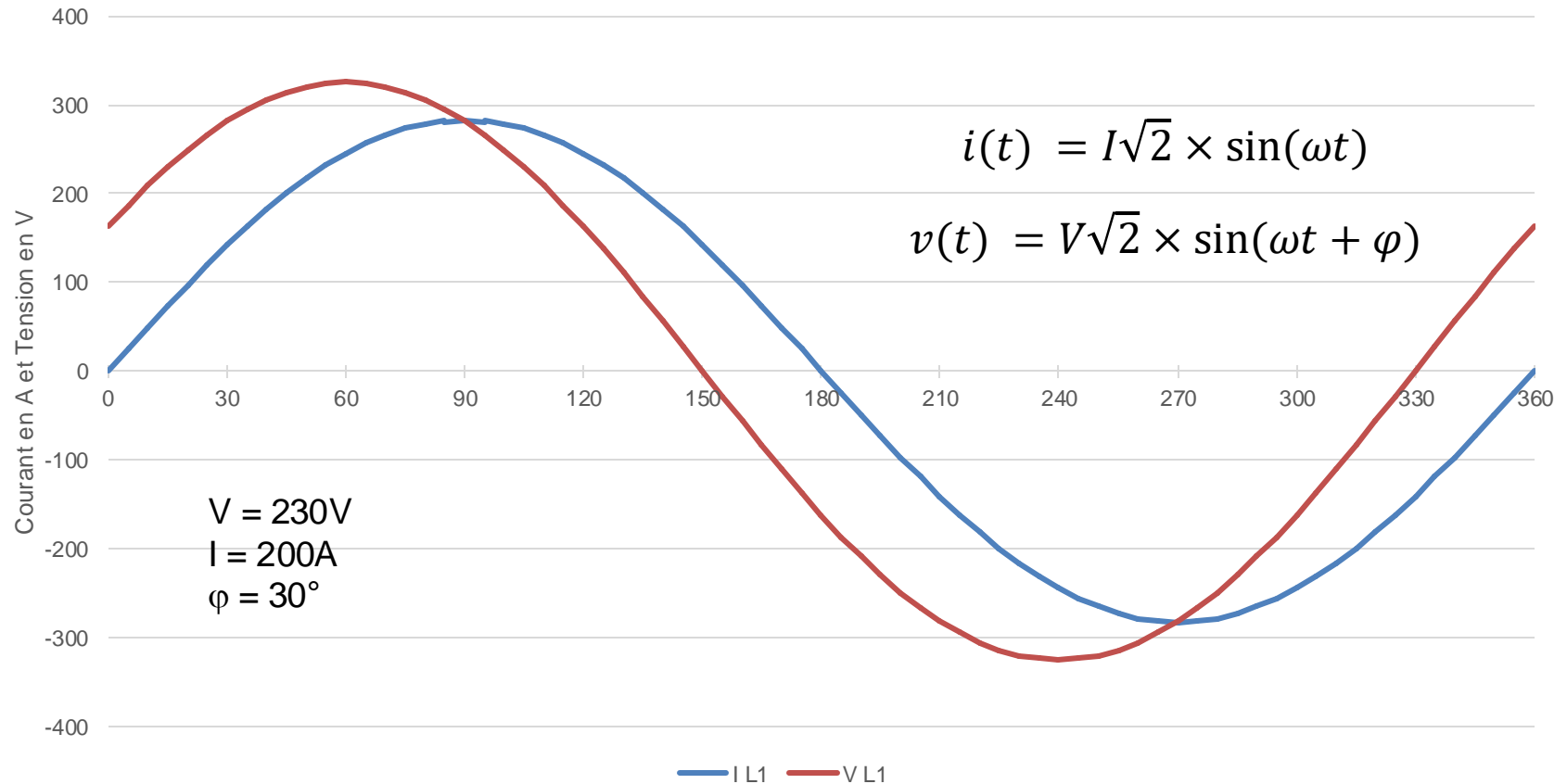- Linear receptor in sinusoidal regime: current and voltages



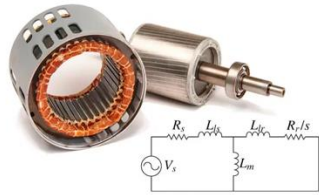

II – Power in sinusoidal regime

Single-phase – Expressions of powers

- Linear receptor in sinusoidal regime
- Instantaneous power:

$$p(t) = v(t) \times i(t)$$


$$p(t) = V\sqrt{2} \times \sin(\omega t + \varphi) \times I\sqrt{2} \times \sin(\omega t)$$

$$p(t) = 2 \times V \times I \times \sin(\omega t + \varphi) \times \sin(\omega t)$$

$$\sin a \times \sin b = \frac{1}{2} (\cos(a - b) + \cos(a + b))$$

$$p(t) = 2 \times V \times I \times \frac{1}{2} (\cos(\omega t + \varphi - \omega t) + \cos(\omega t + \varphi + \omega t))$$

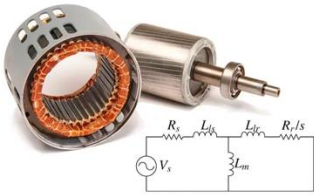
$$p(t) = V I \cos(\varphi) + V I \cos(2 \omega t + \varphi)$$




II – Power in sinusoidal regime

Single-phase – Expressions of powers

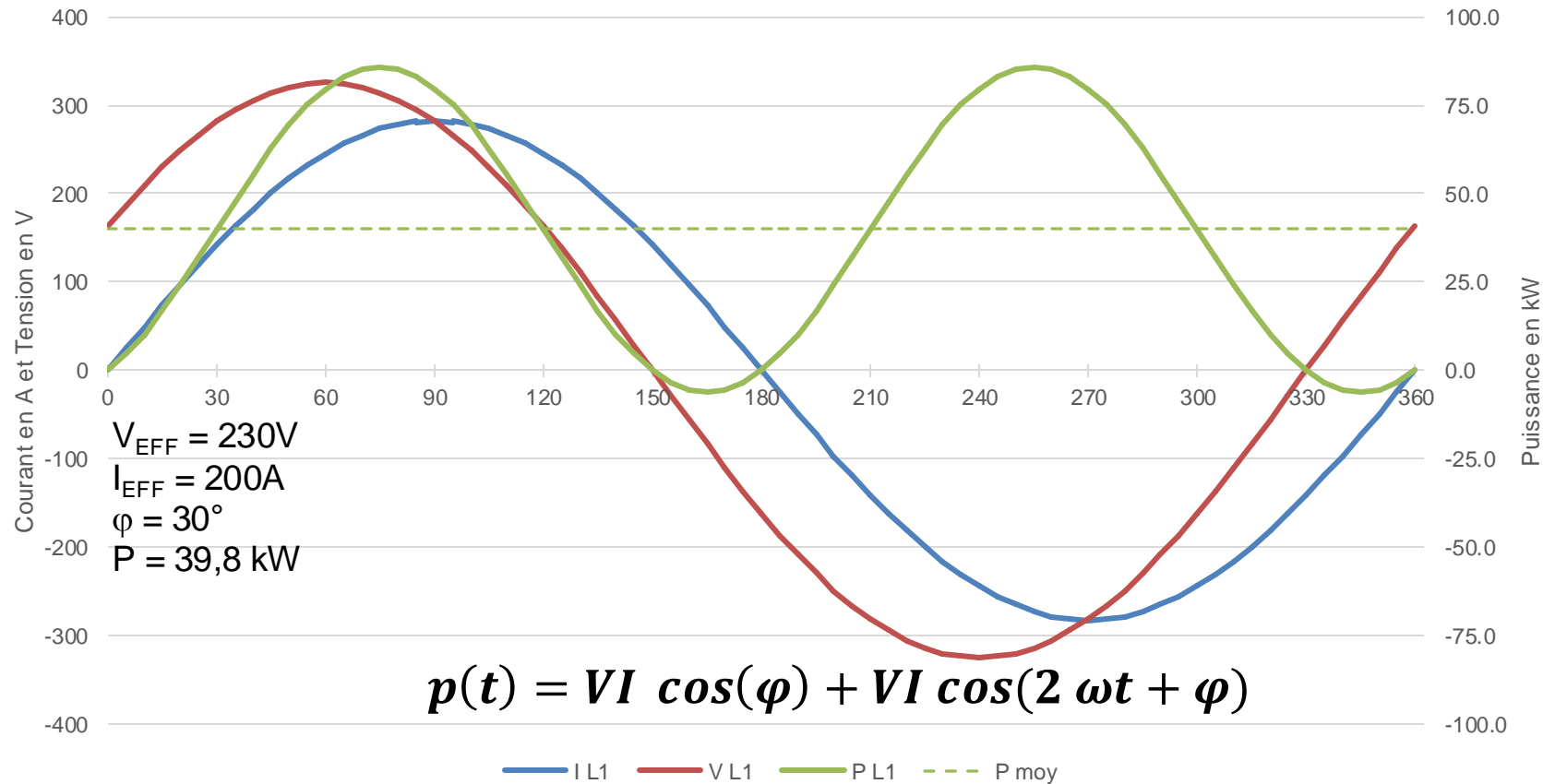- Linear receptor in sinusoidal regime: current, voltage and power



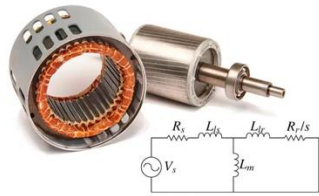

II – Power in sinusoidal regime

Single-phase – Expressions of powers

- Instantaneous power (in W): $p(t) = v(t) \times i(t)$

=> exchange of energy, heat or work, between the network and the dipole at each instant

- Active power or average power (in W): $P = \langle p(t) \rangle = V I \cos(\varphi)$


=> Balance of energy exchanged between the network and the dipole over a period T

- Apparent power (in VA): $S = V \cdot I$

=> Design value (voltage for insulation, current for conductor cross-section)

- Power factor (general expression):
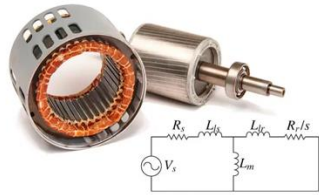
$$FP = \frac{P}{S} \quad FP = \cos(\varphi) \quad \Rightarrow \text{Sinusoidal regime only}$$



II – Power in sinusoidal regime

Single-phase – Expressions of powers

- Reactive power:

- Projection of I on the axes: $\vec{I} = \vec{I}_A + \vec{I}_R$

=> Active current: $I_A = I \cdot \cos(\varphi)$



=> Reactive current: $I_R = I \cdot \sin(\varphi)$


- Reminder of the active power (W):

$$P = V \cdot I \cdot \cos(\varphi) = V \cdot I_A$$

- By analogy, the reactive power (given in VAR) can be written:
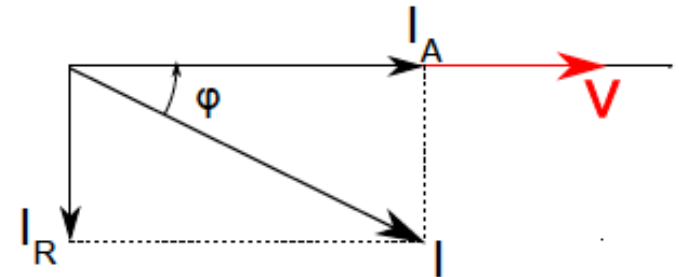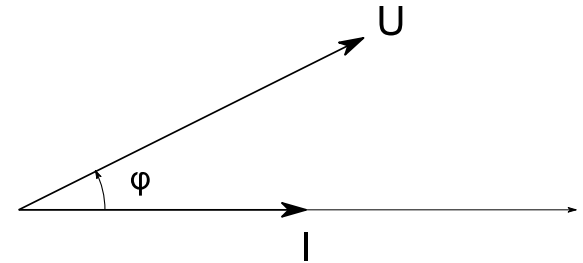
$$Q = V \cdot I \cdot \sin(\varphi) = V \cdot I_R$$



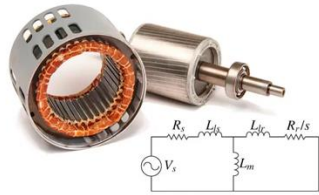

II – Power in sinusoidal regime

Single-phase – Expressions of powers

- Relation between powers S, P and Q:



$$P = V \cdot I \cdot \cos(\varphi)$$


$$Q = V \cdot I \cdot \sin(\varphi) = P \cdot \tan(\varphi)$$

$$S^2 = P^2 + Q^2$$

- Note that: $S \neq P + Q$

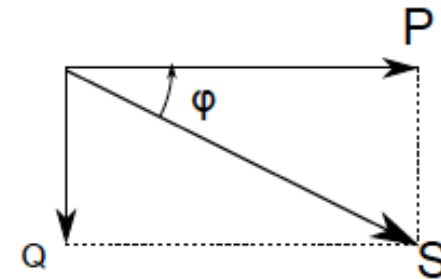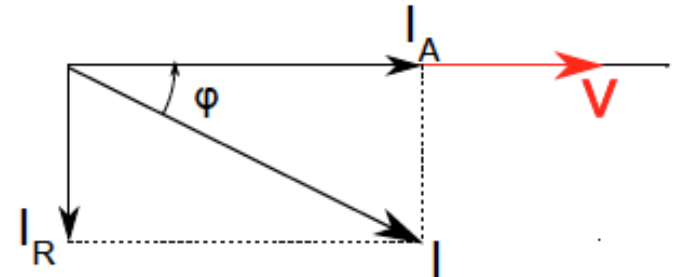- But: $\underline{S} = \underline{V} \underline{I}^* = P + jQ$



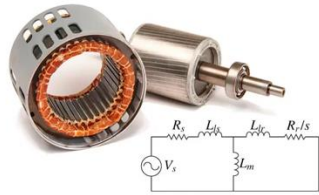

II – Power in sinusoidal regime

Single-phase – Expressions of powers

- The **resistive load** (e.g. a furnace)

=> $\varphi = 0$, voltage in phase with current.

=> $\cos(\varphi) = 1$, $\sin(\varphi) = 0$

=> $P = V \cdot I$ and $Q = 0$

A resistive dipole consumes no reactive power

- The **inductive load** (e.g. a motor)

=> The voltage leads the current, $\varphi > 0$

=> $\sin(\varphi) > 0$, $Q > 0$



An inductive dipole consumes reactive power


- The **capacitive load** (e.g. a capacitor)

=> The voltage lags the current, $\varphi < 0$

=> $\sin(\varphi) < 0$, $Q < 0$

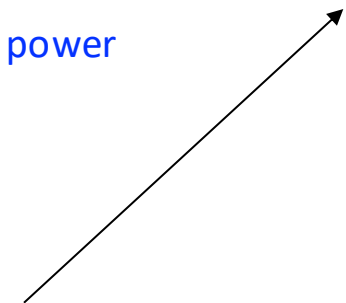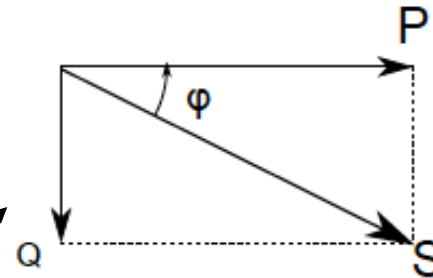An inductive dipole supplies reactive power





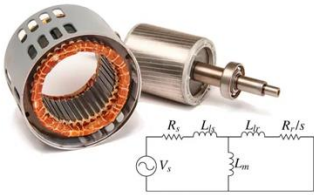


II – Power in sinusoidal regime

Single-phase

- Measurement of powers

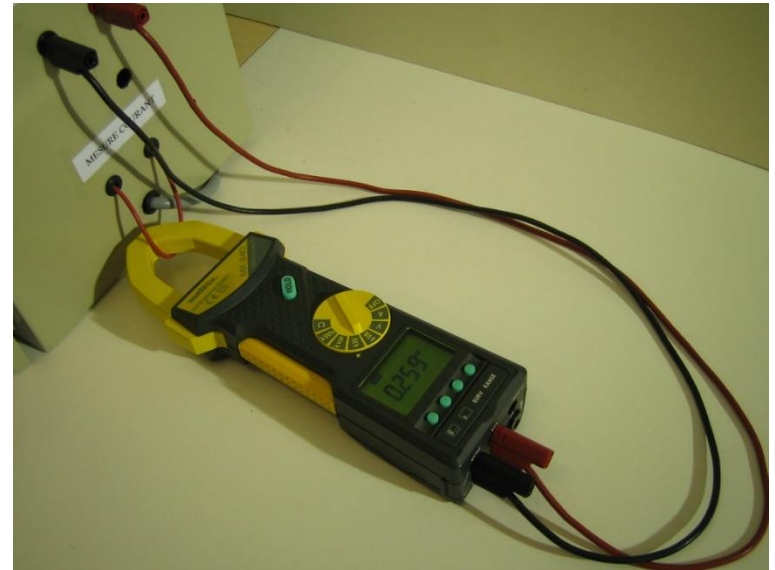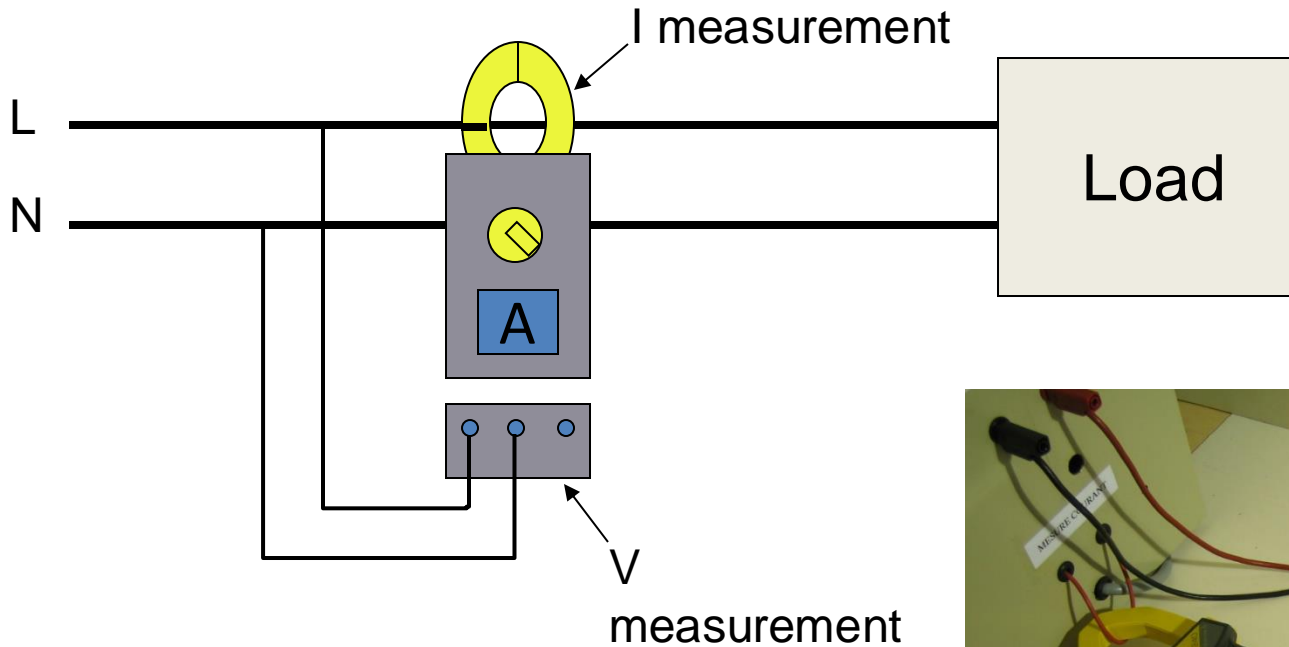

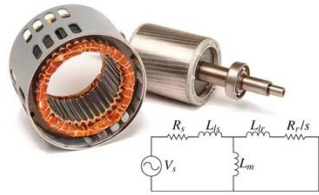

II – Power in sinusoidal regime

Single-phase

- Measurement of powers

