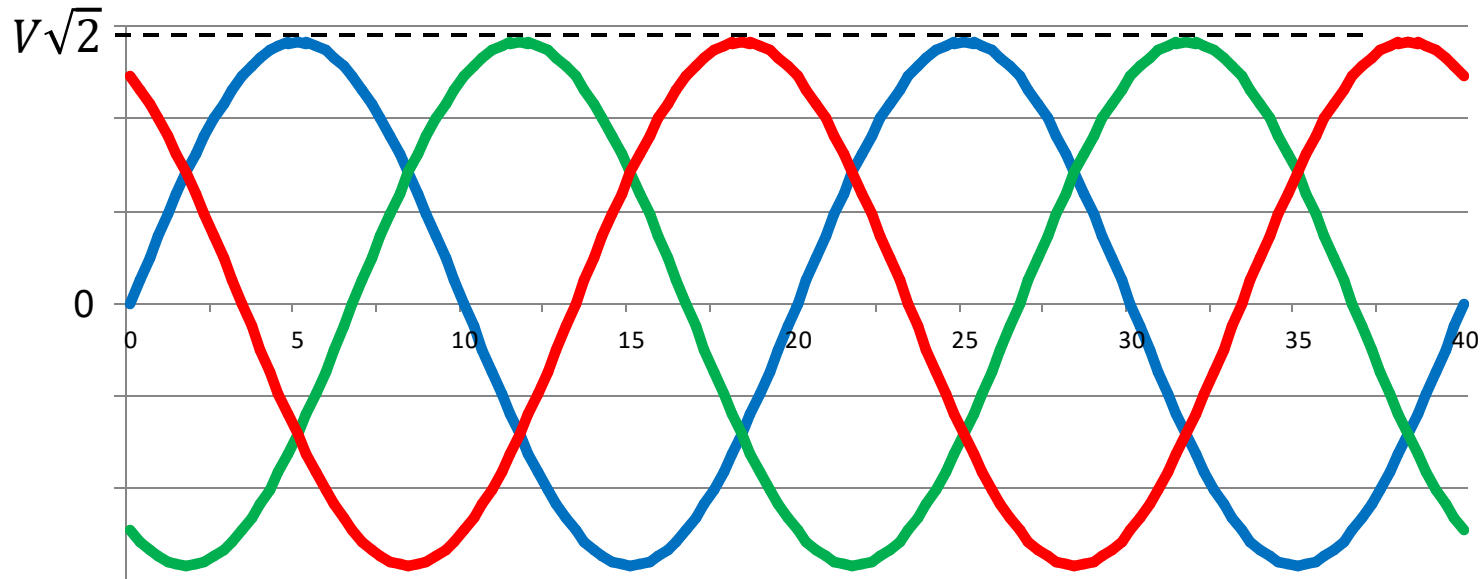


II – Power in sinusoidal regime

3-phase


- A **direct balanced three-phase voltage system** is a set of 3 sinusoidal voltages [phase-shifted by \$2\pi/3\$](#)



$$v_1(t) = V\sqrt{2}\sin(\omega t)$$

$$v_2(t) = V\sqrt{2}\sin\left(\omega t - \frac{2\pi}{3}\right)$$

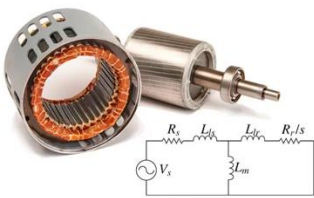
$$v_3(t) = V\sqrt{2}\sin\left(\omega t - \frac{4\pi}{3}\right) = V\sqrt{2}\sin\left(\omega t + \frac{2\pi}{3}\right)$$



II – Power in sinusoidal regime


3-phase

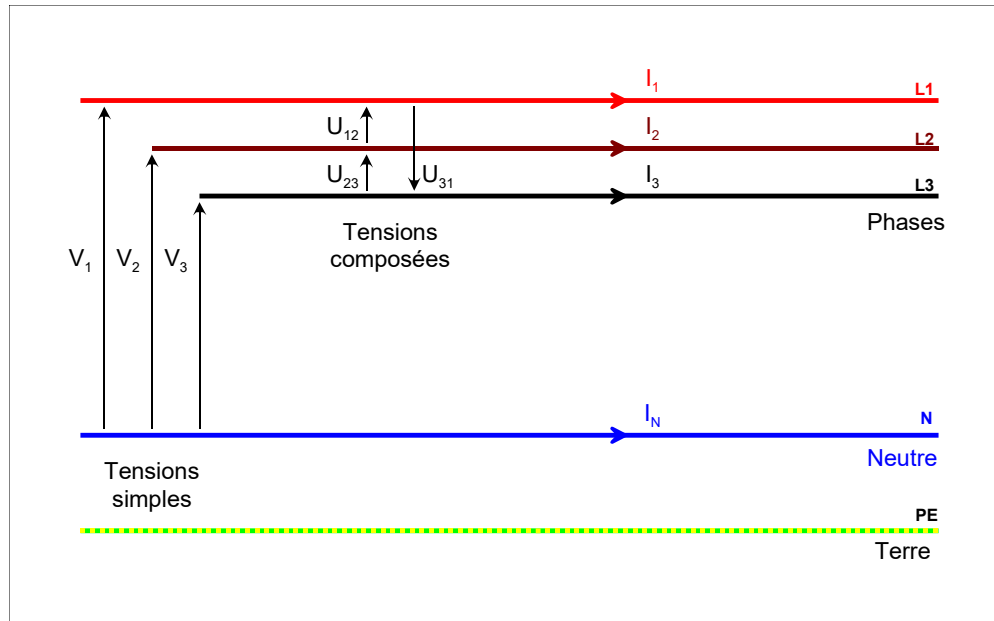- Distribution of 3-phase system: BT (low voltage) 230V / 400 V



- 4-wire (three phases and neutral)
- Voltages 230 / 400 volts: internationally harmonized
- $U = 400V$ / $V = 230V$ / $f = 50Hz$
Transformer neutral grounded.


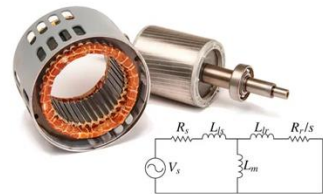
- V is the **line voltage** = potential difference between a line and the neutral
- U is the **phase voltage** = potential difference between two phases



II – Power in sinusoidal regime

3-phase

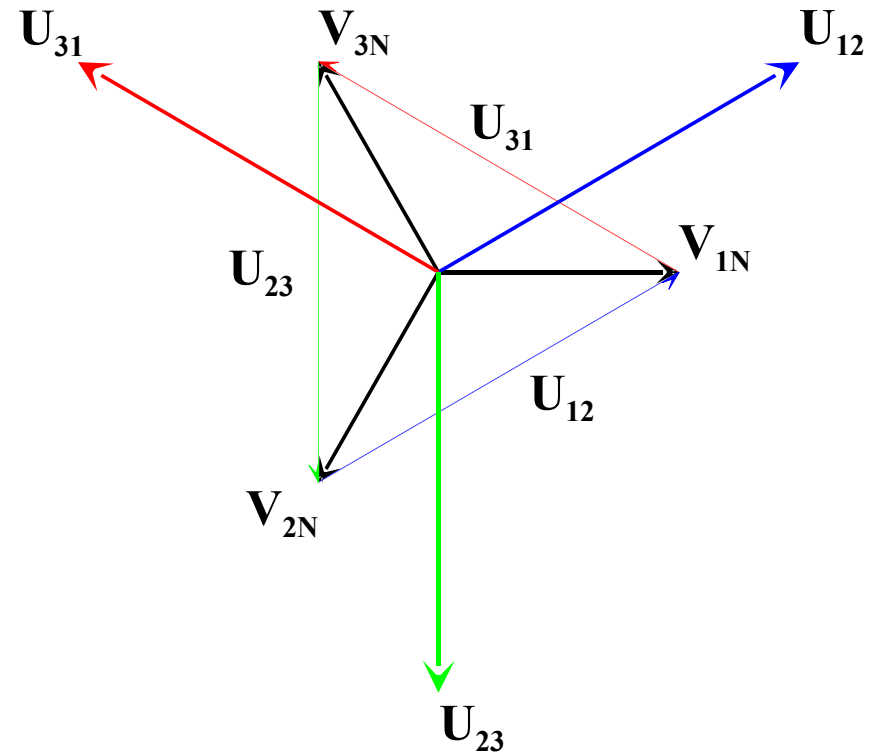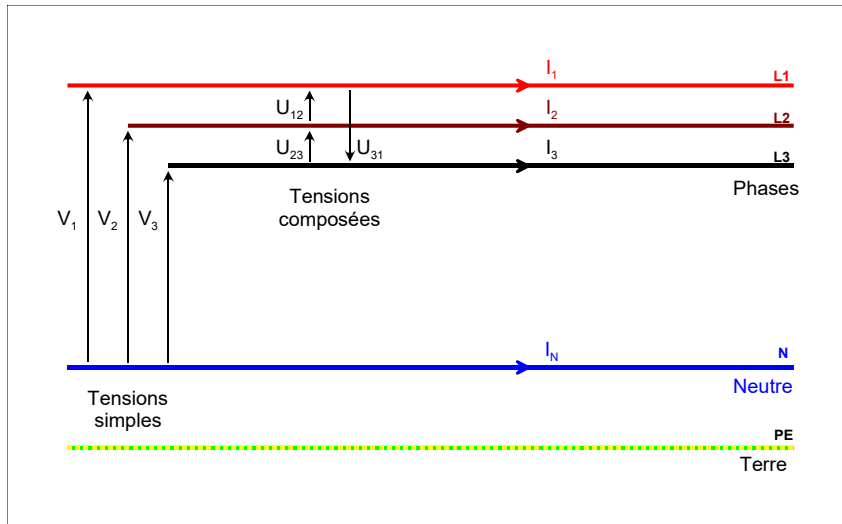- Distribution of 3-phase system: direct balanced 3-phase system




$$\vec{V}_1 + \vec{V}_2 + \vec{V}_3 = 0$$

$$\vec{U}_{12} = \vec{V}_1 - \vec{V}_2$$

$$\vec{U}_{23} = \vec{V}_2 - \vec{V}_3$$

$$\vec{U}_{31} = \vec{V}_3 - \vec{V}_1$$
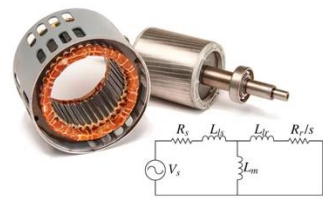
$$\vec{U}_{12} + \vec{U}_{23} + \vec{U}_{31} = 0$$



II – Power in sinusoidal regime

3-phase

- Distribution of 3-phase system: [direct balanced 3-phase system](#)


- Relation between U and V

$$\vec{U}_{12} = \vec{V}_1 - \vec{V}_2$$


$$\vec{U}_{23} = \vec{V}_2 - \vec{V}_3$$

$$\vec{U}_{31} = \vec{V}_3 - \vec{V}_1$$

$$U = \sqrt{3}V$$


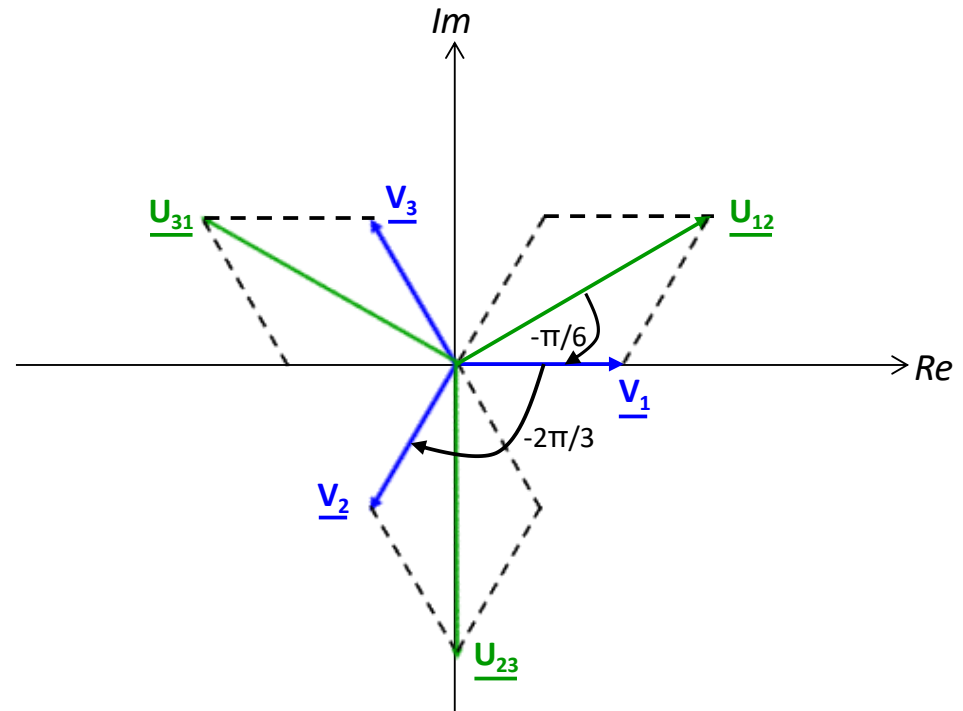


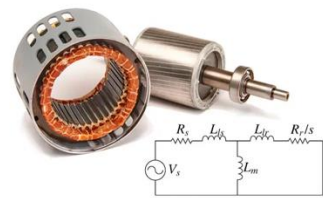- Balanced: $V_1 = V_2 = V_3 = V$ $U_{12} = U_{23} = U_{31} = U$



II – Power in sinusoidal regime

3-phase: summary

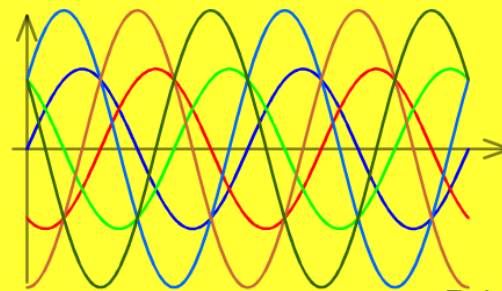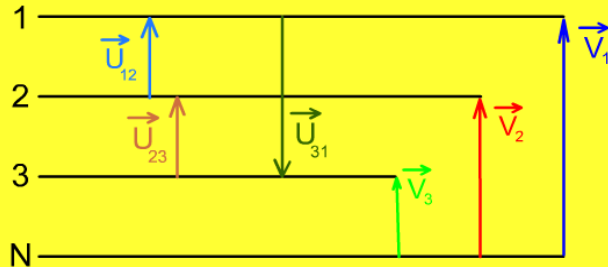

Tensions simples

$$v_1(t) = V_{\text{MAX}} \sin(\omega t)$$

$$v_2(t) = V_{\text{MAX}} \sin(\omega t - \frac{2\pi}{3})$$


$$v_3(t) = V_{\text{MAX}} \sin(\omega t - \frac{4\pi}{3})$$

avec

$$\omega = 2\pi \cdot f$$

$$V_{\text{MAX}} = V \cdot \sqrt{2}$$
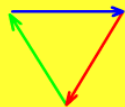
$$\vec{V}_1 + \vec{V}_2 + \vec{V}_3 = \vec{0}$$



Tensions composées

$$u_{12}(t) = U_{\text{MAX}} \sin(\omega t + \frac{\pi}{6})$$

$$u_{23}(t) = U_{\text{MAX}} \sin(\omega t - \frac{\pi}{2})$$


$$u_{31}(t) = U_{\text{MAX}} \sin(\omega t - \frac{7\pi}{6})$$

avec

$$\omega = 2\pi \cdot f$$

$$U_{\text{MAX}} = U \cdot \sqrt{2}$$
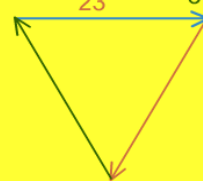
$$\vec{U}_{12} + \vec{U}_{23} + \vec{U}_{31} = \vec{0}$$





Relations entre tensions simples et composées

$$\vec{U}_{12} = \vec{V}_1 - \vec{V}_2$$

$$\vec{U}_{23} = \vec{V}_2 - \vec{V}_3$$

$$\vec{U}_{31} = \vec{V}_3 - \vec{V}_1$$

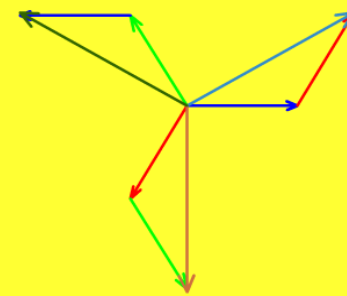

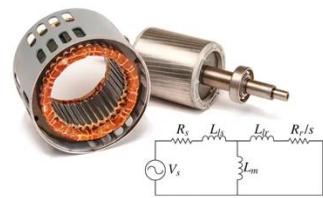


II – Power in sinusoidal regime


3-phase: connections


- Both the 3-phase generator and the 3-phase load can be connected according to the following configurations:

Y connection

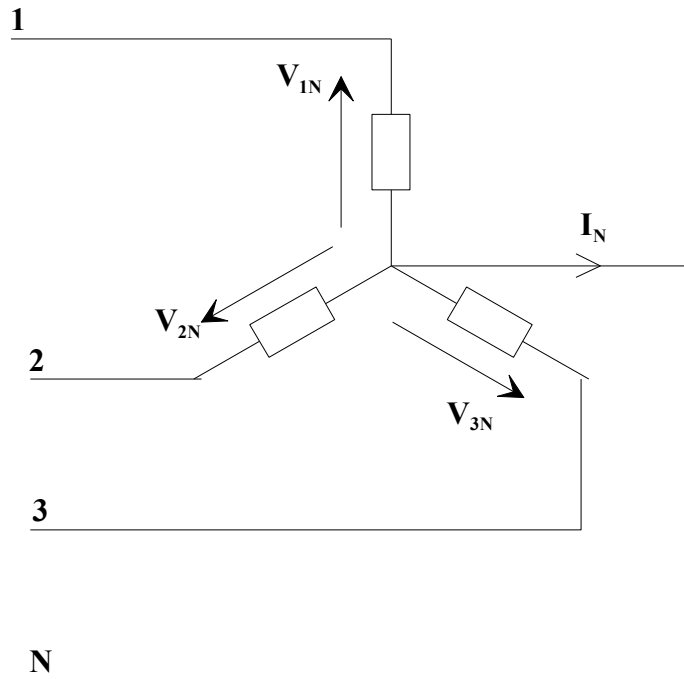

Delta connection

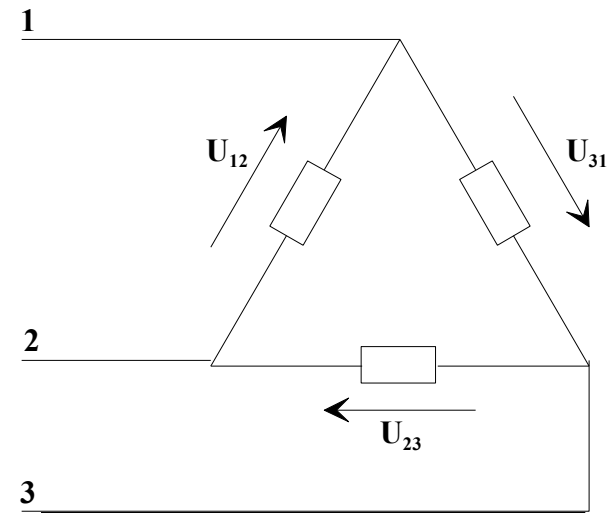

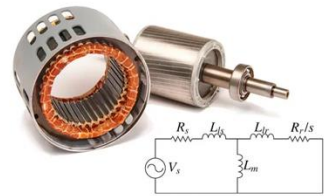


II – Power in sinusoidal regime

3-phase: connections


Y connection

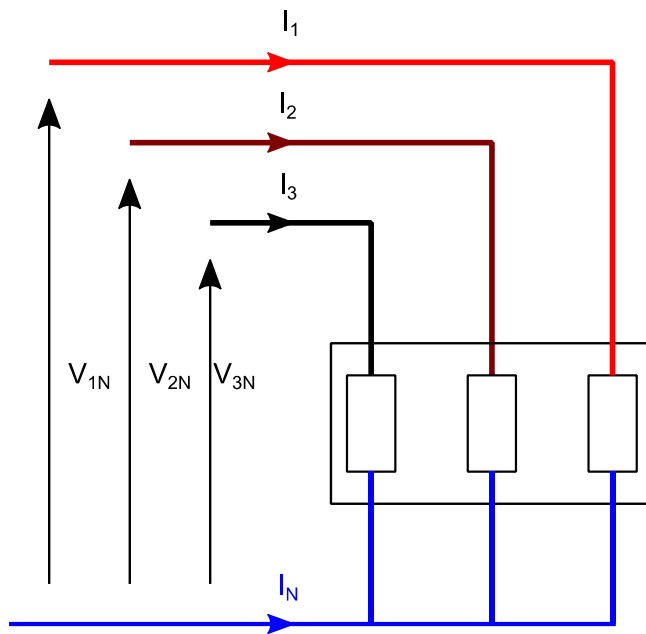
- Each receptor is connected **between phase and neutral** and subjected to the line voltage



Delta connection

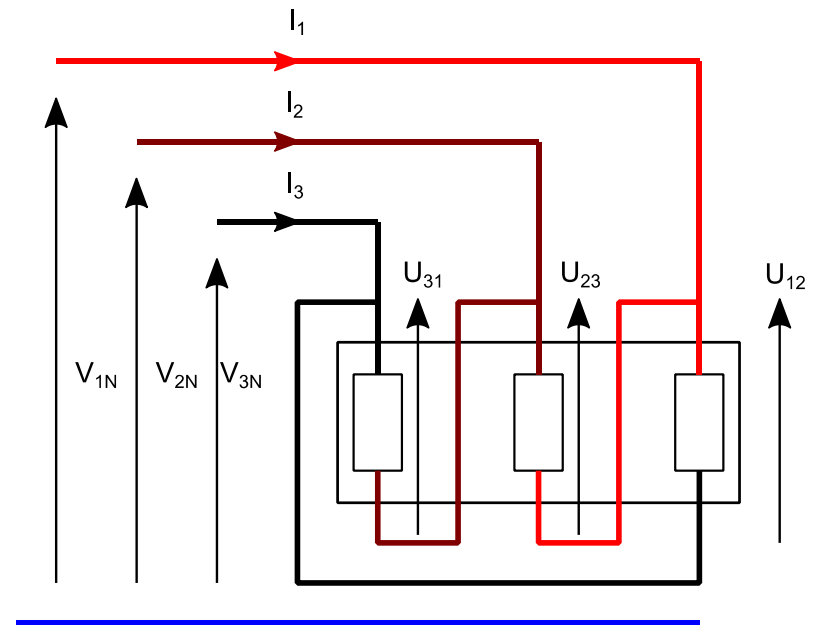
- Each receptor is connected **between two phases** and subjected to a phase voltage



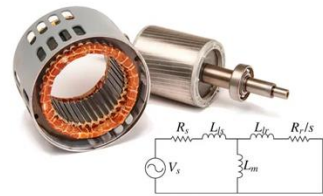

II – Power in sinusoidal regime

3-phase: Y connection

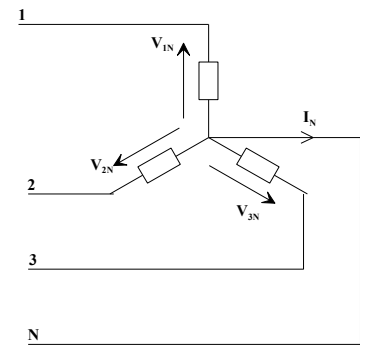

- Each receptor is connected between phase and neutral.

- Each receptor is subjected to the **line voltage** “ V ”.

- The line current “ I ” flows through each receptor.


- If all three loads are **identical**, we speak of a **balanced** load. $I_1 = I_2 = I_3 = I$


⇒ No current flows in the neutral wire.

⇒ $I_N = 0$ A.

⇒ Its presence is therefore unnecessary.
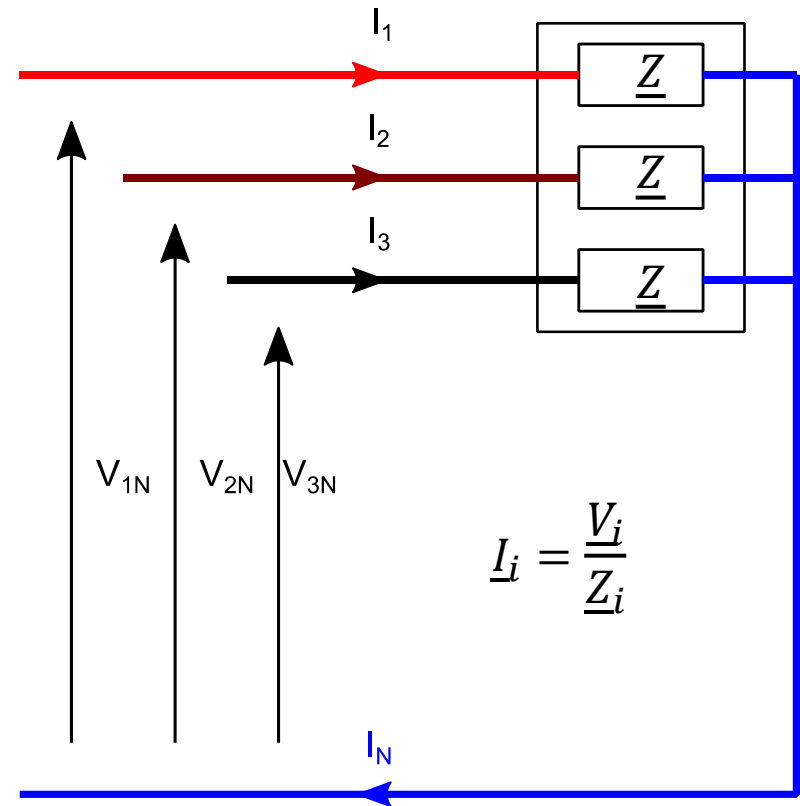
$$\vec{I}_1 + \vec{I}_2 + \vec{I}_3 = 0$$



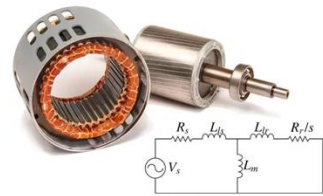

II – Power in sinusoidal regime

3-phase: Delta connection



- Each receptor is connected between two phases.
- It is subjected to a **phase voltage** “U”.
- The phase current “J” flows through the receptor.
- Here, the neutral cannot be wired. Its presence is also not necessary.
- Kirchoff’s law:

$$\vec{I}_1 = \vec{J}_3 - \vec{J}_2$$


$$\vec{I}_2 = \vec{J}_1 - \vec{J}_3$$

$$\vec{J}_3 = \vec{J}_2 - \vec{J}_1$$

$$I = J\sqrt{3}$$

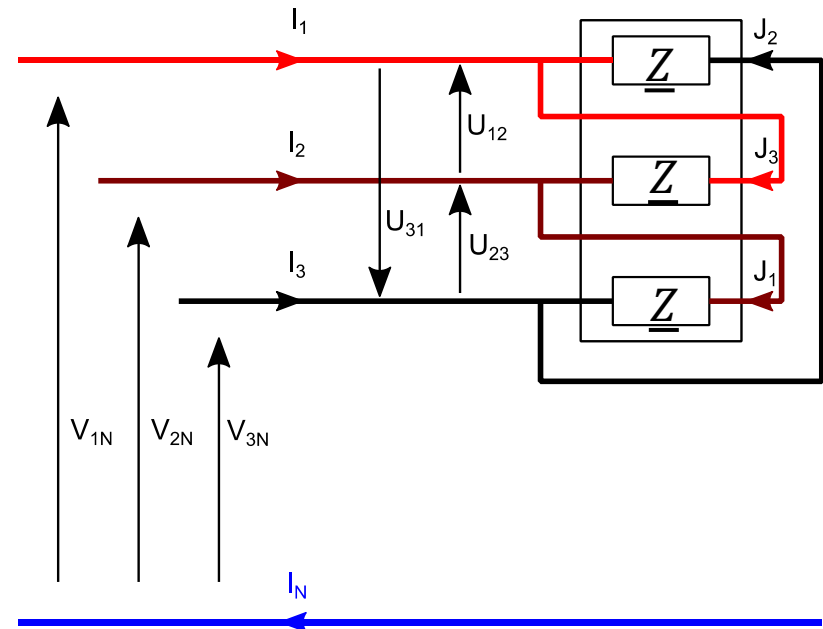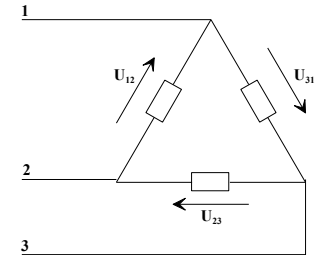


- Balanced load: $J_1 = J_2 = J_3 = J$

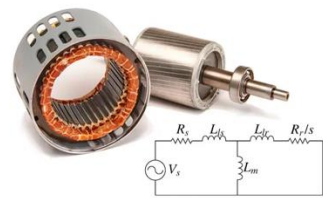

II – Power in sinusoidal regime

3-phase: powers


- Boucherot's theorem:

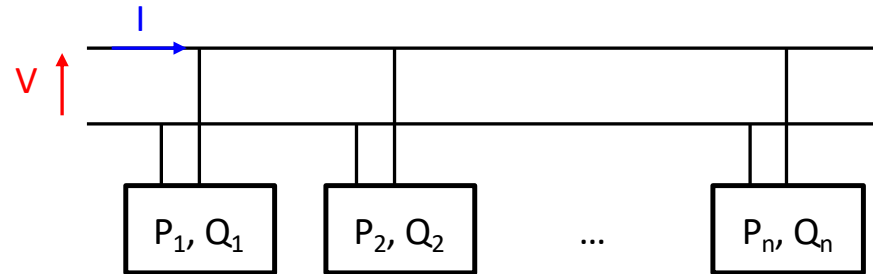

The active power of a system is the sum of the active powers of each element, as are reactive power and complex apparent power. Note that this is not true for real apparent power.

- Active power: $P_{tot} = P_1 + P_2 + \dots + P_n$
- Reactive power: $Q_{tot} = Q_1 + Q_2 + \dots + Q_n$
- Complex apparent power: $\underline{S}_{tot} = \underline{S}_1 + \underline{S}_2 + \dots + \underline{S}_n$
- But: $S_{tot} \neq S_1 + S_2 + \dots + S_n$
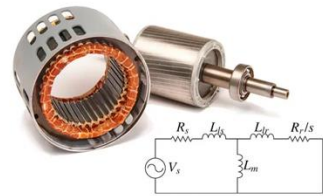
$$S = V \cdot I = \sqrt{P_{tot}^2 + Q_{tot}^2}$$



II – Power in sinusoidal regime

3-phase: powers

- Boucherot's theorem: *general* Y-connection load

$$P = V_1 I_1 \cos(\varphi_1) + V_2 I_2 \cos(\varphi_2) + V_3 I_3 \cos(\varphi_3)$$

$$Q = V_1 I_1 \sin(\varphi_1) + V_2 I_2 \sin(\varphi_2) + V_3 I_3 \sin(\varphi_3)$$

- For the **balanced load**:


$$P = 3VI \cos(\varphi) = \sqrt{3}UI \cos(\varphi)$$


$$Q = 3VI \sin(\varphi) = \sqrt{3}UI \sin(\varphi)$$

$$S = 3VI = \sqrt{3}UI$$

$$FP = \frac{P}{S}$$

$$S^2 = P^2 + Q^2$$

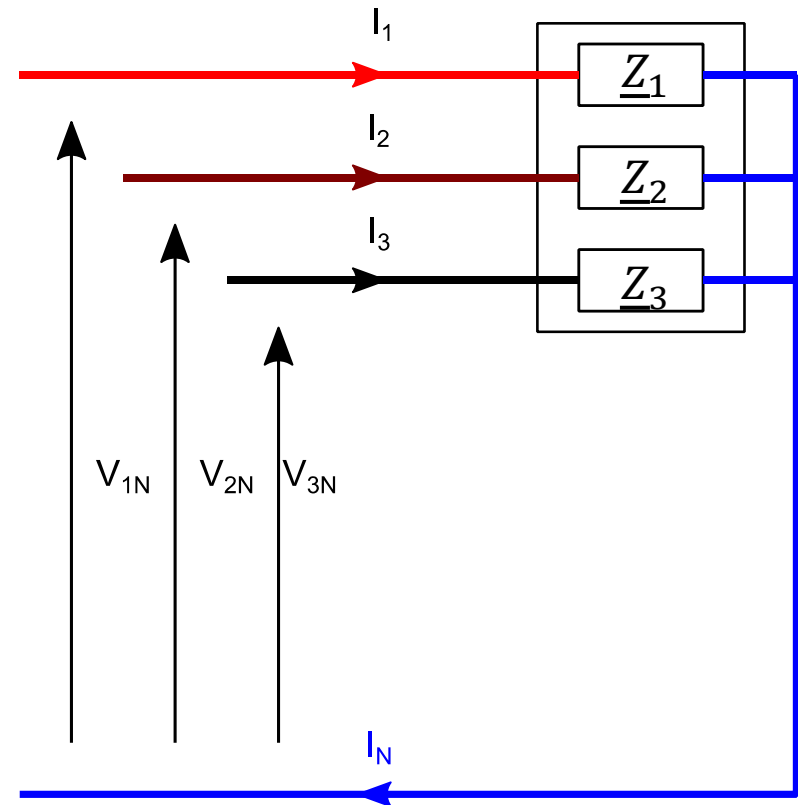

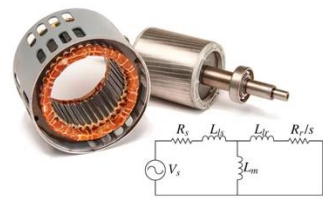

II – Power in sinusoidal regime

3-phase: powers

- Boucherot's theorem: *general* Delta-connection load

$$P = U_{12}J_2\cos(\varphi_1) + U_{23}J_3\cos(\varphi_2) + U_{31}J_1\cos(\varphi_3)$$

$$Q = U_{12}J_2\sin(\varphi_1) + U_{23}J_3\sin(\varphi_2) + U_{31}J_1\sin(\varphi_3)$$

- For the **balanced load**:


$$P = 3UJ\cos(\varphi) = \sqrt{3}UI\cos(\varphi)$$


$$Q = 3UJ\sin(\varphi) = \sqrt{3}UI\sin(\varphi)$$

$$S = 3UJ = \sqrt{3}UI$$

$$FP = \frac{P}{S}$$

$$S^2 = P^2 + Q^2$$

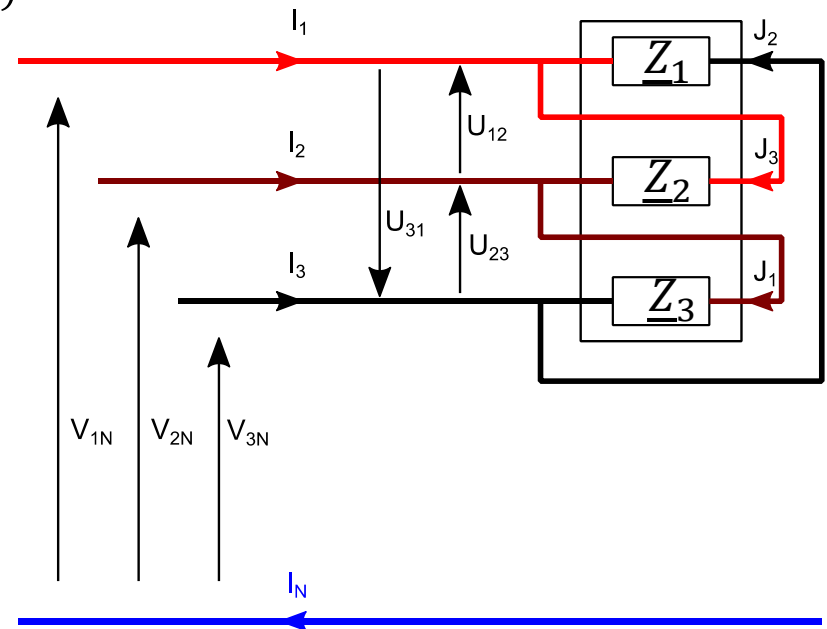

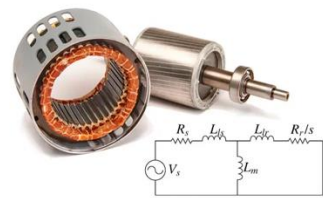


II – Power in sinusoidal regime


3-phase: power measurement

- Balanced 3-phase load

=> Wattmeter with virtual neutral

$$P = 3.V I \cos(\varphi)$$

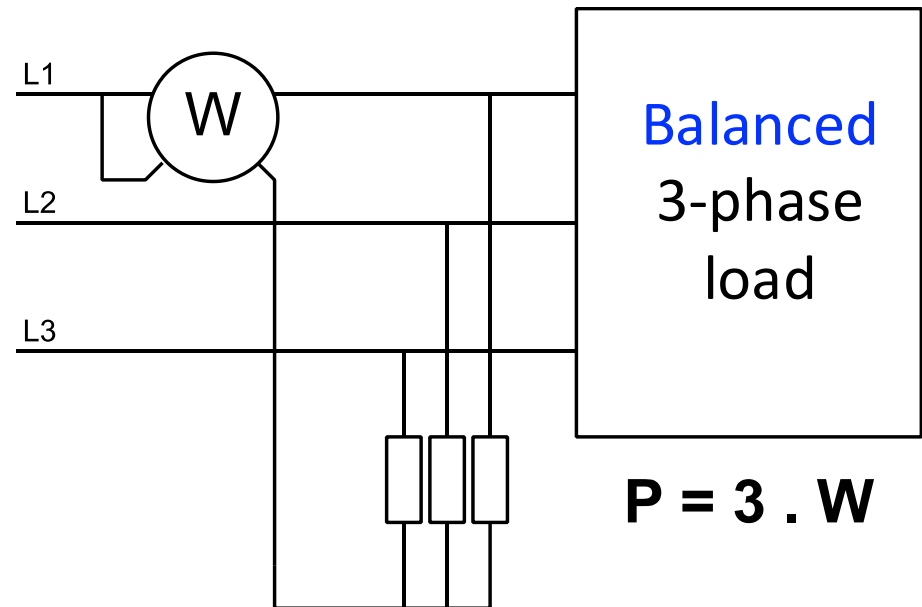

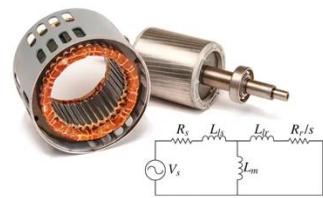

II – Power in sinusoidal regime

3-phase: power measurement

- The 2-wattmeter method:

$$W_1 + W_2 = \langle (v_1(t) - v_3(t))i_1(t) + (v_2(t) - v_3(t))i_2(t) \rangle$$

