

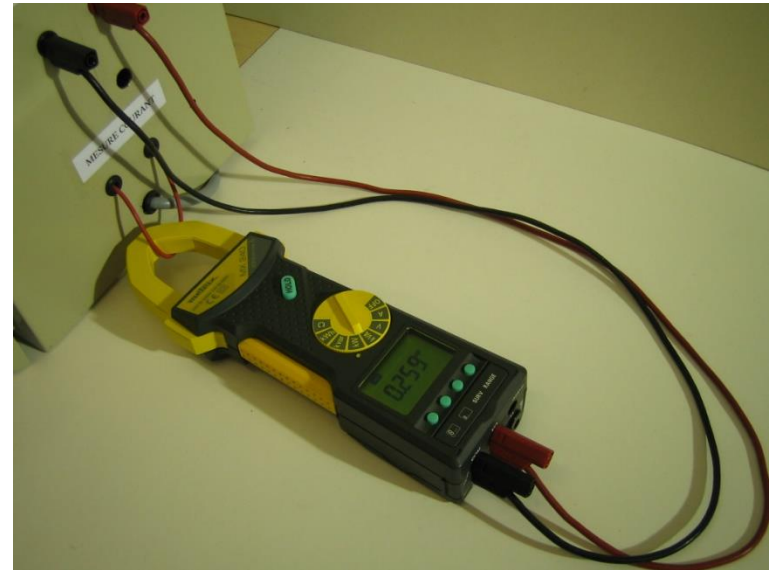


## II – Power in sinusoidal regime

### Single-phase

- Measurement of powers

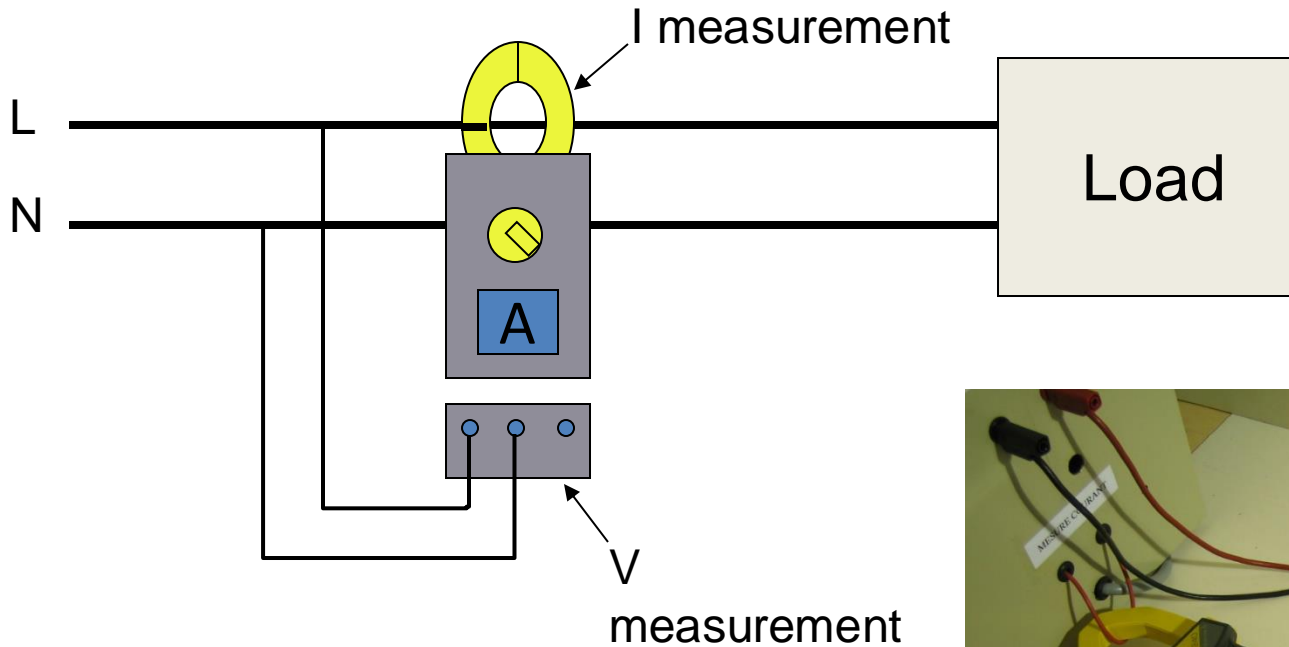


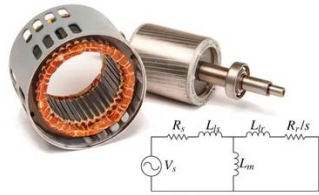


## II – Power in sinusoidal regime

### Single-phase

- Measurement of powers

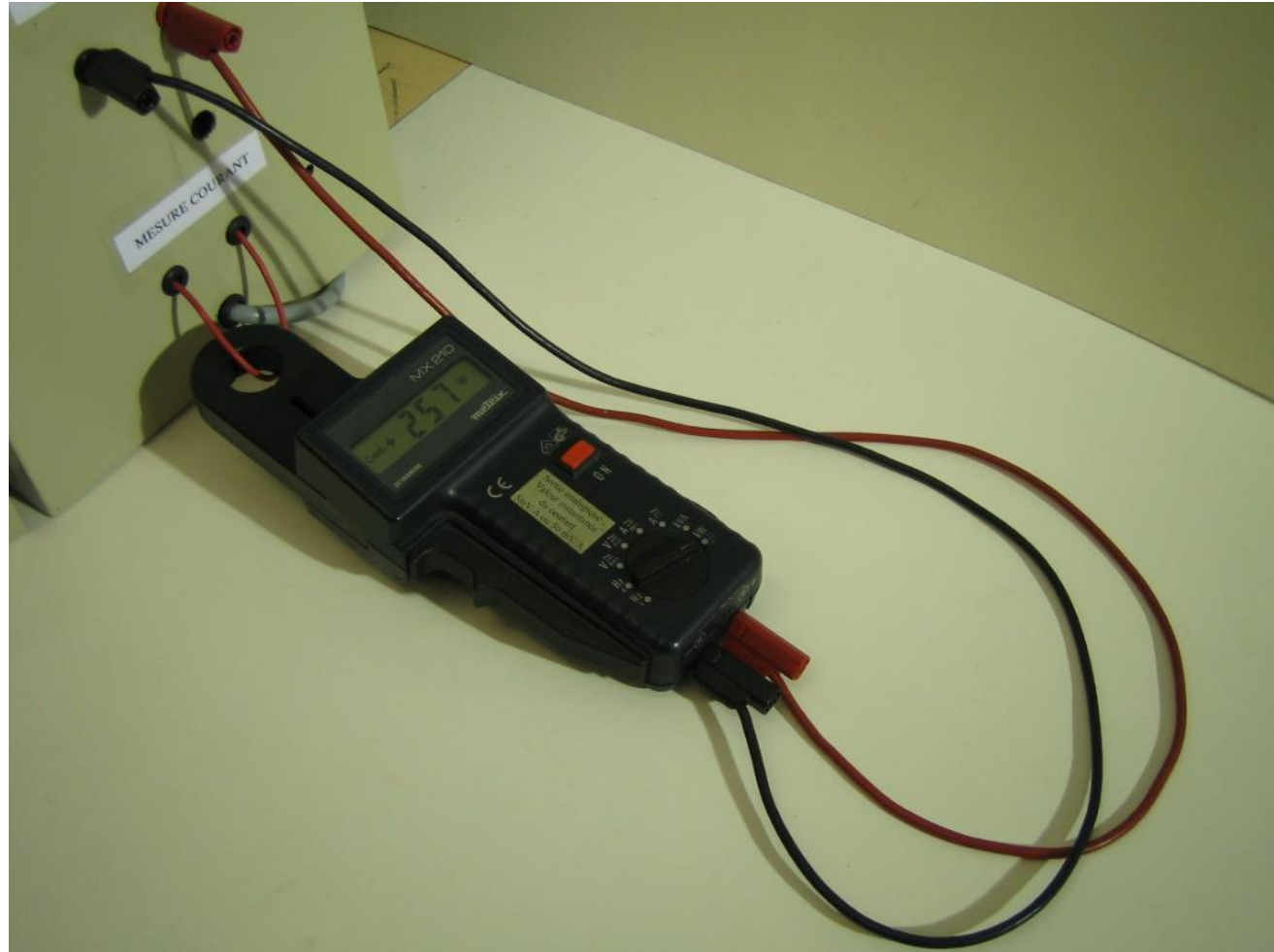


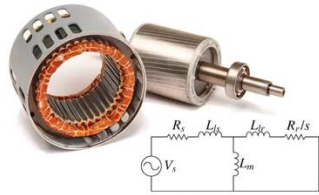

## II – Power in sinusoidal regime
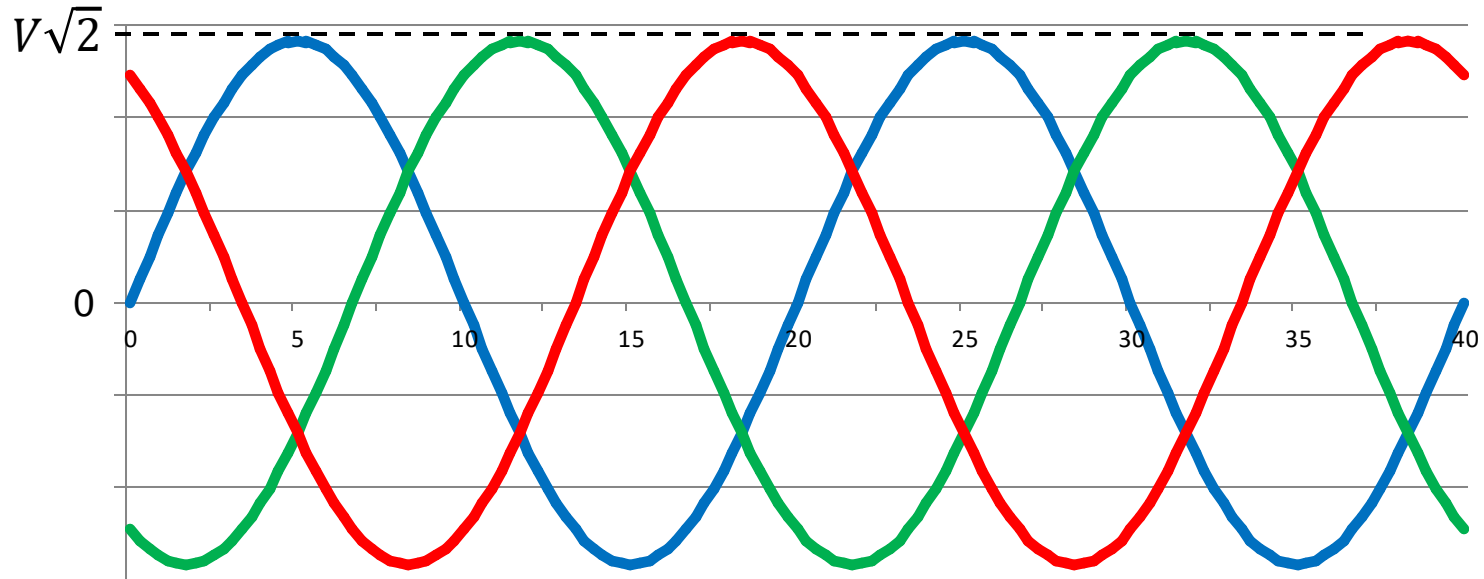
### 3-phase


- A direct balanced three-phase voltage system is a set of 3 sinusoidal voltages [phase-shifted by  \$2\pi/3\$](#)



$$v_1(t) = V\sqrt{2}\sin(\omega t)$$

$$v_2(t) = V\sqrt{2}\sin\left(\omega t - \frac{2\pi}{3}\right)$$

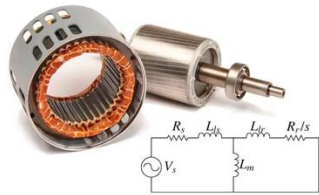
$$v_3(t) = V\sqrt{2}\sin\left(\omega t - \frac{4\pi}{3}\right) = V\sqrt{2}\sin\left(\omega t + \frac{2\pi}{3}\right)$$



## II – Power in sinusoidal regime

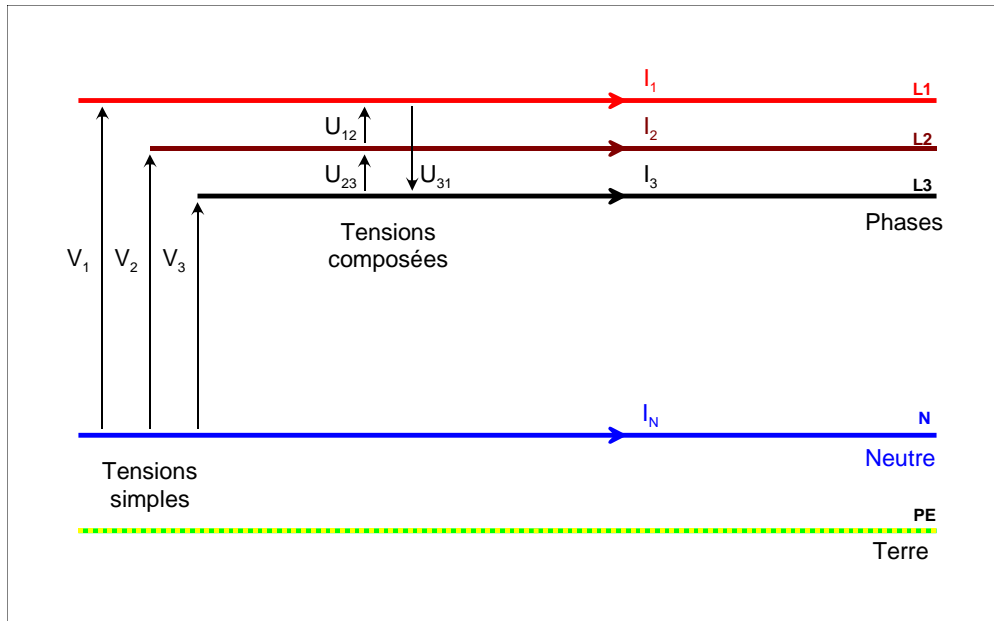
### 3-phase

- Distribution of 3-phase system: BT (low voltage) 230V / 400 V



- 4-wire (three phases and neutral)
- Voltages 230 / 400 volts: internationally harmonized
- $U = 400V / V = 230V / f = 50Hz$   
Transformer neutral grounded.


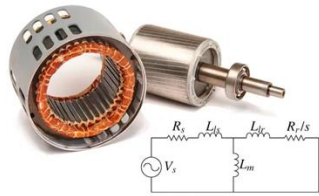
- $V$  is the **line voltage** = potential difference between a line and the neutral
- $U$  is the **phase voltage** = potential difference between two phases



## II – Power in sinusoidal regime
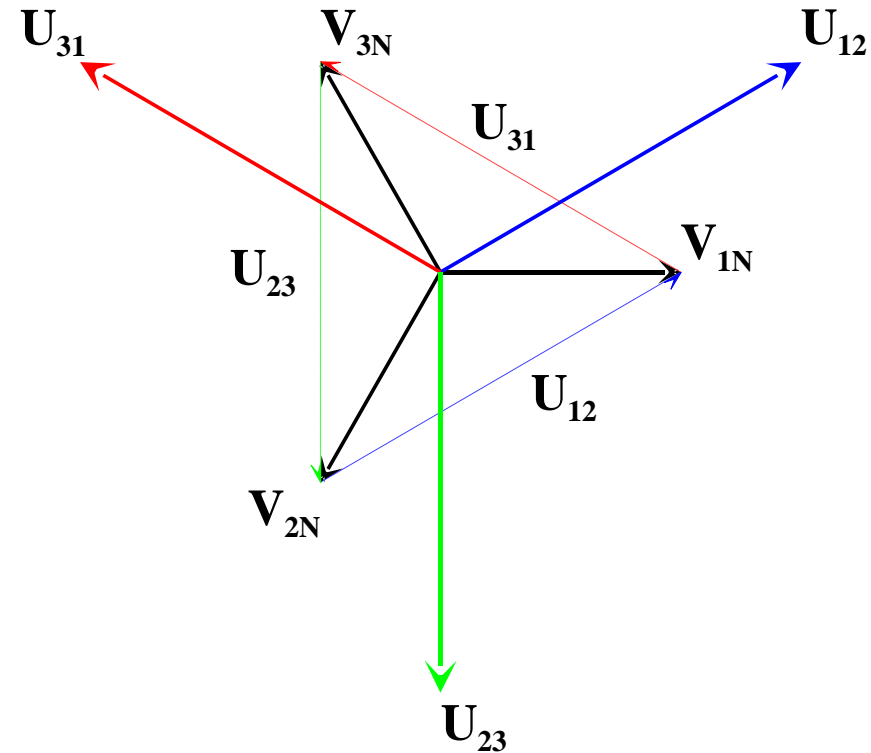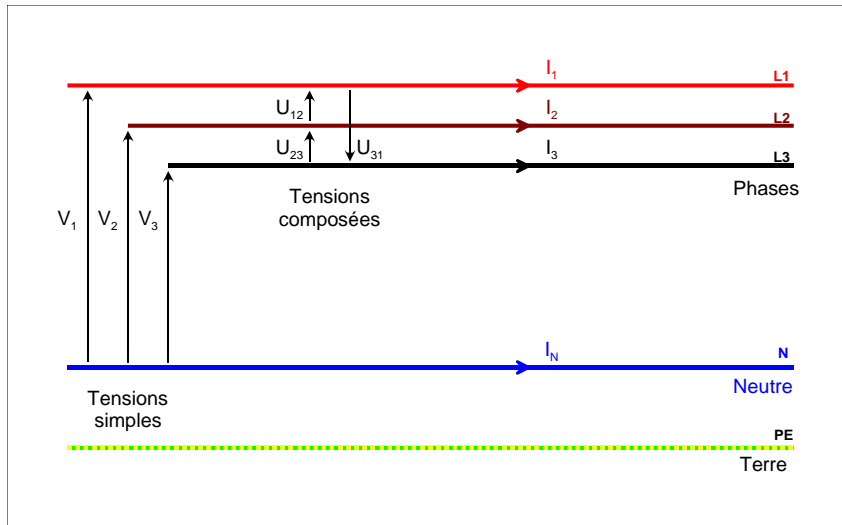
### 3-phase

- Distribution of 3-phase system: [direct balanced 3-phase system](#)




$$\vec{V}_1 + \vec{V}_2 + \vec{V}_3 = 0$$

$$\vec{U}_{12} = \vec{V}_1 - \vec{V}_2$$

$$\vec{U}_{23} = \vec{V}_2 - \vec{V}_3$$

$$\vec{U}_{31} = \vec{V}_3 - \vec{V}_1$$
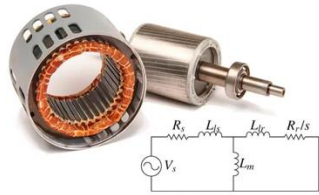
$$\vec{U}_{12} + \vec{U}_{23} + \vec{U}_{31} = 0$$



## II – Power in sinusoidal regime

### 3-phase

- Distribution of 3-phase system: [direct balanced 3-phase system](#)


- Relation between U and V

$$\vec{U}_{12} = \vec{V}_1 - \vec{V}_2$$


$$\vec{U}_{23} = \vec{V}_2 - \vec{V}_3$$

$$\vec{U}_{31} = \vec{V}_3 - \vec{V}_1$$

$$U = \sqrt{3}V$$


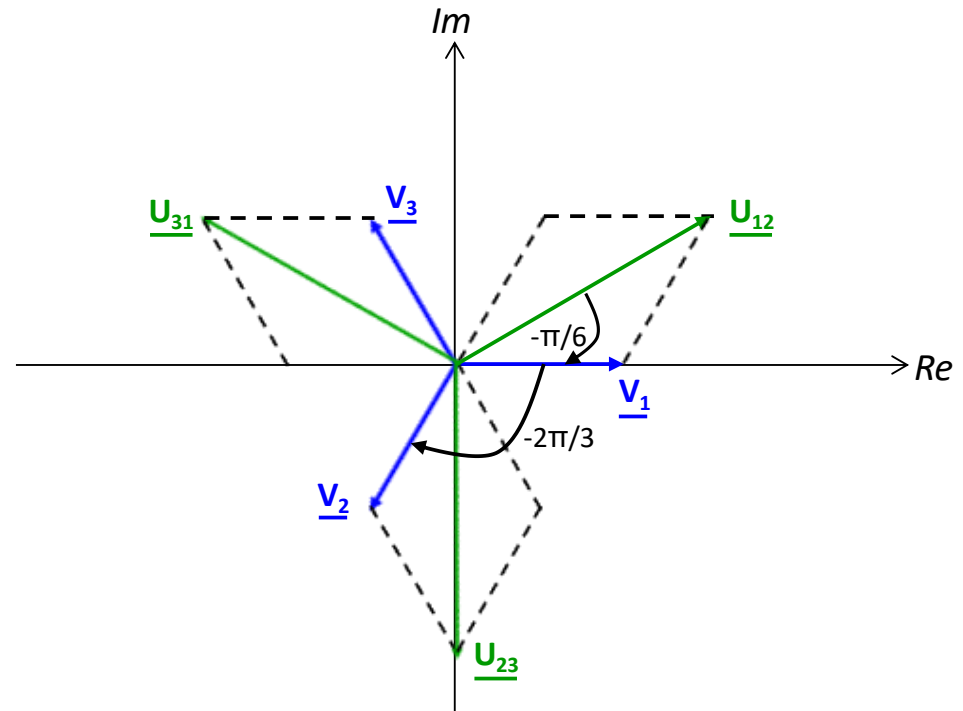


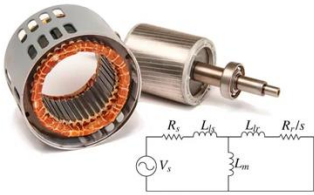- Balanced:  $V_1 = V_2 = V_3 = V$        $U_{12} = U_{23} = U_{31} = U$



## II – Power in sinusoidal regime

### 3-phase: summary

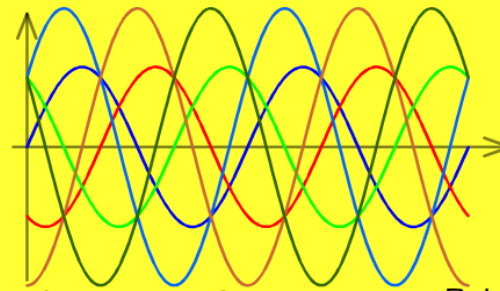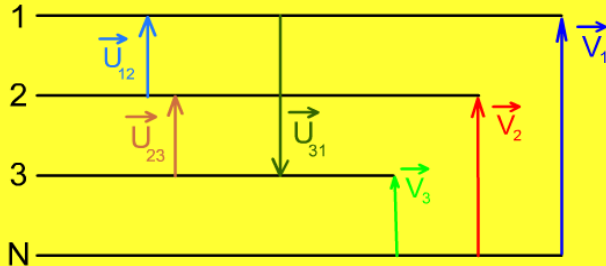

Tensions simples

$$v_1(t) = V_{MAX} \sin(\omega t)$$


$$v_2(t) = V_{MAX} \sin(\omega t - \frac{2\pi}{3})$$

$$v_3(t) = V_{MAX} \sin(\omega t - \frac{4\pi}{3})$$


avec

$$\omega = 2 \cdot \pi \cdot f$$

$$V_{MAX} = V \cdot \sqrt{2}$$

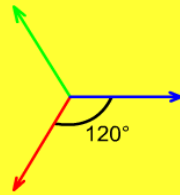
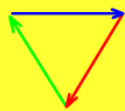
$$\vec{V}_1 + \vec{V}_2 + \vec{V}_3 = \vec{0}$$



Tensions composées

$$u_{12}(t) = U_{MAX} \sin(\omega t + \frac{\pi}{6})$$

$$u_{23}(t) = U_{MAX} \sin(\omega t - \frac{\pi}{2})$$

$$u_{31}(t) = U_{MAX} \sin(\omega t - \frac{7\pi}{6})$$


avec

$$\omega = 2 \cdot \pi \cdot f$$

$$U_{MAX} = U \cdot \sqrt{2}$$

$$U = V \sqrt{3}$$
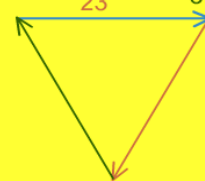
$$\vec{U}_{12} + \vec{U}_{23} + \vec{U}_{31} = \vec{0}$$





Relations entre tensions simples et composées

$$\vec{U}_{12} = \vec{V}_1 - \vec{V}_2$$

$$\vec{U}_{23} = \vec{V}_2 - \vec{V}_3$$

$$\vec{U}_{31} = \vec{V}_3 - \vec{V}_1$$

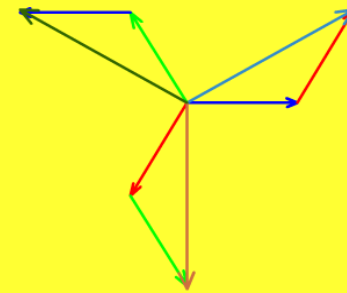

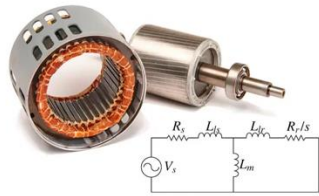


## II – Power in sinusoidal regime


### 3-phase: connections

- Both the 3-phase generator and the 3-phase load can be connected according to the following configurations:


**Y connection**

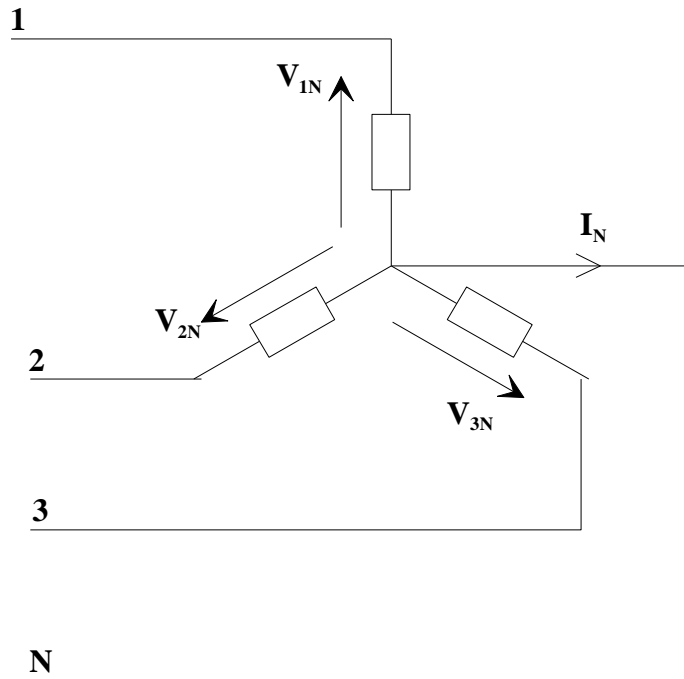

**Delta connection**

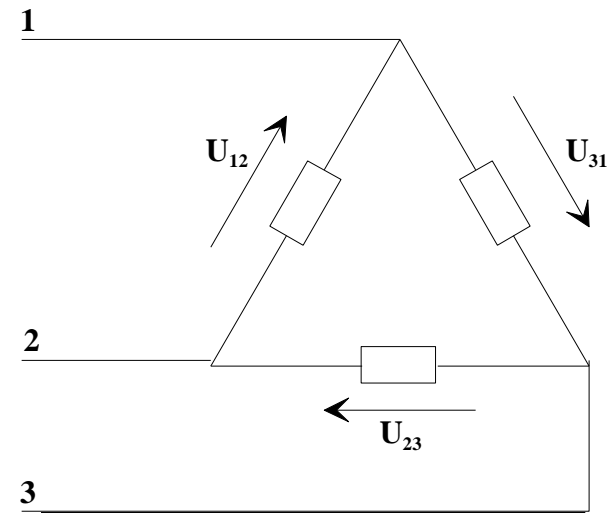



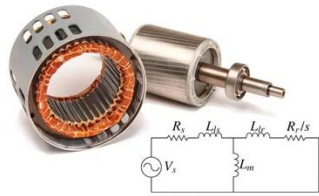


## II – Power in sinusoidal regime

### 3-phase: connections

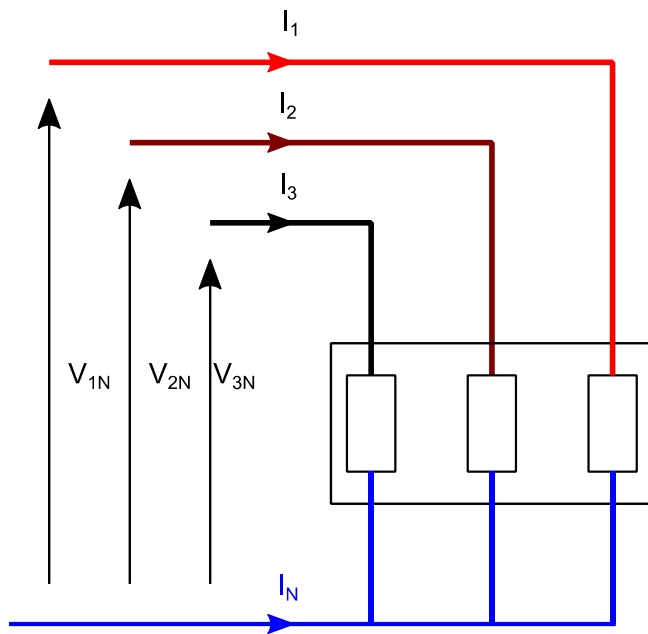
#### Y connection


- Each receptor is connected **between phase and neutral** and subjected to the line voltage


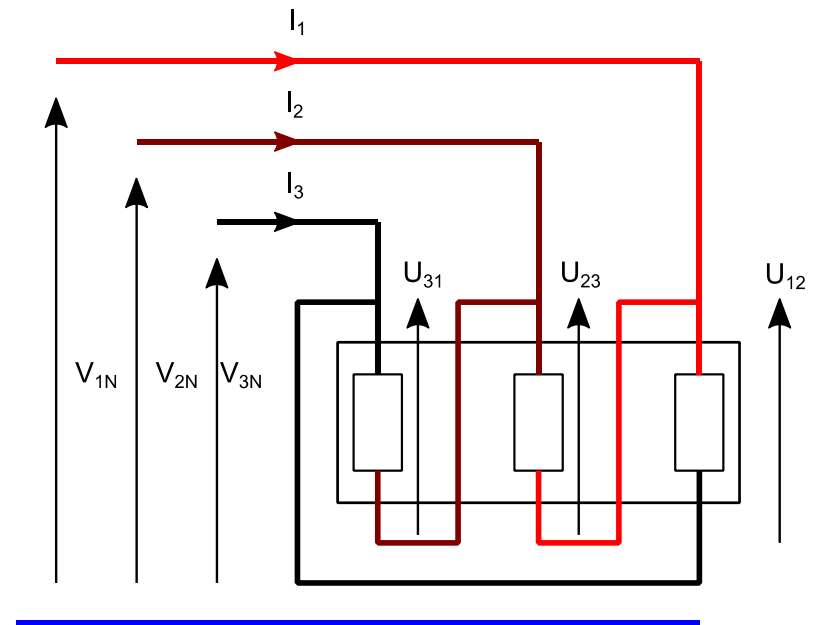
#### Delta connection


- Each receiver is connected **between two phases** and subjected to a phase voltage



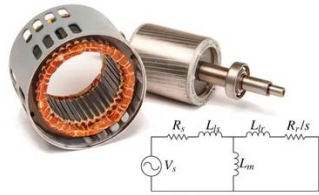


## II – Power in sinusoidal regime


### 3-phase: Y connection

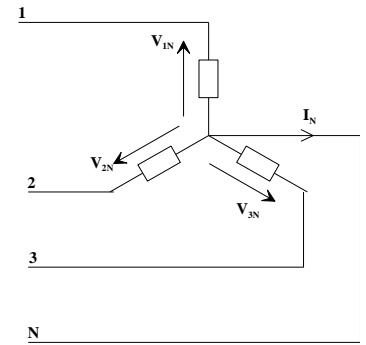

- Each receptor is connected between phase and neutral.
- Each receptor is subjected to the **line voltage** “V”.
- The line current “I” flows through each receptor.
- If all three loads are **identical**, we speak of a **balanced** load.  $I_1 = I_2 = I_3 = I$
- ⇒ No current flows in the neutral wire.
- ⇒  $I_N = 0$  A.
- ⇒ Its presence is therefore unnecessary.
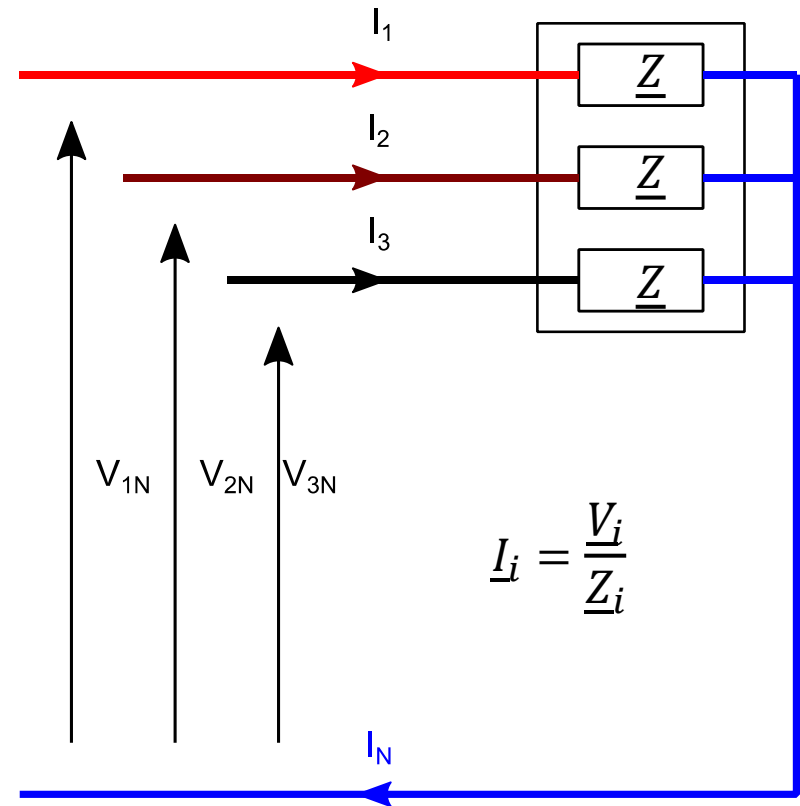
$$\vec{I}_1 + \vec{I}_2 + \vec{I}_3 = 0$$



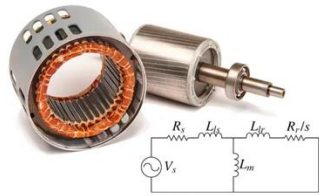

## II – Power in sinusoidal regime

### 3-phase: Delta connection



- Each receptor is connected between two phases.
- It is subjected to a **phase voltage** “U”.
- The phase current “J” flows through the receptor.
- Here, the neutral cannot be wired. Its presence is also not necessary.
- Kirchoff’s law:

$$\vec{I}_1 = \vec{J}_3 - \vec{J}_2$$


$$\vec{I}_2 = \vec{J}_1 - \vec{J}_3$$

$$\vec{J}_3 = \vec{J}_2 - \vec{V}_1$$

$$I = J\sqrt{3}$$

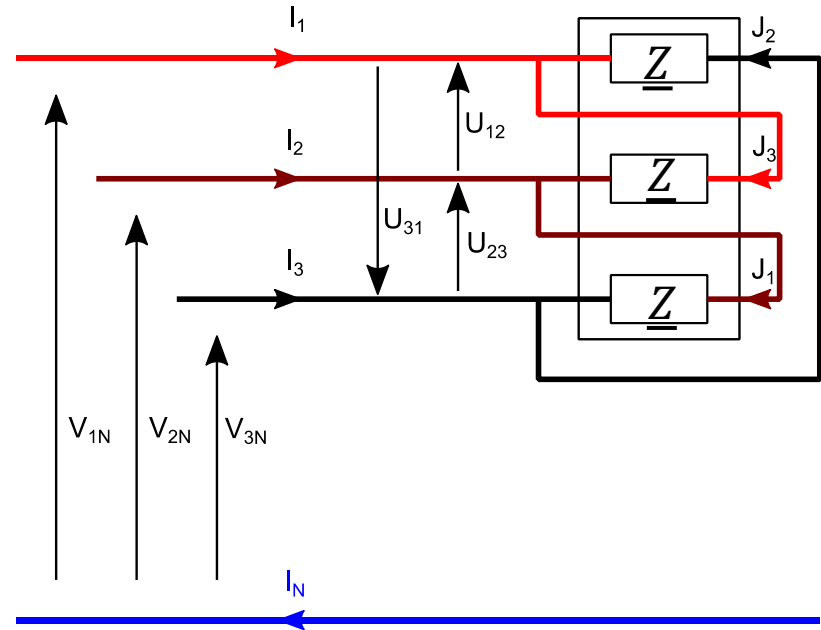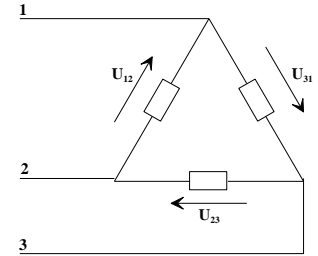


- Balanced load:  $J_1 = J_2 = J_3 = J$

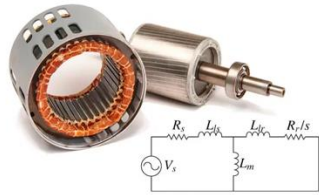

## II – Power in sinusoidal regime

### 3-phase: powers


- Boucherot's theorem:

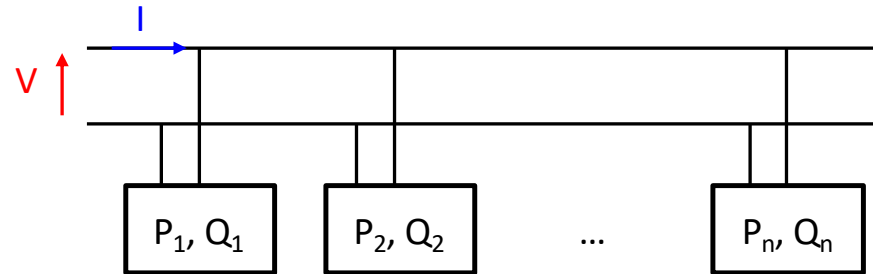

The active power of a system is the sum of the active powers of each element, as are reactive power and complex apparent power. Note that this is not true for real apparent power.

- Active power:  $P_{tot} = P_1 + P_2 + \dots + P_n$
- Reactive power:  $Q_{tot} = Q_1 + Q_2 + \dots + Q_n$
- Complex apparent power:  $\underline{S}_{tot} = \underline{S}_1 + \underline{S}_2 + \dots + \underline{S}_n$
- But:  $S_{tot} \neq S_1 + S_2 + \dots + S_n$
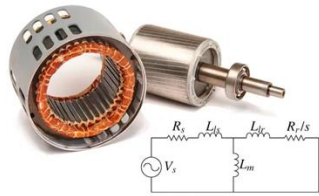
$$S = V \cdot I = \sqrt{P_{tot}^2 + Q_{tot}^2}$$



## II – Power in sinusoidal regime

### 3-phase: powers

- Boucherot's theorem: *general* Y-connection load

$$P = V_1 I_1 \cos(\varphi_1) + V_2 I_2 \cos(\varphi_2) + V_3 I_3 \cos(\varphi_3)$$

$$Q = V_1 I_1 \sin(\varphi_1) + V_2 I_2 \sin(\varphi_2) + V_3 I_3 \sin(\varphi_3)$$

- For the **balanced load**:


$$P = 3VI \cos(\varphi) = \sqrt{3}UI \cos(\varphi)$$


$$Q = 3VI \sin(\varphi) = \sqrt{3}UI \sin(\varphi)$$

$$S = 3VI = \sqrt{3}UI$$

$$FP = \frac{P}{S}$$

$$S^2 = P^2 + Q^2$$

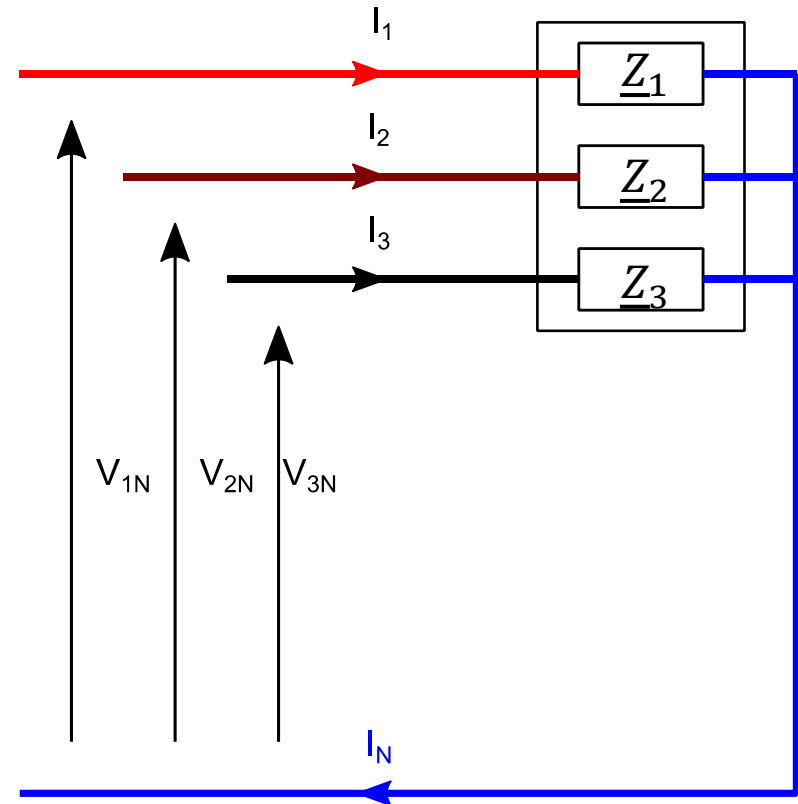

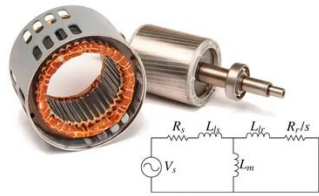

## II – Power in sinusoidal regime

### 3-phase: powers

- Boucherot's theorem: *general* Delta-connection load

$$P = U_{12}J_2 \cos(\varphi_1) + U_{23}J_3 \cos(\varphi_2) + U_{31}J_1 \cos(\varphi_3)$$

$$Q = U_{12}J_2 \sin(\varphi_1) + U_{23}J_3 \sin(\varphi_2) + U_{31}J_1 \sin(\varphi_3)$$

- For the **balanced load**:


$$P = 3UJ \cos(\varphi) = \sqrt{3}UI \cos(\varphi)$$


$$Q = 3UJ \sin(\varphi) = \sqrt{3}UI \sin(\varphi)$$

$$S = 3UJ = \sqrt{3}UI$$

$$FP = \frac{P}{S}$$

$$S^2 = P^2 + Q^2$$

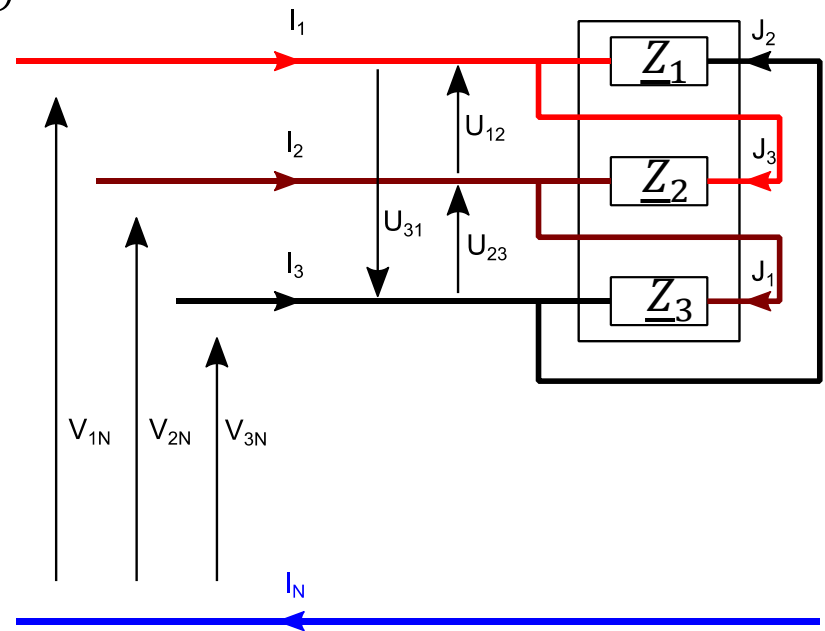

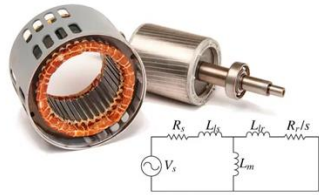


## II – Power in sinusoidal regime


### 3-phase: power measurement

- Balanced 3-phase load

=> Wattmeter with virtual neutral

$$P = 3 \cdot V I \cos(\varphi)$$

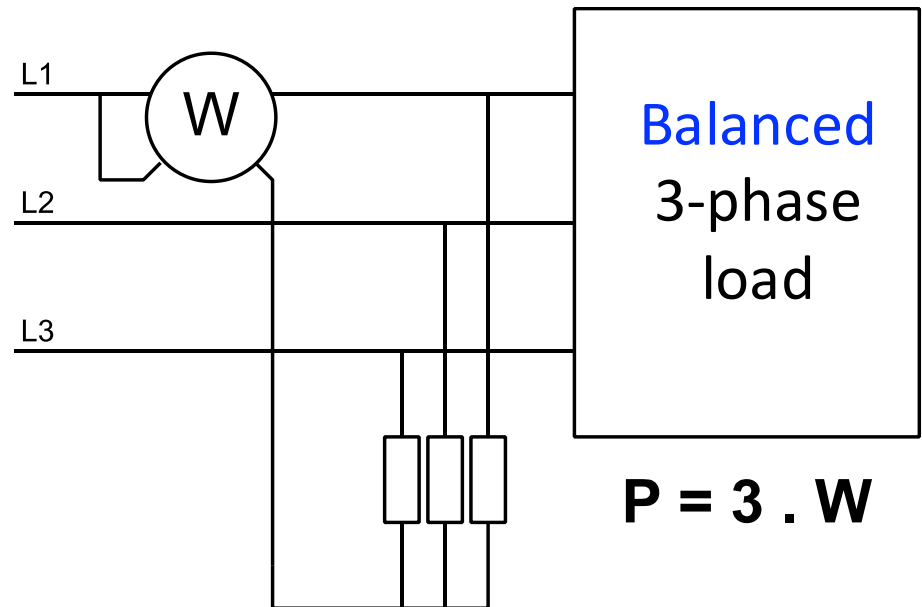

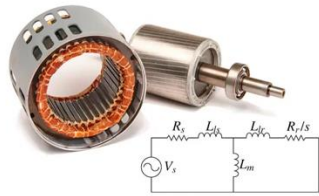

## II – Power in sinusoidal regime

### 3-phase: power measurement

- The 2-wattmeter method:

$$W_1 + W_2 = \langle (v_1(t) - v_3(t))i_1(t) + (v_2(t) - v_3(t))i_2(t) \rangle$$

