

Electrical Engineering




Thomas TILLOCHER

Université d'Orléans
Laboratoire GREMI

thomas.tillocher@univ-orleans.fr

Year 2023/2024

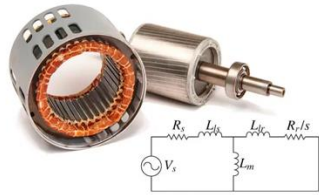

Introduction


Schedule

	M1 AEMS
Lectures	14 x 1,25 h dont 2 DS
Tutorials	8 x 1,25 h
Lab work	1 x 2,50 h + 6 x 3,75 h

Outline

Introduction

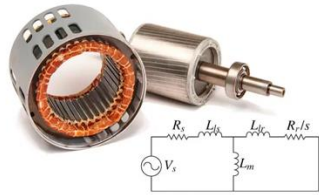- I) Reminders (electricity)
- II) Power in sinusoidal regime (single-phase and 3-phase)
- III) Transformers
- IV) Electric motors



III - Transformers


Reminders: electromagnetism

- The electrical field: an electrical charge, q_A , placed at any point A in space, acts at any other point M in space, in the form of a vector field called the “electric field $E_A(M)$ ” expressed in $V.m^{-1}$

- **Electrical field due to charge q_A at point M**

$$\vec{E}_A(M) = \frac{q_A}{4 \cdot \pi \cdot \epsilon_0 \cdot AM^2} \cdot \vec{u}$$

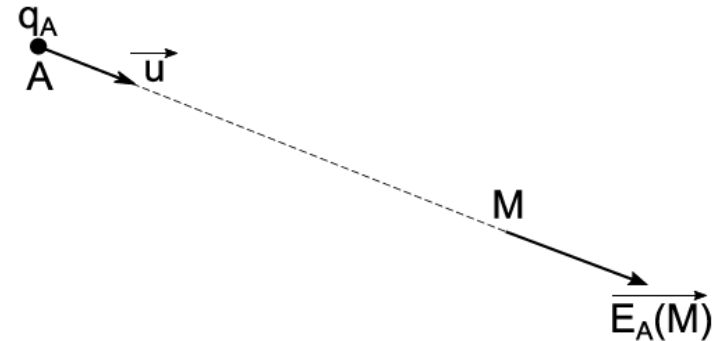
$E_A(M)$ in $V.m^{-1}$, q_A in C, AM in m
 ϵ_0 , vacuum permittivity: $\epsilon_0 = 10^{-9} / 36\pi \text{ F.m}^{-1}$



- Properties of the electrical field:

=> Inversely proportional to the square of the distance from its source. It scales with “ $1/r^2$ ”

=> Additive quantity

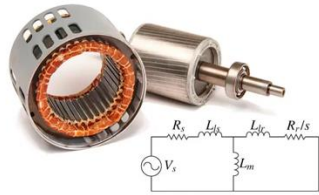

III - Transformers

Reminders: electromagnetism


- The magnetic field: An electrical charge, q_A , located at any point A in space and moving with velocity “V”, acts at any other point M in space, in the form of a vector field called the “magnetic field $B_A(M)$ ” expressed in Tesla (T).

- **Magnetic field in vacuum at point M due to charge displacement q_A**

$$\vec{B}_A(M) = \frac{\mu_0}{4 \cdot \pi} \cdot \frac{q_A \cdot \vec{V} \wedge \vec{u}}{AM^2}$$

$B_A(M)$ in Tesla, q_A in C, V in m/s, AM in m

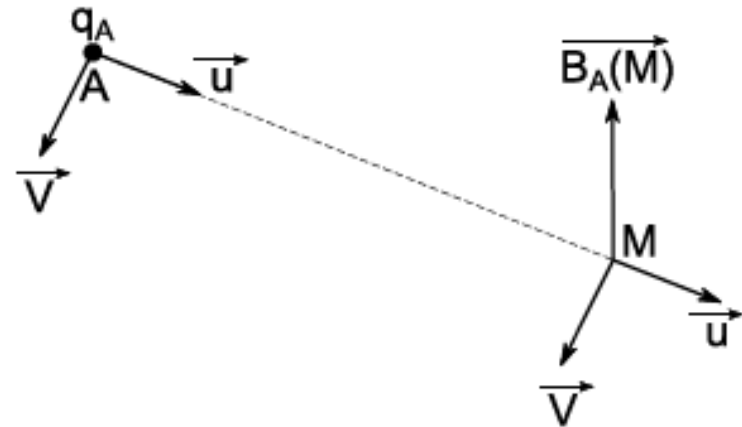
μ_0 , vacuum permeability in m.T.A.m⁻¹, $\mu_0 = 4 \cdot \pi \cdot 10^{-7}$ m.T.A.m⁻¹ (or H.m⁻¹)



- Properties of the magnetic field:

=> Inversely proportional to the square of the distance from its source. It varies in “1/r²”.

=> Additive quantity

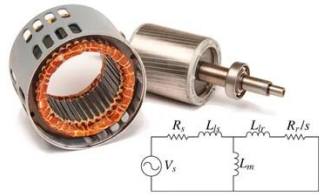

III - Transformers


Reminders: electromagnetism

- [The Biot and Savart's law](#): The elementary part $d\vec{l}$ of an electrical circuit in P through which a current of intensity I flows creates the “magnetic field $d\vec{B}_P(M)$ ” at a point M in space


- Magnetic field at point M due to the current I flowing through the elementary part $d\vec{l}$

$$\overrightarrow{dB_P(M)} = \frac{\mu_0}{4 \cdot \pi} \cdot \frac{I \cdot \overrightarrow{dl} \wedge \overrightarrow{PM}}{PM^3}$$
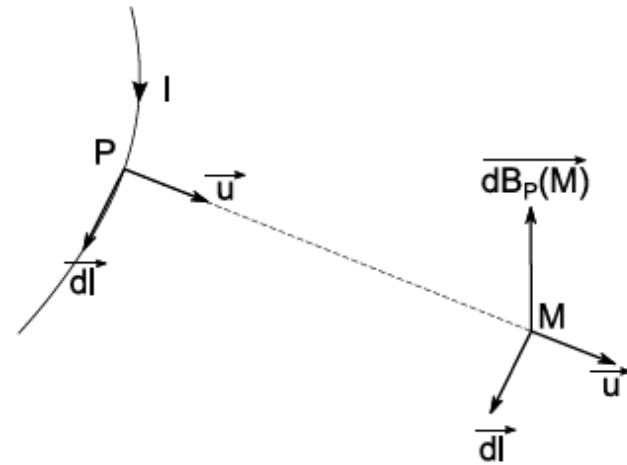
$$\overrightarrow{dB_P(M)} = \frac{\mu_0}{4 \cdot \pi} \cdot \frac{I \cdot \overrightarrow{dl} \wedge \vec{u}}{r^2}$$



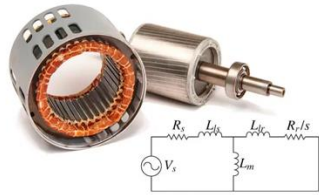- Total magnetic field in M created by the electrical circuit : $\overrightarrow{B(M)} = \frac{\mu_0}{4 \cdot \pi} \cdot \int_{P \in \text{circuit}} \frac{I \cdot \overrightarrow{dl} \wedge \vec{u}}{r^2}$



III - Transformers

Reminders: electromagnetism

- The excitation magnetic field \vec{H} : dHP(M), is related to the state of magnetic excitation of the medium and is given in $A.m^{-1}$.

- Magnetic excitation field at point M due to the current I flowing through portion dl:


$$\vec{dH}_P(M) = \frac{1}{4 \cdot \pi} \cdot \frac{I \cdot d\vec{l} \wedge \vec{u}}{r^2}$$

- Total magnetic excitation field at M created by the wire through which a current I flows:

$$\vec{H}(M) = \frac{1}{4 \cdot \pi} \cdot \int_{P \in \text{fil}} \frac{I \cdot d\vec{l} \wedge \vec{u}}{r^2}$$

- If \vec{H} is the excitation magnetic field, \vec{B} is the magnetic induction field: $\vec{B} = \mu_0 \mu_r \vec{H}$

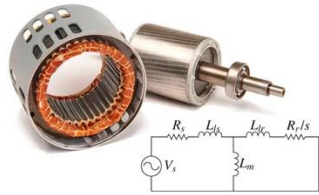μ_0 vacuum permeability, μ_r the relative permeability



III - Transformers


Reminders: electromagnetism

- The **magnetic flux**: The flux of induction magnetic field B across a closed surface (S) is the quantity ϕ_B given in **Weber (Wb)**


$$\Phi_B = \oiint_{(S)} \vec{B} \cdot \vec{n}_{ext} \cdot dS$$

- The magnetic flux F is usually given by the product $B.S$
- If magnetic leakage is neglected, the flux in a magnetic circuit is conservative

$$\Phi = B.S$$

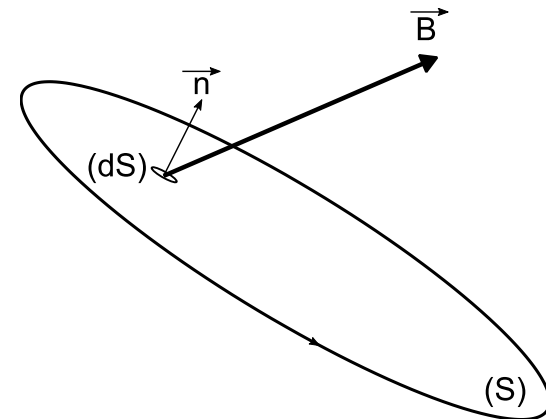

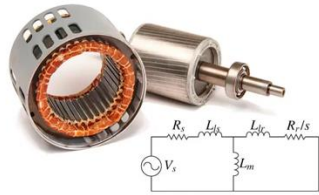
Analogy with the garden hose :
 magnetic flux $F \rightarrow$ flow
 magnetic field $B \rightarrow$ water speed
 solenoid cross-section $S \rightarrow$ pipe cross-section



III - Transformers

Reminders: electromagnetism

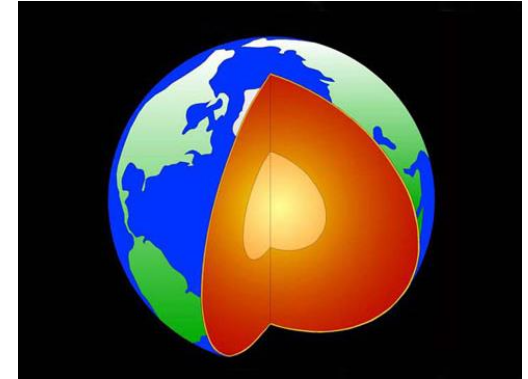
- Orders of magnitude
- Earth induction magnetic field: $50 \cdot 10^{-6}$ T



In electrical machines:

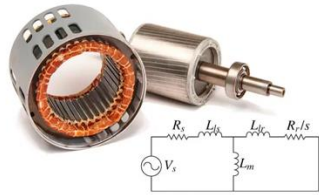- Induction magnetic field: 1 T à 1,5 T
- Excitation magnetic field : 1000 à 100000 A.m⁻¹
- Magnetic flux: 10^{-5} à 10^{-3} Wb






III - Transformers

Reminders: electromagnetism

- [Ampere's theorem](#): If (C) is a closed contour of space surrounding N wire conductors through which currents of intensities I_k flow, then the circulation of the magnetic excitation vector H along a closed contour Γ is equal to the sum of the entwined currents

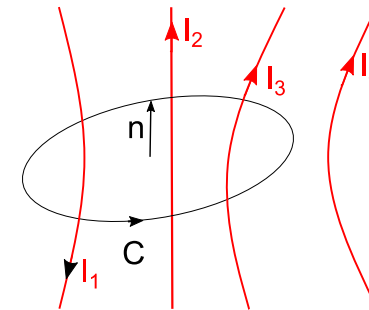
$$\oint_{(C)} \vec{H} \cdot d\vec{\ell} = \sum_{k=1}^{k=N} i_k \quad \mathbf{H \cdot \ell = N \cdot I}$$



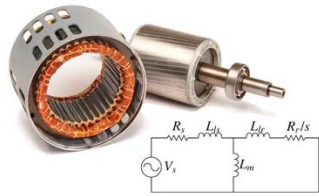- Example:

$$\oint_{(C)} \vec{H} \cdot d\vec{\ell} = -i_1 + i_2 + i_3$$

- i_1 is counted as negative,
- i_2 and i_3 are counted as positive
- i_4 is outside the contour (not taken into account)




III - Transformers

Reminders: electromagnetism



- Example: magnetic field created by a solenoid
 - A solenoid is a straight winding with length l greater than its radius r .
 - Inside the solenoid, far from its ends, the magnetic field is uniform.
 - The field lines are parallel
 - They enter at the coil's SOUTH face and exit at its NORTH face (corkscrew rule).
- N : number of turns, l : length of solenoid


$$\vec{B} = \mu \times \vec{H}$$

$$\mu = \mu_0 \times \mu_R$$

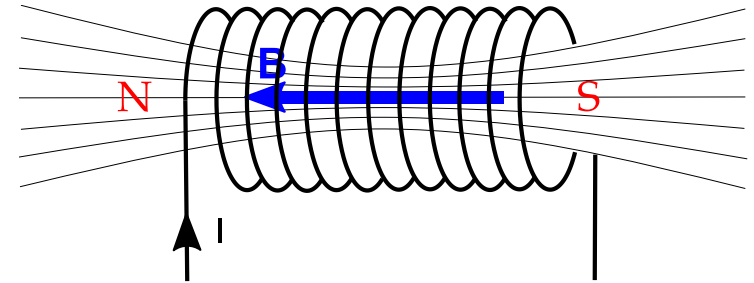
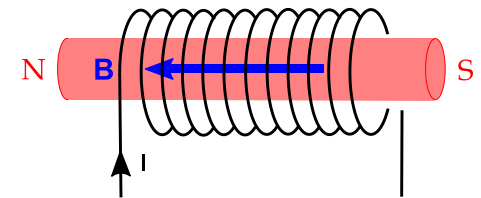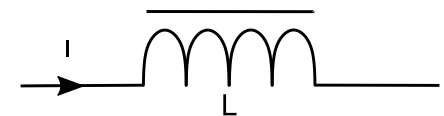
$$H = \frac{N \cdot I}{l} \qquad B = \mu_0 \cdot \frac{NI}{l}$$



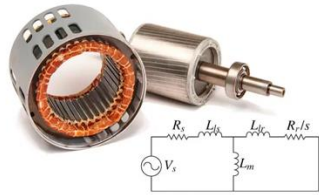

III - Transformers

Reminders: magnetic materials

- Materials are classified according to their **magnetic susceptibility** χ

=> χ is related to the relative permeability through: $\mu_r = 1 + \chi$

- **Para-magnetic** materials: $\chi > 0$, between 10^{-3} and 10^{-7}


=> These materials are rare and their magnetization is negligible (Al, W, Pt, Sn...)

- **dia-magnetic** materials: $\chi < 0$, between 10^{-4} and 10^{-6}

=> These materials are common and their magnetization is negligible (non magnetic materials such as Cu, Bi, Au, Ag...)

- **Ferro-magnetic** materials: $\chi > 0$, between 10^3 and 10^6

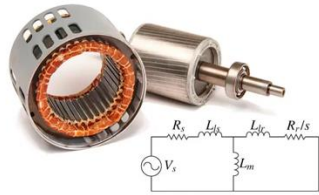=> These are magnetic material of interest for magnetic circuits or transformer core (Fe, Ni, Co)



III - Transformers

Reminders: magnetic materials

- Magnetic materials are characterized by their **hysteresis loop**
 - => $B=f(H)$ curve showing magnetizing/demagnetizing of the ferromagnetic material

- A ferromagnetic material that has never been magnetized will magnetize starting from O ("first magnetizing curve")

- The loop is run only in the direction of the arrows


- B_S : **saturation** induction magnetic field


- B_R : **point of retentivity**

=> Remanence of residual magnetism in the material

- H_C : **point of coercivity**

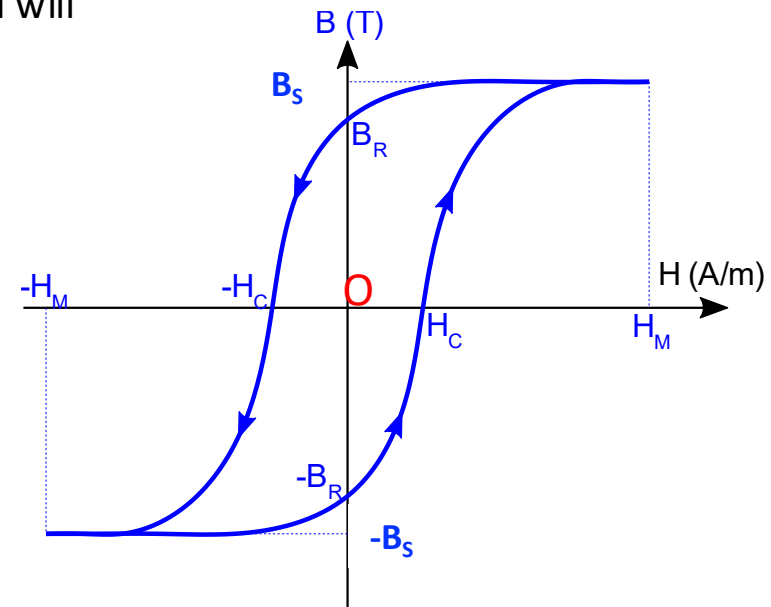=> Coercive excitation magnetic field required to remove the residual magnetism in the material



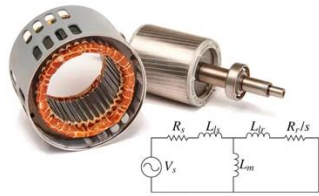


III - Transformers

Reminders: magnetic materials


- The shape of the hysteresis loop varies according to the magnetic material

Soft magnetic material

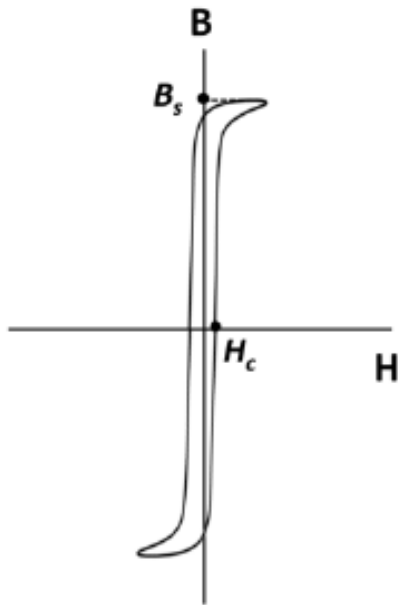


$B_s = 1.5 - 2\text{T}$
 $B_R < 1\text{T}$
 $H_c = 1-10\text{ A/m}$


Hard magnetic material

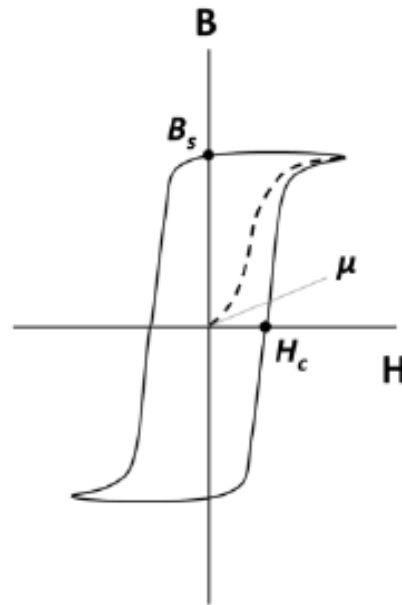

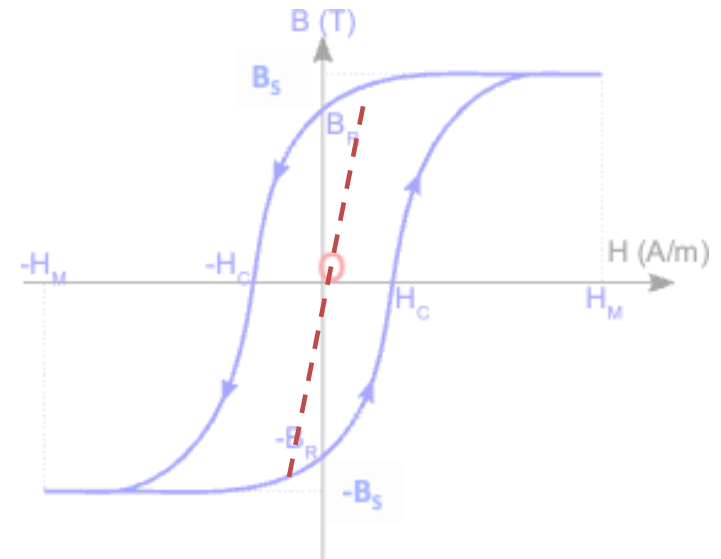$B_R - 1\text{T}$
 $H_c = 10^3\text{ A/m}$



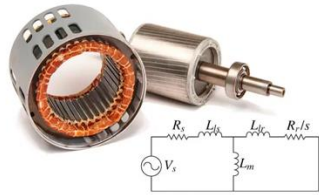
Linear approximation outside the saturation region: $B = \mu H$



III - Transformers

Magnetic circuits

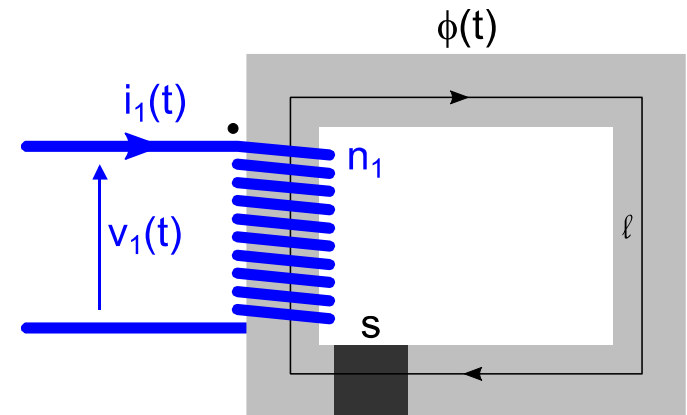
- Linear homogeneous magnetic circuits:
- Materials and geometry are chosen to concentrate flux density as much as possible, thus creating the strongest possible induction => limitation of both mass and size/volume
- **Homogeneous** = a single magnetic material
- Homogeneous = constant cross section
- **Linear** = outside the saturation regime
- ℓ (schematic) = mean field line



$$\oint \vec{H} \cdot d\vec{\ell} = n \cdot I$$

$$H \cdot \ell = n \cdot I$$

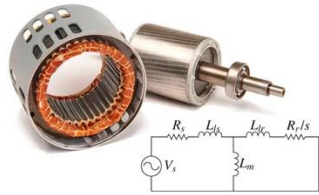- The nI quantity is also called magnetomotive force



III - Transformers

Magnetic circuits

- Hopkinson's relation:

- In a linear homogeneous magnetic circuit, the material exhibits a constant permeability

$$\mu = \mu_0 \mu_r$$


- Therefore: $\mathbf{B} = \mu \mathbf{H}$

- We have shown previously that $\mathbf{\Phi} = \mathbf{B} \cdot \mathbf{S}$

- By considering the Ampere's theorem as well, it can be shown that:

$$\mathbf{NI} = \mathfrak{R} \mathbf{\Phi} \quad \text{Hopkinson's relation, with the reluctance} \quad \mathfrak{R} = \frac{\ell}{\mu S} \quad (\text{in H}^{-1})$$

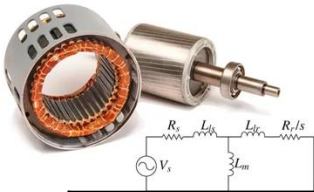
- The reluctance is the opposition that a ferromagnetic material produces to the establishment of a magnetic field



III - Transformers

Magnetic circuits: analogy with electrical circuits

Electrical circuit	Magnetic circuit
Electromotive force in V : V	Magnetomotive force in A.tr : $\varepsilon = n \cdot I$
Electrical current in A : I	Magnetic flux in Wb : Φ
Electrical resistance in Ω : R $R = \rho \times \frac{\ell}{S}$ <ul style="list-style-type: none"> • Electrical resistivity in $\Omega \cdot m$: ρ • Conductor length in m : ℓ • Conductor cross section in m^2 : s 	Magnetic reluctance: \mathcal{R} $\mathcal{R} = \frac{1}{\mu_0 \times \mu_R} \times \frac{\ell}{S}$ <ul style="list-style-type: none"> • Magnetic permeability in H/m : μ • Circuit length in m : ℓ • Circuit cross section in m^2 : s
Ohm's law: $V = R \cdot I$	Hopkinson's law: $n \cdot I = \mathcal{R} \cdot \Phi$
Electrical field in V/m : E	Excitation magnetic field in A/m : H
Current density in $A \cdot m^{-2}$: $J = \frac{I}{s} = \sigma \cdot E$	Induction magnetic field in T : $B = \frac{\Phi}{s} = \mu \cdot H$

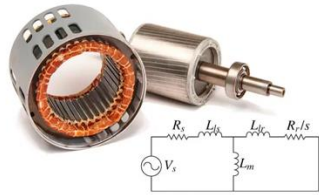


III - Transformers

Magnetic circuits


- Lenz's law and Faraday's law:
- **Lenz's law (qualitative law):** Induced currents and fields oppose the causes that gave rise to them
=> The induced field and current oppose the change in flux through the circuit
- **Faraday's law (quantitative law):** Any flux variation produces an induced electromotive force across a circuit
=> For a coil, an electromotive force is produced at across each turn of the winding

$$e(t) = - \frac{d\phi(t)}{dt} \quad (\text{receptor convention})$$
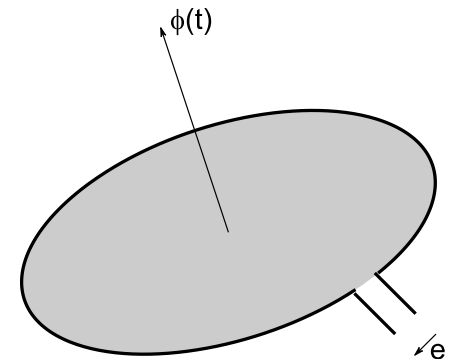
$$\text{For } n \text{ turns: } e(t) = -n \times \frac{d\phi(t)}{dt}$$



III - Transformers


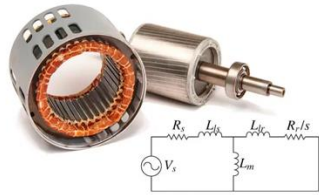



Magnetic circuits

- The iron-core coil:

- A **winding of copper** wire **wrapped** on a magnetic circuit of **ferromagnetic material** forms an iron-core coil

=> transformers, electromagnets, motors

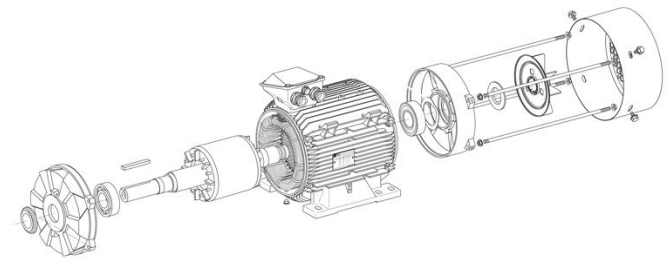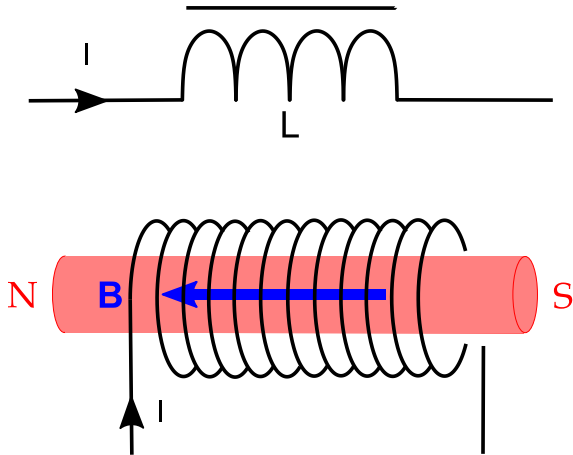

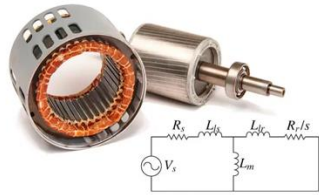

III - Transformers

Magnetic circuits


- The iron-core coil:

- Consider an iron-core coil with N turns

=> Each turn is crossed by the flux ϕ created in the material => Total flux $\phi_T = N\phi$

- By considering both Hopkinson's relation and Faraday's law:

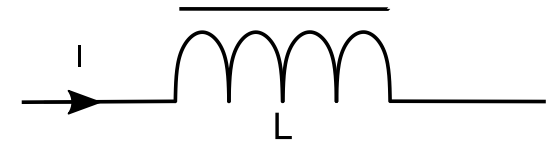
$$Ni = \mathfrak{R}\Phi \quad e(t) = -\frac{d\phi_T(t)}{dt} = -N\frac{d\phi(t)}{dt}$$




- We introduce the inductance L such that: $\phi_T = Li$

- With L (in H): $L = \frac{N^2}{\mathfrak{R}} = \frac{N^2\mu S}{\ell}$

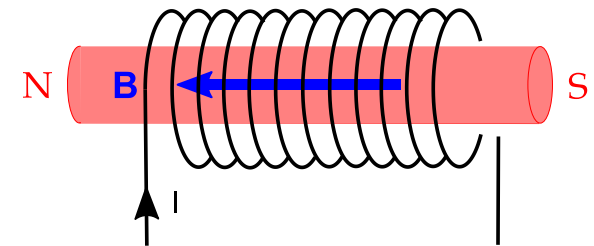- We retrieve the expression: $e(t) = -L\frac{di(t)}{dt}$



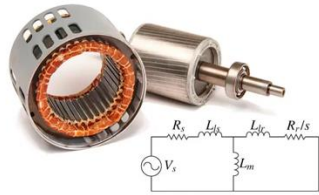


III - Transformers

Magnetic circuits

- Mutual inductance: (case of the homogeneous linear magnetic circuit)
- **Mutual inductance** occurs when the magnetic circuit has **at least two windings**
- => Each current has an influence on the flux flowing in the circuit.

- Flux created by coil 1 (current i_1) and flowing through coil 2
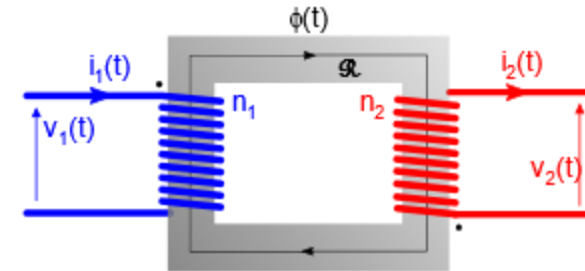
$$\phi_{1 \rightarrow 2} = \frac{N_1 i_1}{\mathcal{R}} \quad \longrightarrow \quad \phi_{T2} = N_2 \phi_{1 \rightarrow 2}$$




- By analogy with the definition of the inductance: $\phi_{T2} = N_2 \phi_{1 \rightarrow 2} = M_{12} i_1$

- With M (in H): $M_{12} = \frac{N_1 N_2}{\mathcal{R}} \quad \longrightarrow \quad e_2(t) = -M_{12} \frac{di_1(t)}{dt}$

- Voltage across winding k among n other windings: mutual inductances + self-inductance
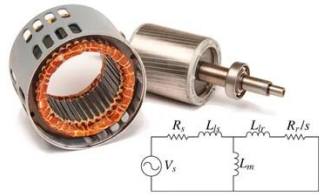
$$-e_k(t) = M_{1k} \frac{di_1(t)}{dt} + M_{2k} \frac{di_2(t)}{dt} + \dots + M_{nk} \frac{di_n(t)}{dt} + L \frac{di_k(t)}{dt}$$



III - Transformers

Magnetic circuits


- Boucherot's formula : Ideal coil (no losses)

- The winding is subjected to a sinusoidal voltage

$$v(t) = V\sqrt{2} \cdot \cos(\omega t)$$

=> Assumption of forced flux

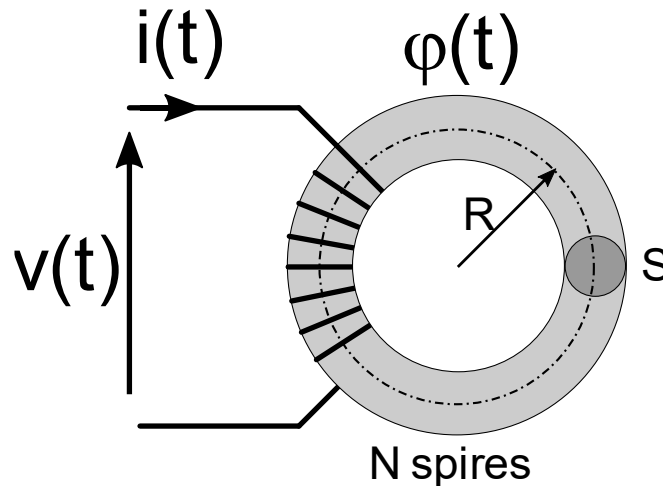
$$\frac{d\varphi(t)}{dt} = \frac{V\sqrt{2}}{N} \cdot \cos(\omega t)$$



$$\varphi(t) = \frac{V\sqrt{2}}{N} \cdot \int_0^t \cos(\omega t) \cdot dt$$

$$\varphi(t) = \frac{V\sqrt{2}}{N\omega} \cdot \sin(\omega t) + \varphi(0)$$


III - Transformers

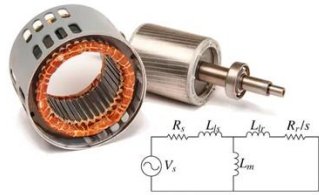

Magnetic circuits

- Boucherot's formula : Ideal coil (no losses)
- $\phi(0)=0$: no permanent magnet, no remanent flux, no second DC winding).
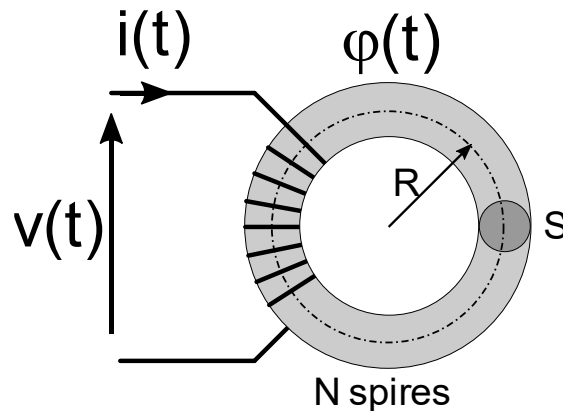
$$\varphi(t) = \frac{V\sqrt{2}}{N\omega} \cdot \sin(\omega t) + \varphi(0)$$




$$\varphi(t) = \frac{V\sqrt{2}}{N\omega} \cdot \sin(\omega t)$$

$$\varphi(t) = \frac{V\sqrt{2}}{N\omega} \cdot \cos(\omega t - \pi/2)$$

- The flux lags the current
- The relation $N\phi=Li$ (Hopkinson's law) gives the current

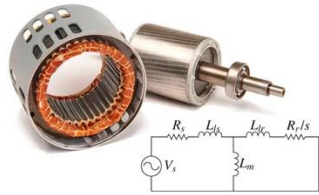
$$i(t) = \frac{V\sqrt{2}}{L\omega} \cdot \cos(\omega t - \pi/2)$$



III - Transformers

Magnetic circuits

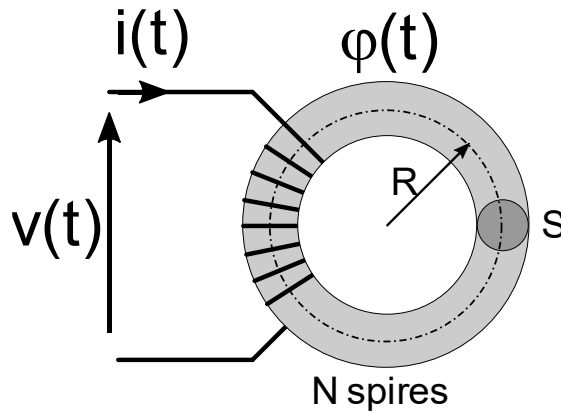- Boucherot's formula : Ideal coil (no losses)



$$\begin{cases} \varphi(t) = \frac{V\sqrt{2}}{N\omega} \cdot \cos(\omega t - \pi/2) \\ \varphi(t) = \Phi_M \cdot \cos(\omega t - \pi/2) \end{cases}$$


$$\frac{V\sqrt{2}}{N\omega} = \Phi_M$$

$$V = \frac{N \cdot \omega \cdot \Phi_M}{\sqrt{2}}$$

$$V = \frac{N \cdot (2 \cdot \pi \cdot f) \cdot S \cdot B_M}{\sqrt{2}}$$

$$V = \frac{2 \cdot \pi}{\sqrt{2}} \cdot S \cdot N \cdot B_M \cdot f$$
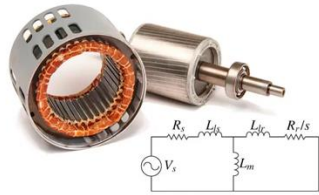
$$V = 4,44 \cdot S \cdot N \cdot B_M \cdot f$$




III - Transformers

Magnetic circuits

- Boucherot's formula : Ideal coil (no losses)


$$V = 4,44 \cdot S \cdot N \cdot B_M \cdot f$$

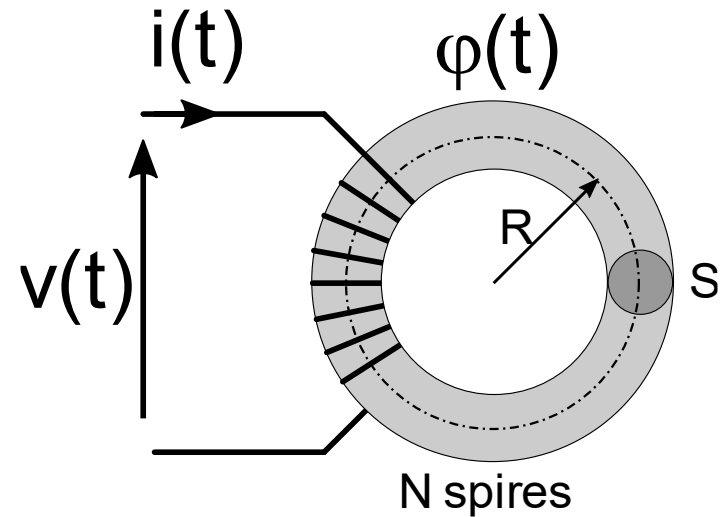If the flux ϕ of a coil is due to the current i flowing through it (Hopkinson's law), its maximum value ϕ_M depends only on the RMS value of the voltage v (at constant frequency).



The voltage imposes a flux and the winding draws the current accordingly

III - Transformers

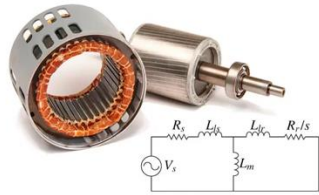



Magnetic circuits

- Defects of the iron-core coil: **hysteresis losses**
- Hysteresis losses correspond to the power required to magnetize and demagnetize the material over its hysteresis loop.
- Empirical formula:

$$P_H = K_H l S f B_{max}^n$$

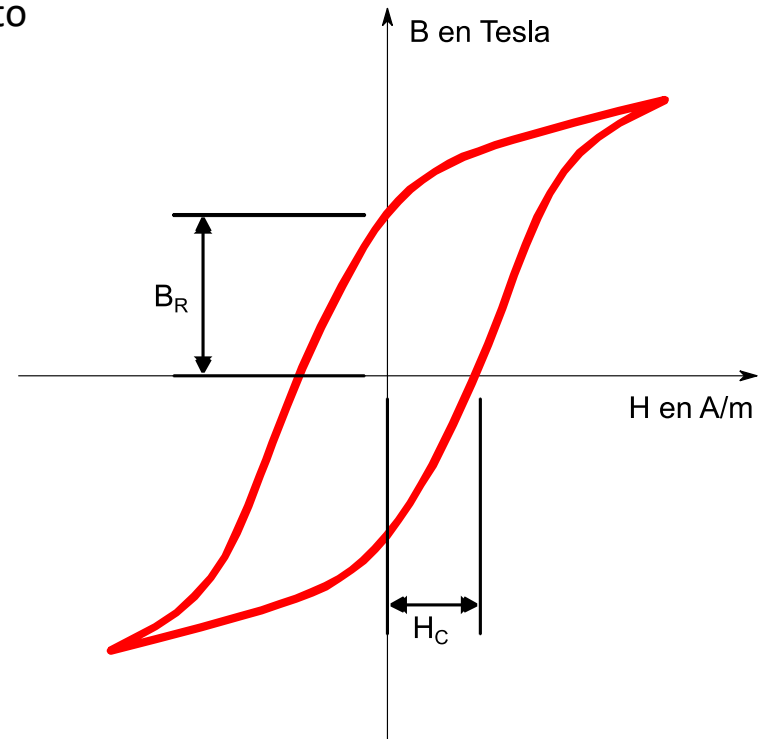- K_H is a material-related constant
- n is the Steinmetz coefficient (around 1.8)
- l is the mean field line, f the frequency, B_{max} the maximum induction field




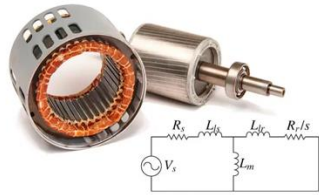


III - Transformers

Magnetic circuits

- Defects of the iron-core coil: Eddy currents
- Currents induced in the magnetic material in which they flow freely
- These currents cause losses in the form of power dissipated by Joule effect
- Empirical formula: $P_H = K_{FC} l S f^2 B_{max}^2$
- K_{FC} is a material-related constant
- d is the thickness of the foil in the case of a laminated material
- l is the mean field line, f the frequency, B_{max} the maximum induction field
- Defects of the iron-core coil: **IRON LOSSES P_F** $P_F = P_H + P_{FC}$

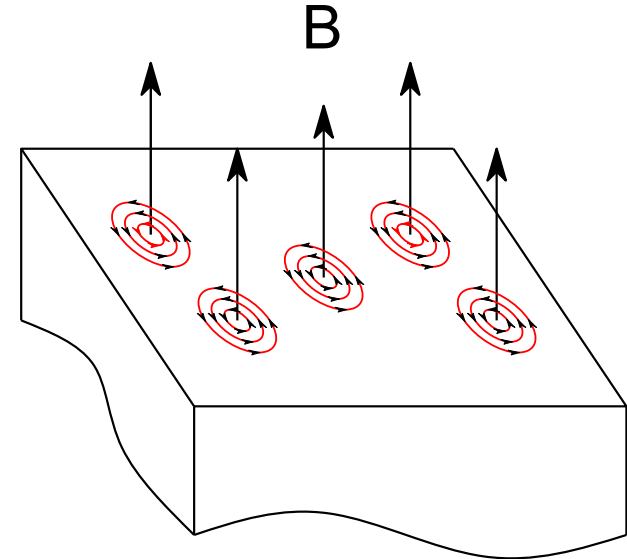

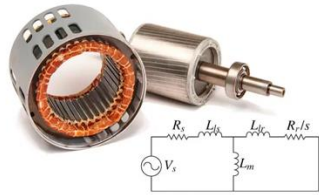

III - Transformers


Magnetic circuits

- Defects of the iron-core coil: [Leak inductance](#)
- Magnetic materials are never perfect, and never channel all the field lines
 - => Part of the magnetic flux propagates in the air via less reluctant paths
 - => This corresponds to magnetic leaks (flux outside the magnetic circuit)
- The magnetic field channeled in the magnetic circuit is called “magnetizing flux”


$$\phi = \phi_m + \phi_f$$

$$v(t) = -N \frac{d\phi}{dt} = -\left(L_m \frac{di}{dt} + L_f \frac{di}{dt}\right)$$

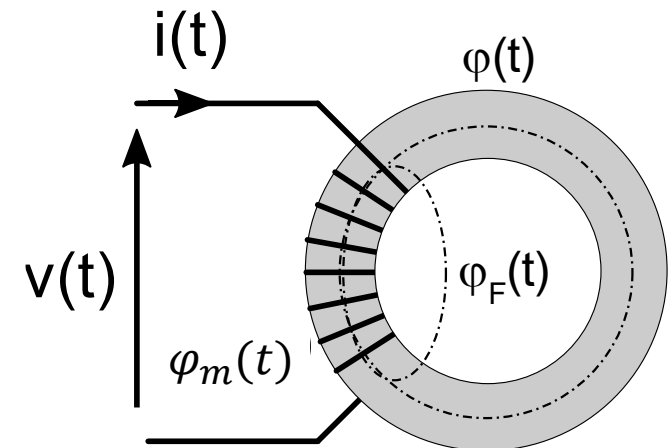- L_m is the magnetizing inductance, L_f is the leak inductance




III - Transformers

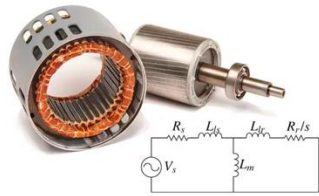


Magnetic circuits

- Linear model of the iron-core coil:

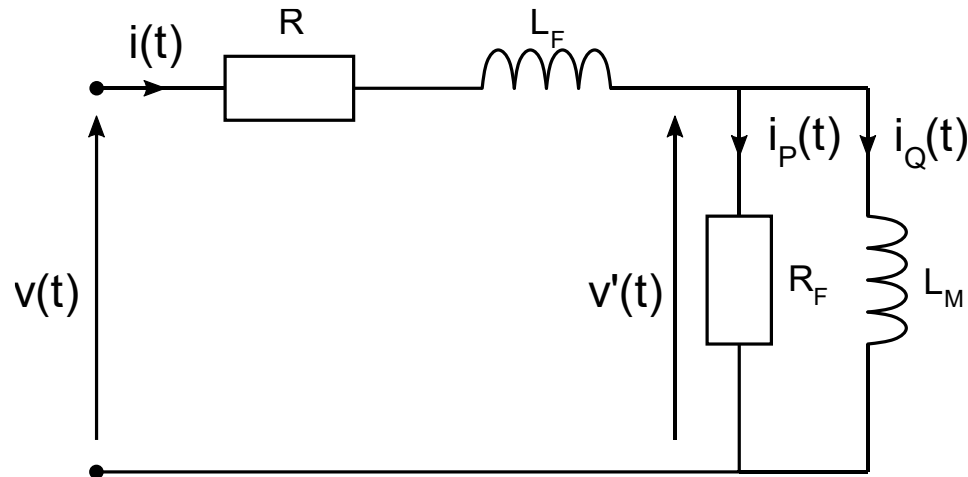

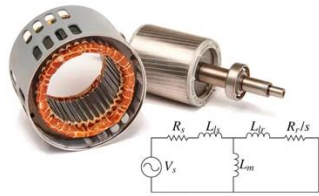- R is the resistance of the coil N turns
- L_F is the leak inductance, L_M is the magnetizing inductance
- R_F is the resistor modelling the iron losses




III - Transformers


Single-phase transformer

- The transformer enables a **change in the RMS value of an AC voltage** to be achieved with high efficiency => step-up transformer or step-down transformer
- A single-phase transformer consists of two windings wound on the same magnetic circuit
=> Usually, the two windings have different numbers of turns

PRIMARY SIDE

SECONDARY SIDE

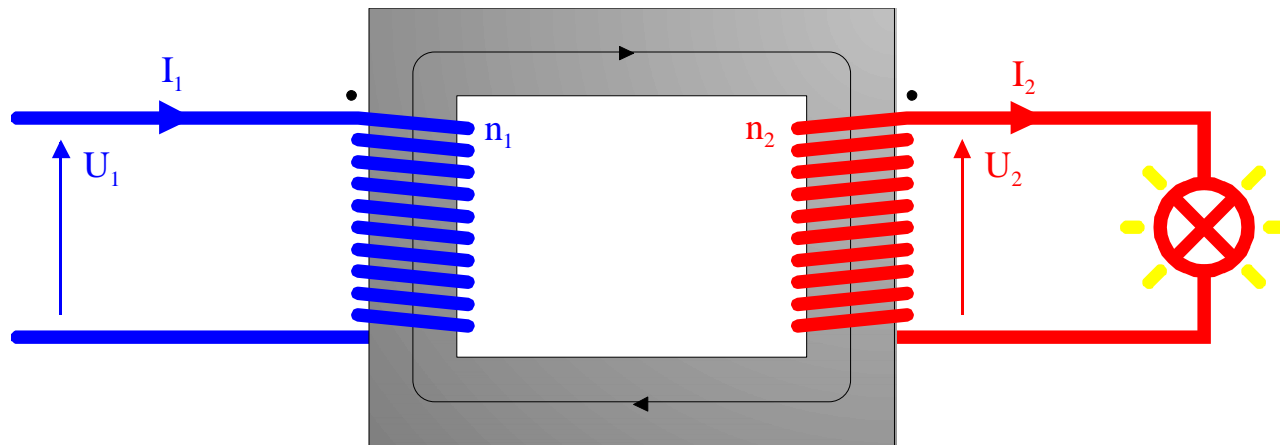

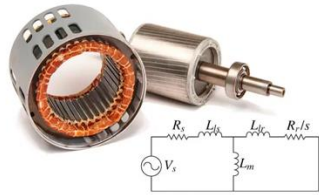


III - Transformers


Single-phase transformer

- Functional approach: More precisely, The transformer is a static machine that allows sinusoidal quantities (voltages, currents) to be modified without changing their frequency.

=> **Voltage adaptation**: step-down or step-up transformer

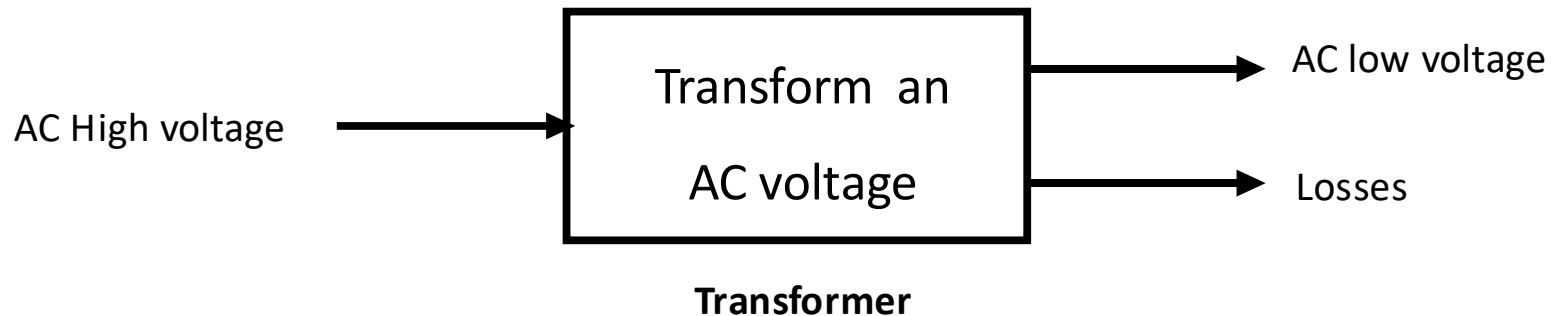=> **Galvanic insulation**: insulation transformer





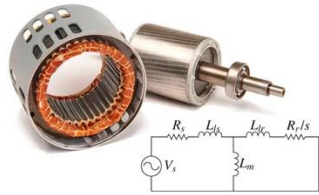


III - Transformers

Single-phase transformer

- Power grid base structure:

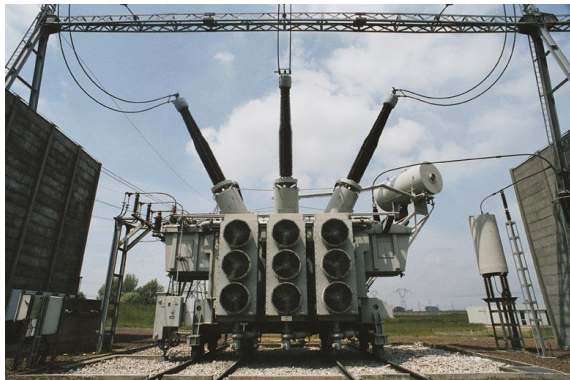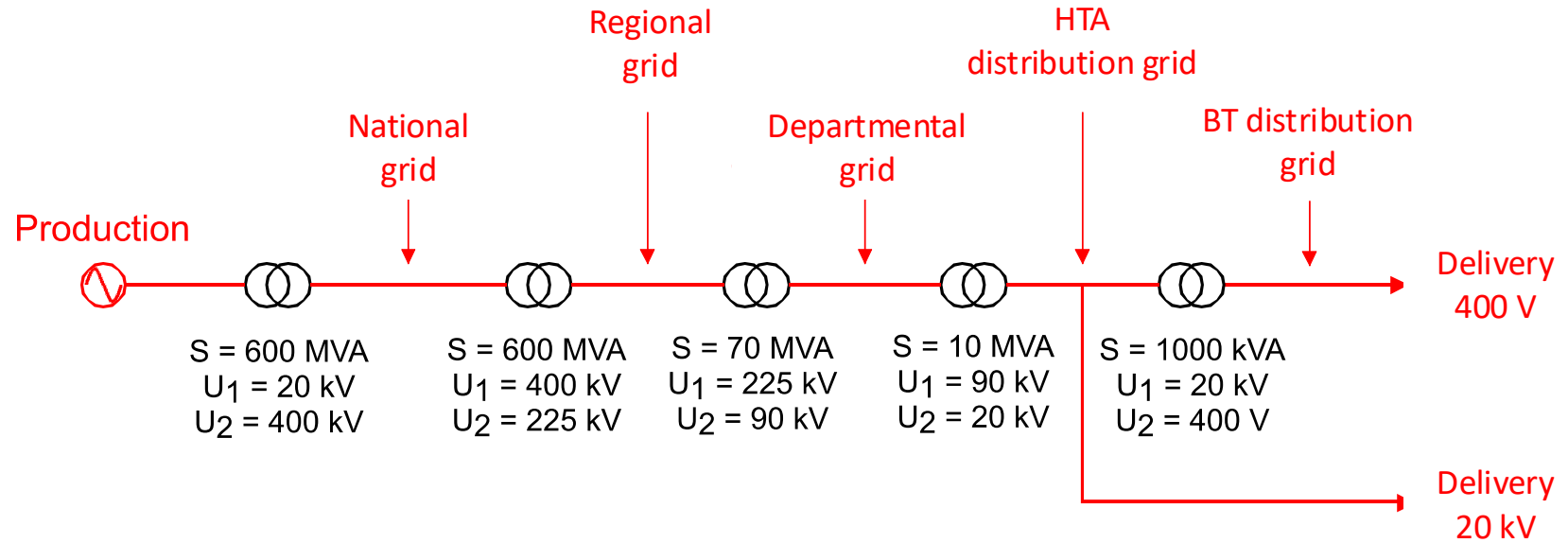

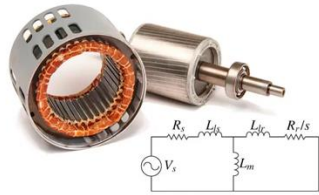

III - Transformers

Single-phase transformer

- Principle:

- Hopkinson's relation in the case of a single winding at the primary side:



$$n_1 \cdot i_1 = \mathcal{R} \cdot \Phi$$

- For two windings and $i_2 = 0$ (no load)


$$e_1 = -v_1 = -n_1 \frac{d\phi}{dt}$$

$$v_1 = n_1 \frac{d\phi}{dt}$$

$$e_2 = -n_2 \frac{d\phi}{dt} = v_2$$

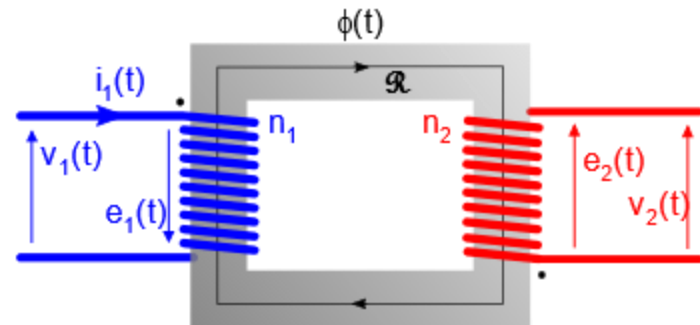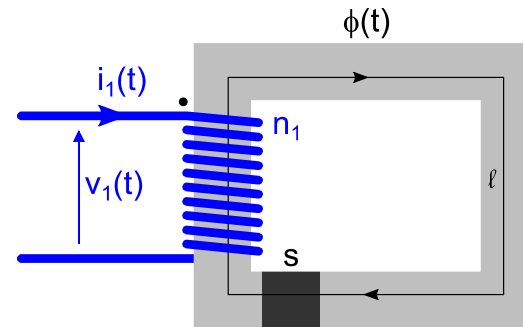

III - Transformers

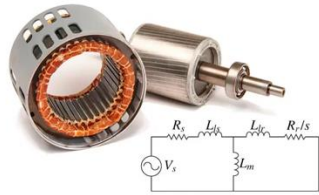

Single-phase transformer

- Principle:


- For two windings and $i_2 \neq 0$ (presence of a load)


$$n_1 \cdot i_1 + n_2 \cdot i_2 = \mathcal{R} \phi$$

$$e_1 = -v_1 = -n_1 \frac{d\phi}{dt}$$

$$v_1 = n_1 \frac{d\phi}{dt}$$

$$e_2 = -n_2 \frac{d\phi}{dt} = v_2$$

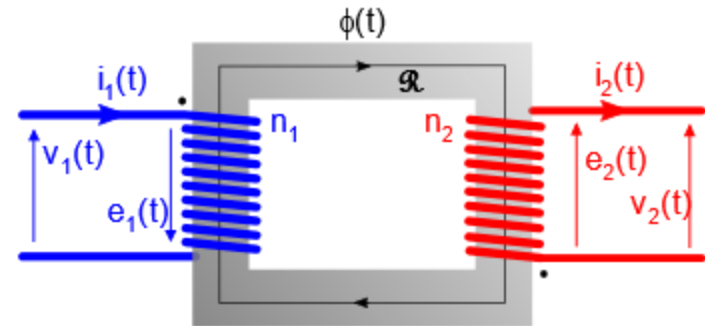

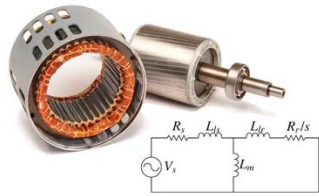

III - Transformers

Single-phase transformer


- Principle: receptor convention/generator convention


- Seen from the primary grid, the transformer is a receptor

- Seen from the load, the transformer is a generator

=> Receptor convention at the primary side

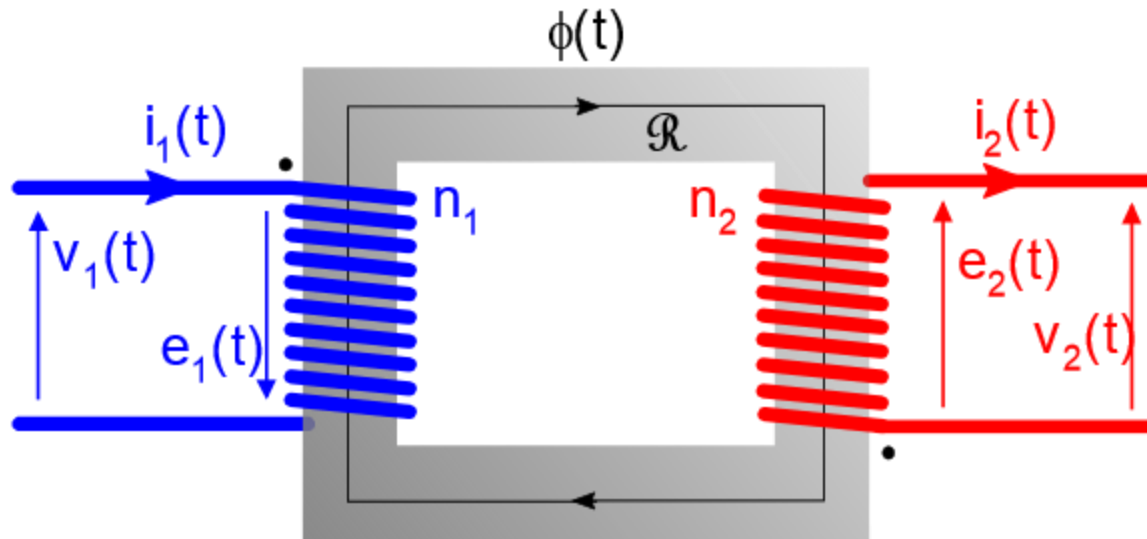=> Generator convention at the secondary side



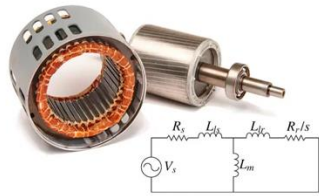

III - Transformers

Single-phase transformer



- Principle: homonymous terminals


- The winding direction is marked with dots (\bullet). Terminals marked in this way are called “homonymous terminals”. They correspond to points of the same instantaneous polarity.

- Sign conventions for magnetic and electrical quantities:

=> A positive current entering through a homonymous terminal creates a positive flux in the magnetic circuit

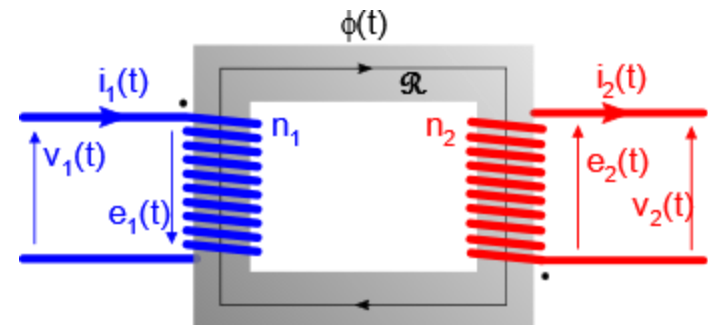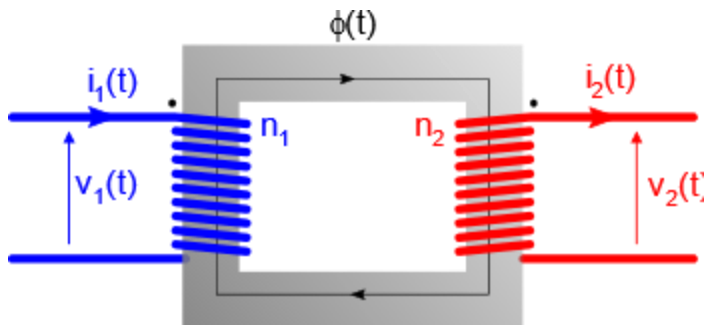=> According to Hopkinson's law, the magnetomotive force is preceded by the sign + if the current orientation arrow enters through a homologous terminal, and by the sign - otherwise.



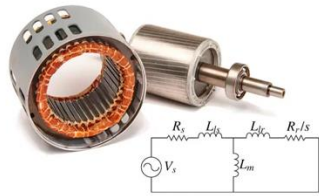


III - Transformers

Single-phase transformer

- Principle: the **ideal transformer** - voltages
- Ideal windings = no voltage drop, no losses
- Ideal magnetic circuit = zero reluctance

$$v_1 = -e_1 = n_1 \frac{d\phi}{dt}$$

$$v_2 = e_2 = -n_2 \frac{d\phi}{dt}$$

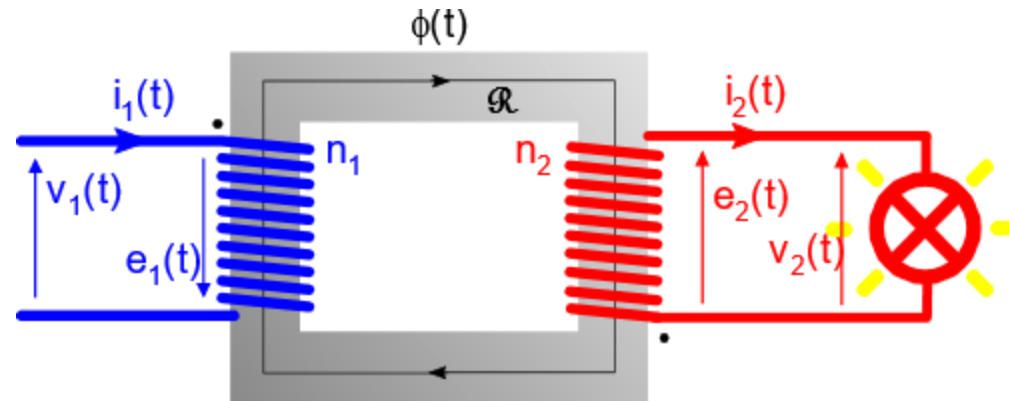


- The **transformation ratio** is given by:

$$m = \frac{n_2}{n_1} = -\frac{v_2}{v_1}$$

$m > 1$: Step-up transformer

$m < 1$: Step-down transformer

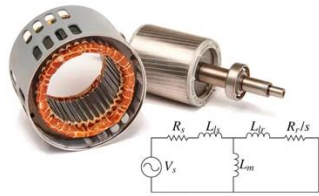

III - Transformers

Single-phase transformer

- Principle: the **ideal transformer** - currents

- Ideal windings = no voltage drop, no losses


- Ideal magnetic circuit = **zero reluctance**

- Hopkinson's relation:

$$n_1 \cdot i_1 + n_2 \cdot i_2 = \mathcal{R}\phi$$



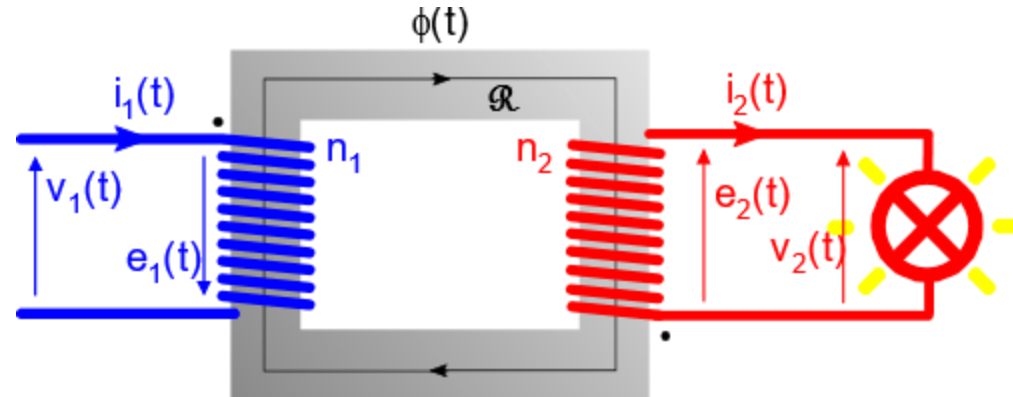
$$n_1 \cdot i_1 + n_2 \cdot i_2 = \mathcal{R}\phi = 0$$



$$\frac{i_2}{i_1} = -\frac{n_1}{n_2}$$

$$\frac{i_2}{i_1} = -\frac{1}{m}$$

$$i_1 = -m \cdot i_2$$

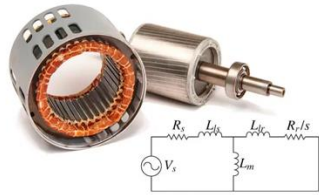


III - Transformers

Single-phase transformer


- Principle: the ideal transformer - symbol

$$m = \frac{n_2}{n_1} = \frac{V_2}{V_1} = \frac{I_1}{I_2}$$
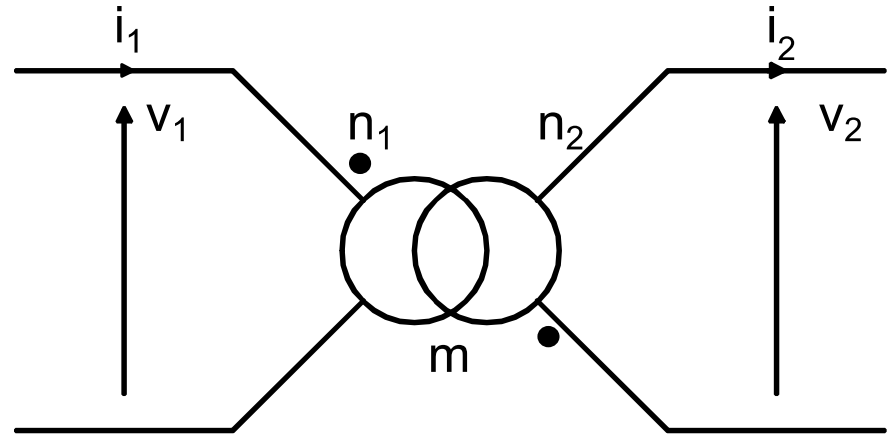
$$\eta = \frac{P_2}{P_1} = \frac{V_2 \cdot I_2}{V_1 \cdot I_1} = 1$$



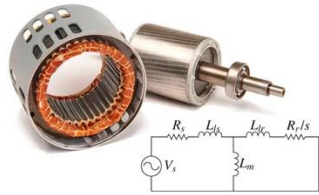- Conservation of power, for the ideal transformer only



III - Transformers

Single-phase transformer

- Principle: winding imperfection
- Joule losses (or copper losses)

$$P_J = r_1 \cdot I_1^2 + r_2 \cdot I_2^2$$


$$R = \rho \cdot \frac{l}{S} \quad \rho_\Theta = \rho_0 (1 + a\Theta)$$

Copper (Cu) : $\rho_0 = 1,6 \cdot 10^{-8} \Omega \cdot m$, $a = 0,39$

Aluminum (Al) : $\rho_0 = 2,42 \cdot 10^{-8} \Omega \cdot m$, $a = 0,43$

$$v_1 = -e'_1 + r_1 \cdot i_1$$

$$v_2 = e'_2 - r_2 \cdot i_2$$

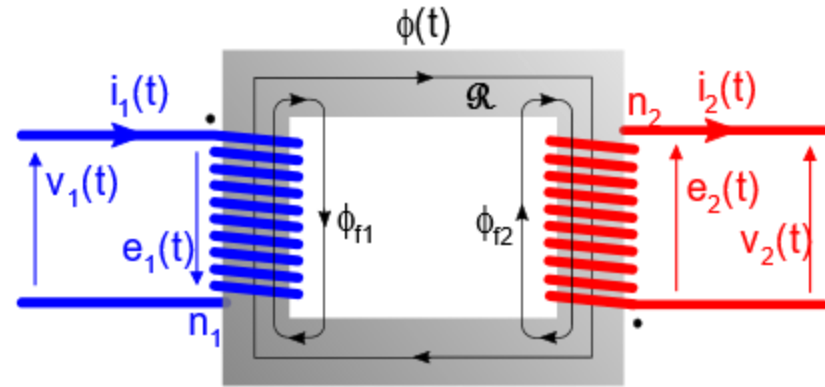


- Magnetic leaks


$$\phi_T = \phi_{f1} + \phi_{f2} + \phi$$

$$e'_1 = n_1 \cdot \frac{d\phi}{dt} + n_1 \cdot \frac{d\phi_{f1}}{dt}$$

$$e'_1 = e_1 + l_1 \cdot \frac{di_1}{dt}$$
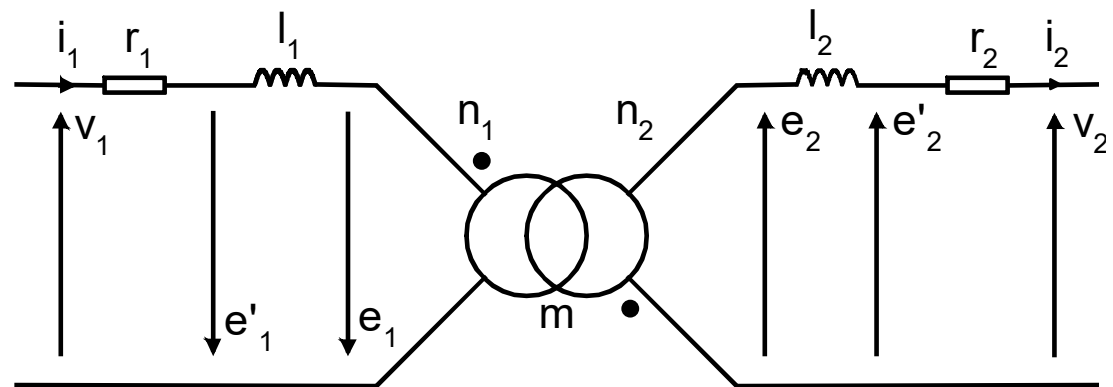
$$e'_2 = e_2 + l_2 \cdot \frac{di_2}{dt}$$



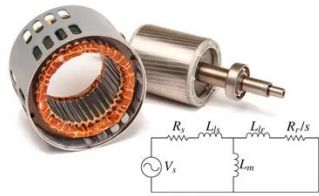



III - Transformers


Single-phase transformer

- Principle: magnetic circuit imperfection
- Finite permeability and non zero reluctance of the magnetic circuit

=> A primary current is consumed at no load

$$\mathcal{R}\phi = n_1 \cdot i_{10}$$

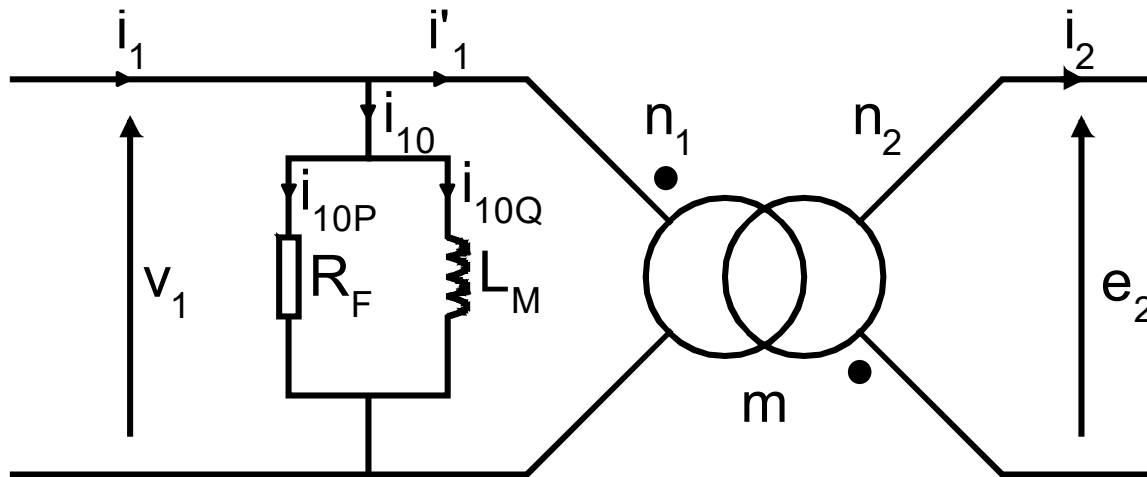
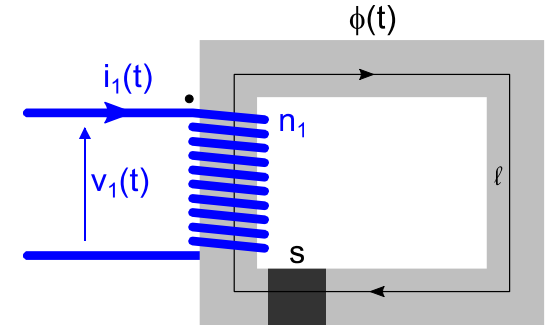


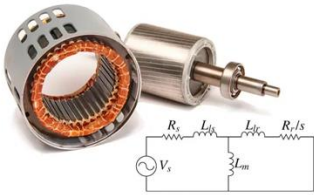


III - Transformers

Single-phase transformer

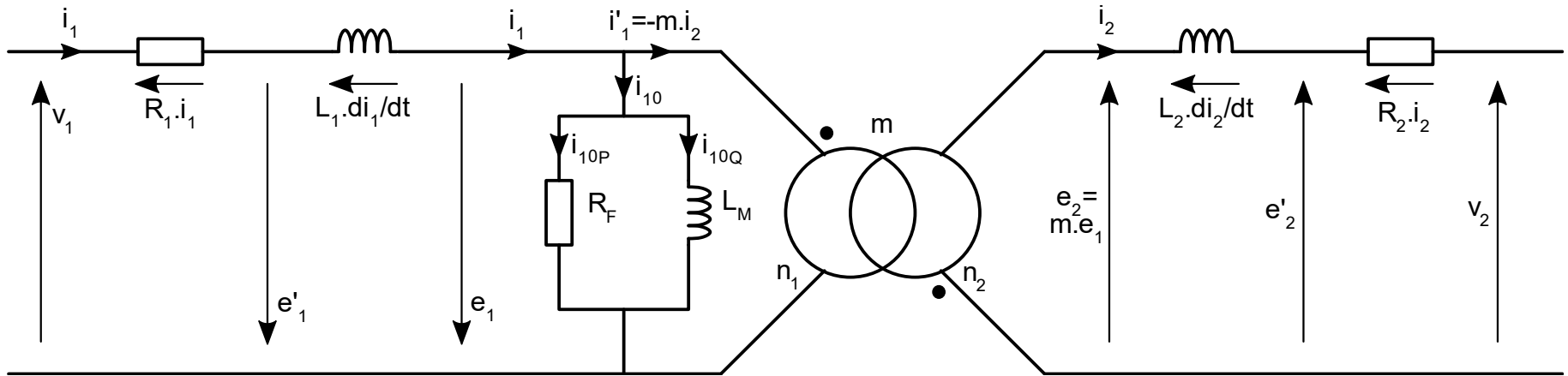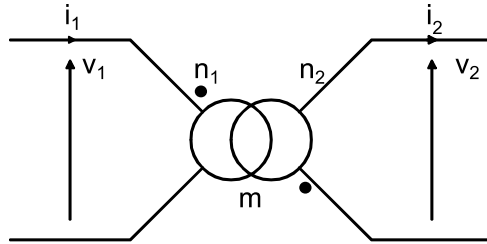- Equivalent model of the real transformer



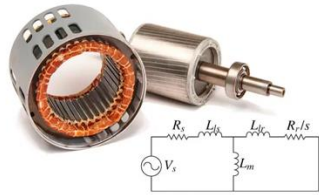


III - Transformers

Single-phase transformer

- Equivalent model of the real transformer: Impedance transfer
- A transformer, in which an impedance Z_2 is connected to the secondary side is equivalent to an impedance Z_1 connected to the primary side with:

$$Z_1 = \frac{Z_2}{m^2}$$

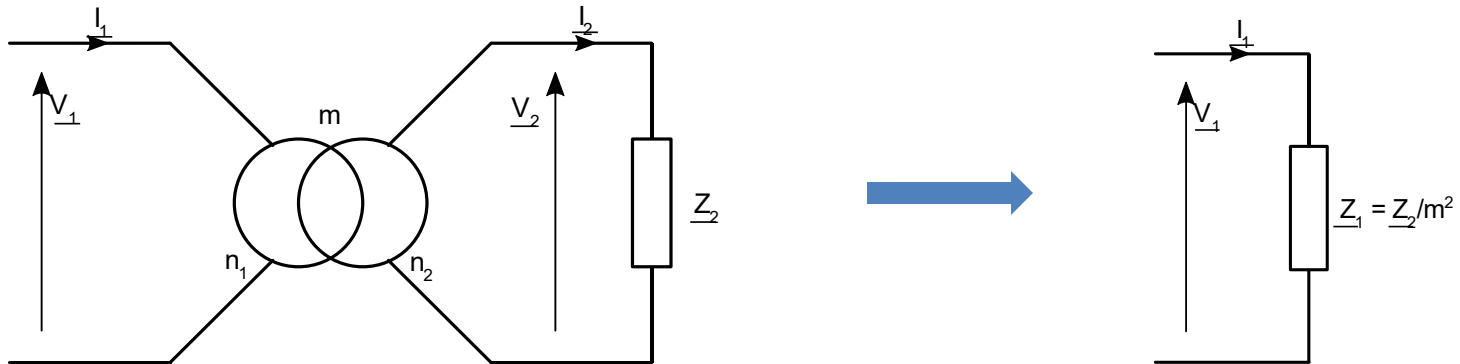


- We remind: $I_1 = m \cdot I_2$ et $V_1 = \frac{V_2}{m}$

- We write: $Z_2 = \frac{V_2}{I_2}$ et $Z_1 = \frac{V_1}{I_1}$

$$Z_1 = \frac{V_1}{I_1} = \frac{V_2/m}{m \cdot I_2} = \frac{1}{m^2} \cdot \frac{V_2}{I_2} = \frac{Z_2}{m^2}$$

$$Z_1 = \frac{Z_2}{m^2}$$

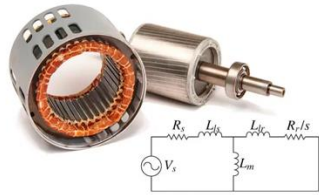



III - Transformers

Single-phase transformer

- Equivalent model of the real transformer: [Kapp's assumption](#)
- The voltage drop across R_1 and L_1 is small compared to the voltages e_1 and V_1

=> R_1/L_1 and R_F/L_p can be swapped

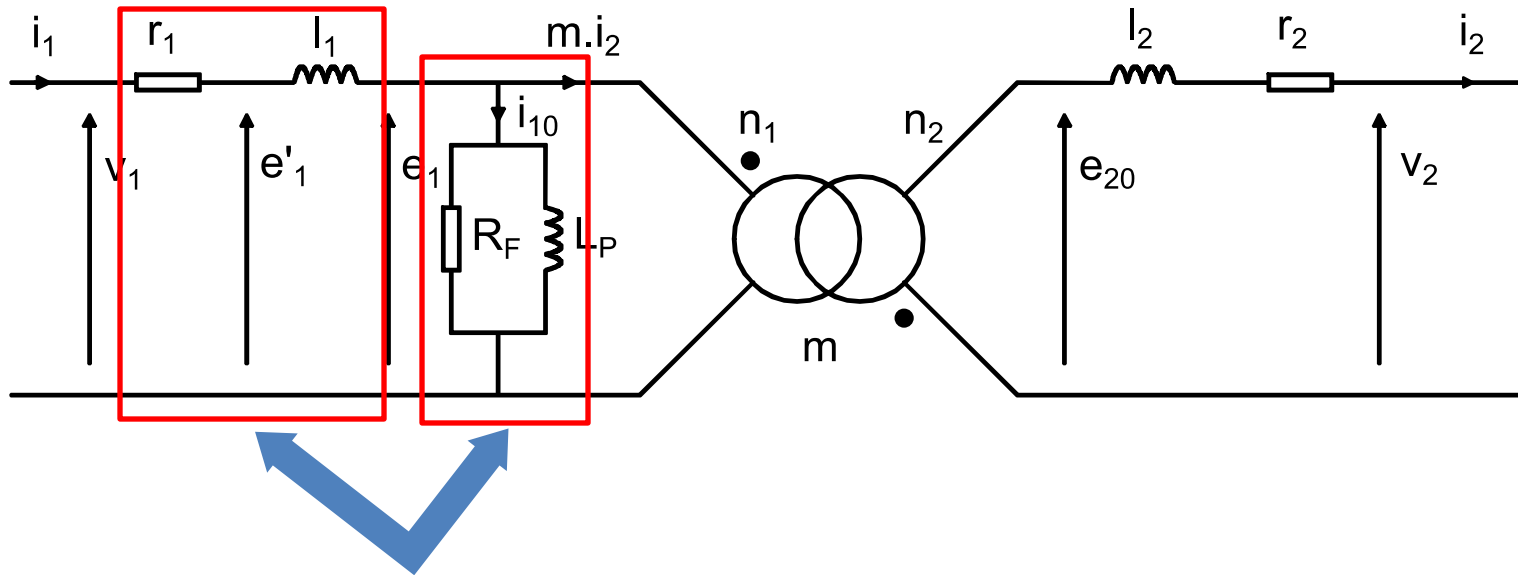


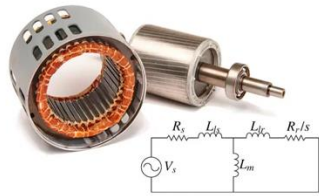

III - Transformers

Single-phase transformer

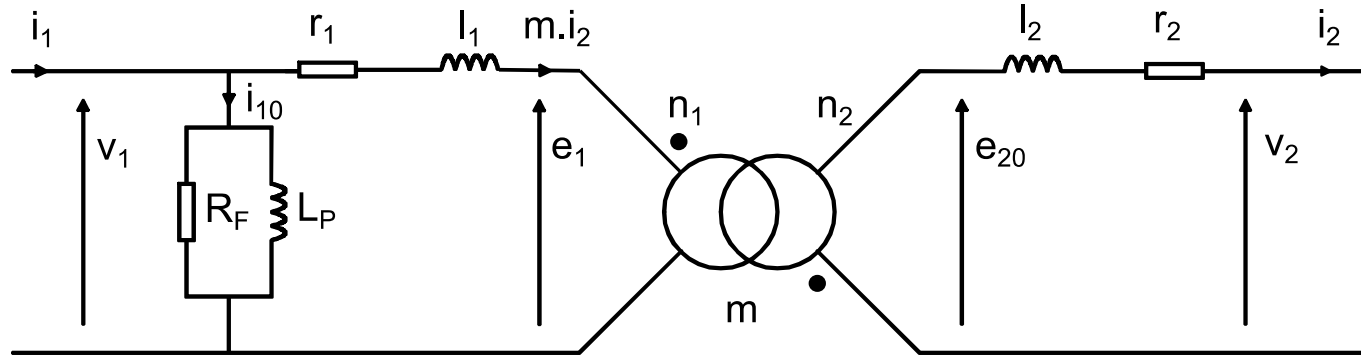- Equivalent model of the real transformer: **Kapp's assumption**




- **Kapp's equivalent secondary model** (R_1 and L_1 are transferred to the secondary side)


$$r_s = r_2 + m^2 \cdot r_1$$

$$l_s = l_2 + m^2 \cdot l_1$$
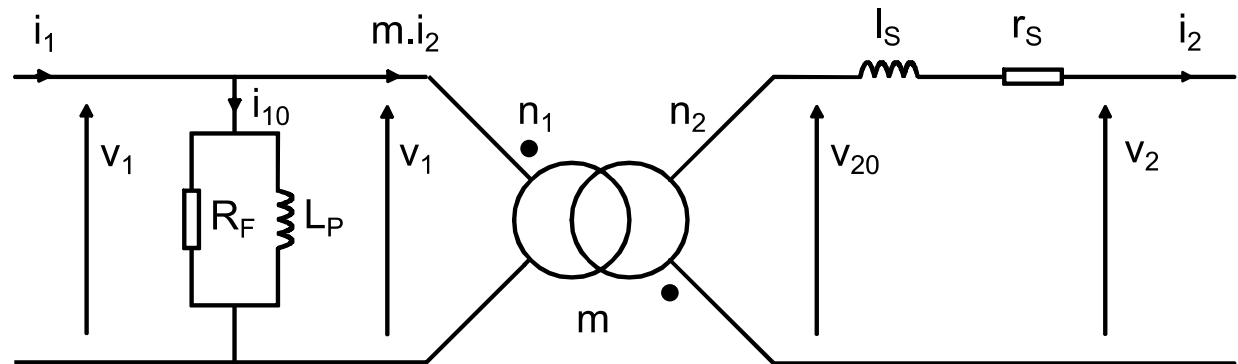
$$m = \frac{n_2}{n_1} = \frac{V_{20}}{V_1} \cong \frac{I_1}{I_2}$$


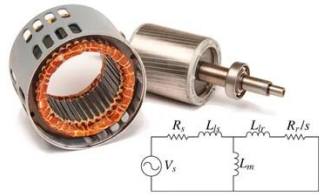
$$\underline{V}_2 = -m \cdot \underline{V}_1 + R_s \cdot \underline{I}_2 + jX_s \cdot \underline{I}_2$$



III - Transformers

Single-phase transformer

- Equivalent model of the real transformer: Kapp's assumption
- Kapp's equivalent primary model (R_2 and L_2 are transferred to the primary side)

$R_p = R_1 + \frac{R_2}{m^2}$: total winding resistance transferred to the primary side


$X_p = X_1 + \frac{X_2}{m^2}$: total winding reactance transferred to the primary side


$Z_p = R_p + jX_p$: total winding impedance transferred to the primary side

$\frac{Z}{m^2}$: secondary side load transferred to the primary side.

$$\underline{V}_1 = \frac{\underline{Z}}{m^2} \cdot \underline{I}_1 + \underline{Z}_p \cdot \underline{I}_1$$

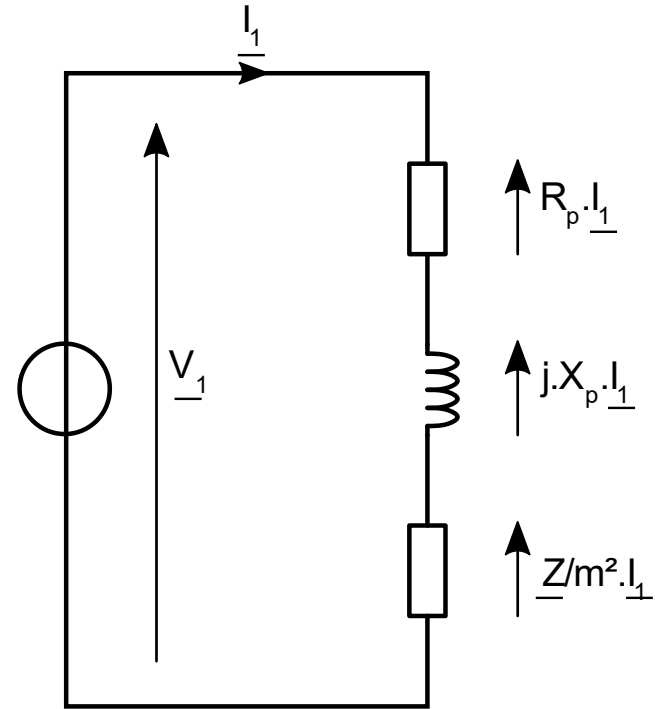(this model will be useful for the induction motor)



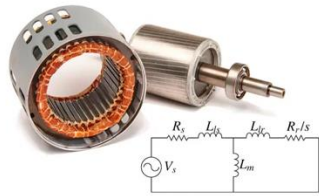

III - Transformers


Single-phase transformer


- Determining the elements of the Kapp secondary equivalent model:
- **Test at no load:**
- conditions: Transformer supplied at **rated** voltage (V_{1N}) + open secondary side ($I_2 = 0$)
- Measured quantities: V_{1N} , I_{10} , V_{20} , P_{10} (iron losses) and Q_{10}

$$R_F = \frac{V_{1N}^2}{P_{10}}$$

$$X_P = L_P \cdot \omega = \frac{V_{1N}^2}{Q_{10}} \quad \text{with } Q_{10} = \sqrt{(V_{1N} \cdot I_{10})^2 - P_{10}^2}$$

$$m = \frac{V_{20}}{V_1}$$

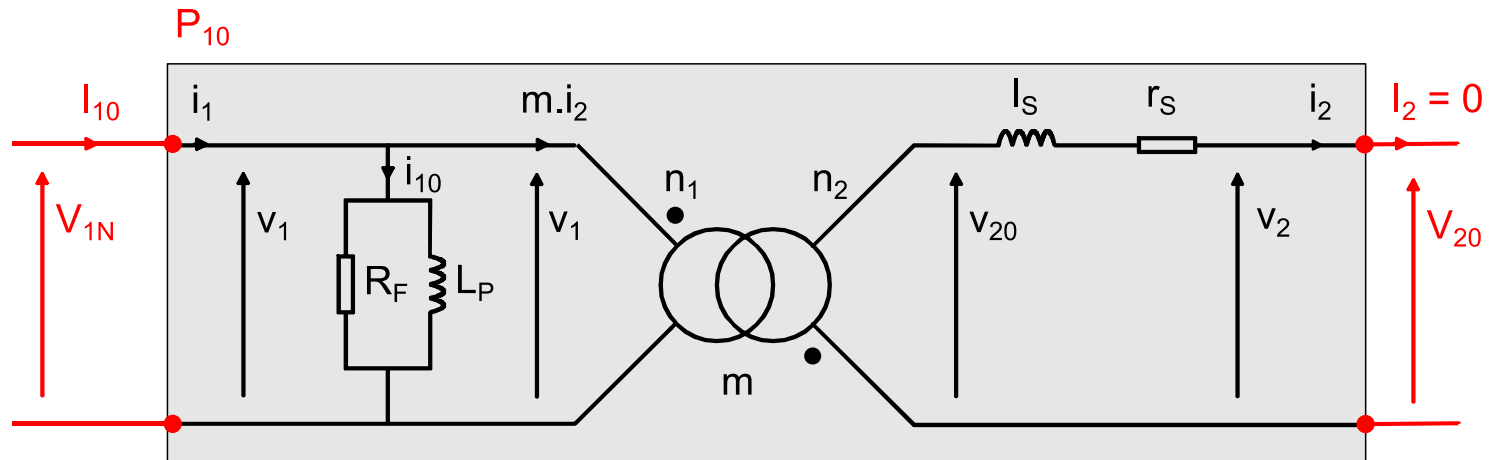

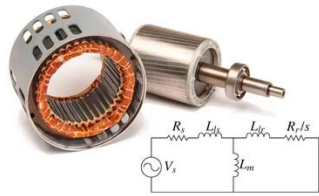



III - Transformers

Single-phase transformer

- Determining the elements of the Kapp secondary equivalent model:
- **Short-circuit test:** (short circuit at the secondary side)
- conditions: Transformer supplied at **reduced** voltage (V_{1CC}) + **rated** secondary side current ($I_{2CC} = I_{2N}$)
- Measured quantities: V_{1CC} , I_{1CC} , I_{2CC} , P_{1CC} (Joule losses) and Q_{1CC}
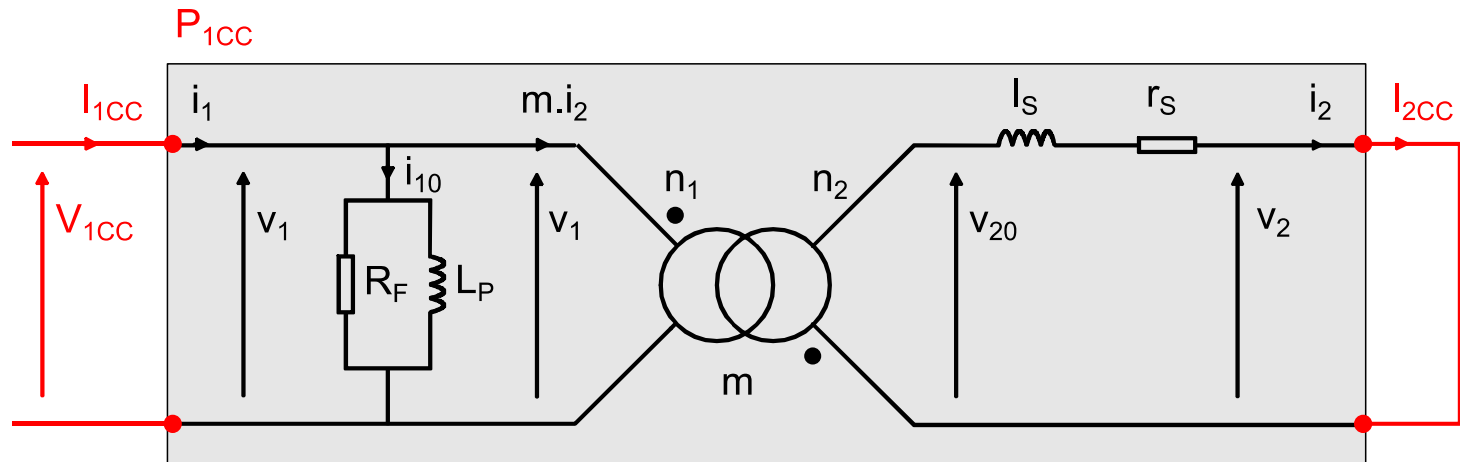
$$R_S = \frac{P_{1CC}}{I_{2CC}^2} \quad X_S = L_S \cdot \omega = \frac{Q_{1CC}}{I_{2CC}^2} \quad \text{with } Q_{1CC} = \sqrt{(V_{1CC} \cdot I_{1CC})^2 - P_{1CC}^2}$$



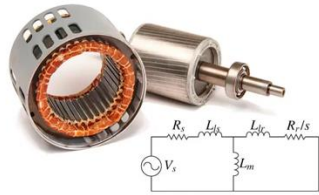



III - Transformers


Single-phase transformer

- Voltage drop at the secondary side of the transformer:
- **Kapp's triangle:** case of the inductive load ($\phi_2 > 0$)

$$\underline{V}_{20} = m \cdot \underline{V}_1 = (R_S + jX_S) \cdot \underline{I}_2 + \underline{V}_2$$
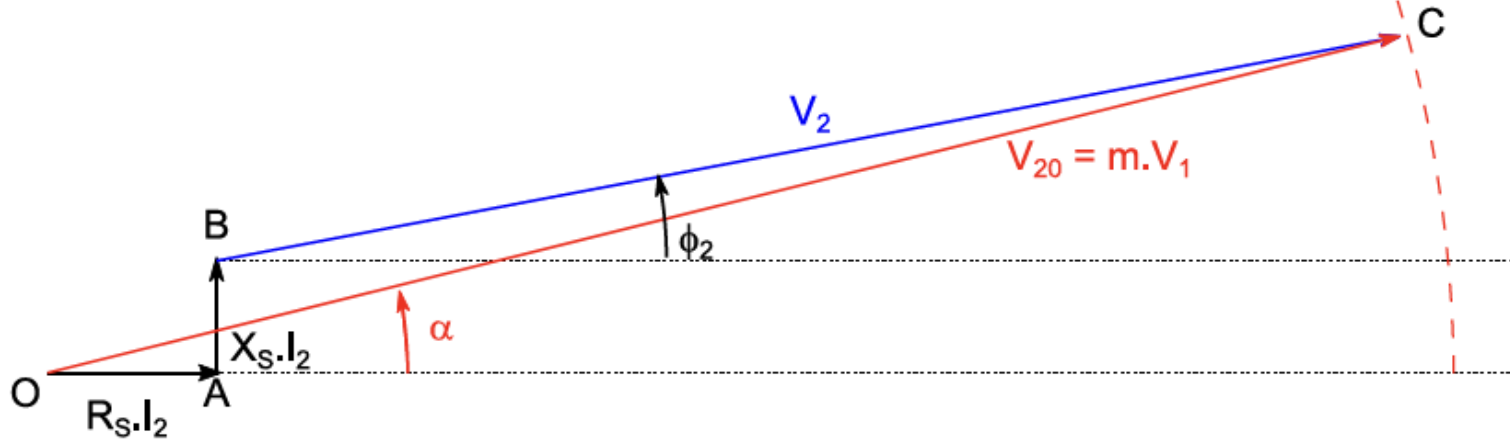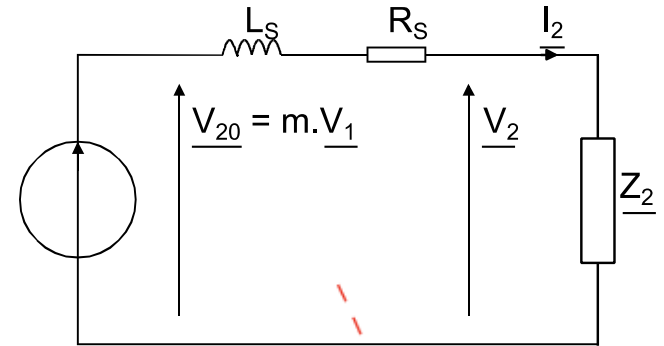
$$\Delta V_2 \approx R_S \cdot I_2 \cos \phi_2 + X_S \cdot I_2 \cdot \sin \phi_2$$



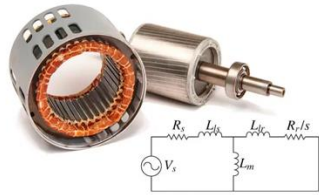


III - Transformers

Single-phase transformer

- Efficiency:
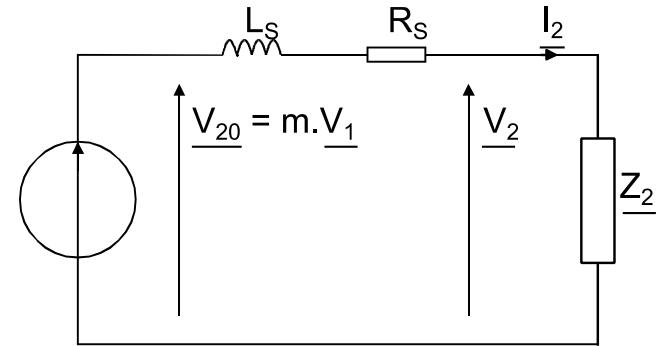
$$\eta = \frac{V_2 \cdot I_2 \cdot \cos \varphi_2}{V_2 \cdot I_2 \cdot \cos \varphi_2 + R_S \cdot I_2^2 + P_F}$$




- P_F is obtained from the test at no load (P_{10})

- Optimum current obtained from

$$\eta = \frac{V_2 \cdot \cos \varphi_2}{V_2 \cdot \cos \varphi_2 + R_S \cdot I_2 + \frac{P_{Fer}}{I_2}}$$

- The maximum efficiency is given for
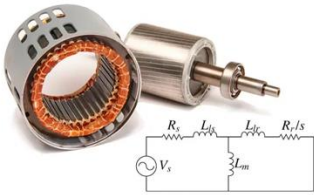
$$R_S \cdot I_{2opt} = \frac{P_{Fer}}{I_{2opt}} \text{ and } I_{2opt} = \sqrt{\frac{P_{Fer}}{R_S}}$$




III - Transformers


Three-phase transformer


- Construction and connection:

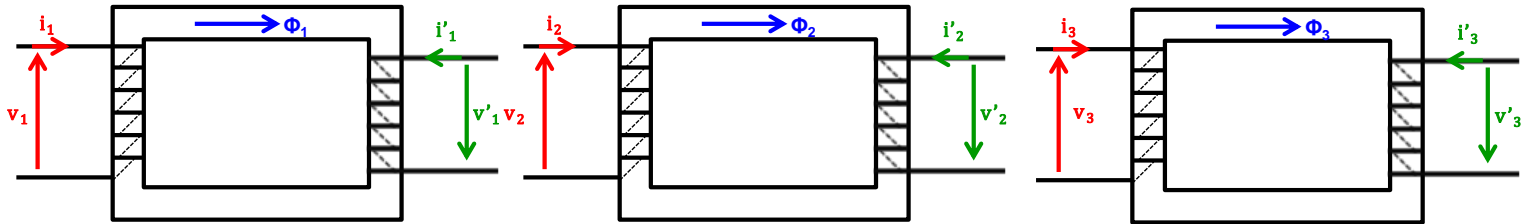- At first glance, the three-phase transformer can be considered as the combination of 3 single-phase transformers



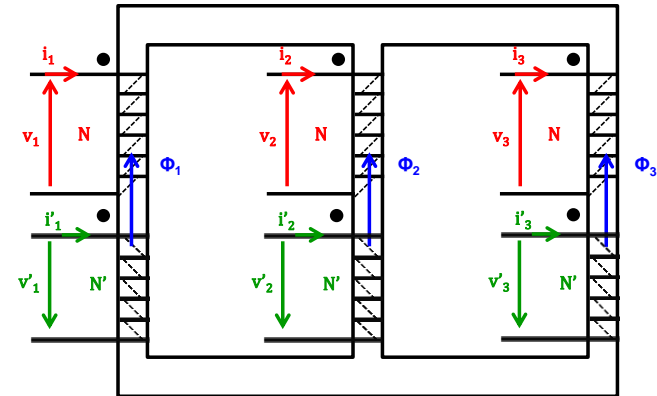- Or it can be integrated on a single magnetic circuit comprising 3 columns, each carrying the primary winding and the secondary winding



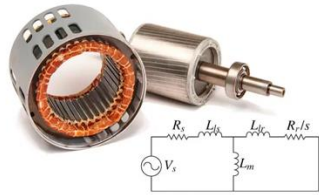

III - Transformers

Three-phase transformer

- Construction and connection:
- Both the primary and the secondary sides of the transformer need to be connected (delta or Y)
- The nature of these couplings is designated by letters, using upper case letters for the high voltage side and lower case letters for the secondary side

1st letter (upper case): connection on H.T. side

- **Y:** « star »


- **D** or **Δ:** delta

2nd letter (lower case): coupling on B.T. side

- **y:** star

- **d:** delta

Add letter “ N ou n ” if neutral is out.

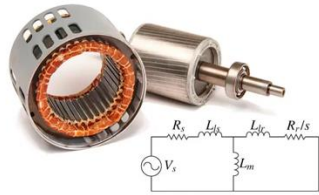

III - Transformers

Three-phase transformer

- Hourly index: Phase shift angle between primary and secondary voltages expressed in hours

- Marked from 0 to 11, each hour angle is always a multiple of 30° :


=> 0 for 0°

=> 1 for 30°

=> 2 for 60° , and

=> 6 for 180°

=> ...

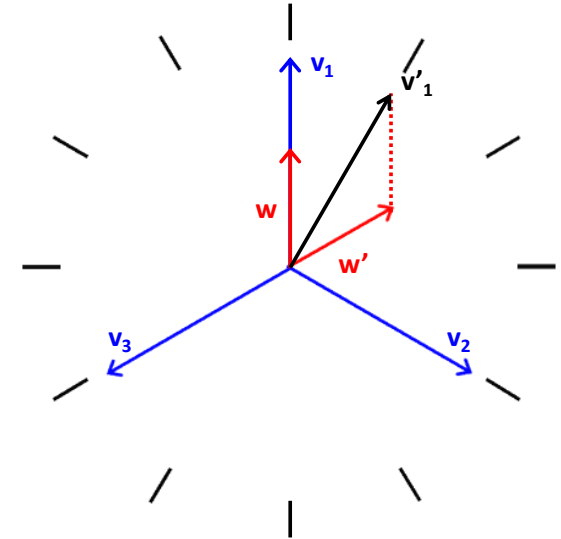


- That's why a specific representation has been chosen:

=> On the same Fresnel diagram, we plot two vectors representing two homologous voltages, one on the primary side, the other on the secondary side.

=> The voltage on the primary side is shown vertically, pointing upwards.



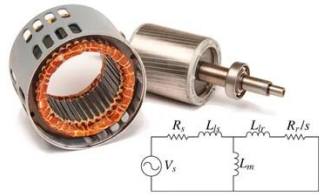
If we consider these two vectors as the two hands of a watch, the time indicated by the watch is by definition the transformer hourly index




III - Transformers

Three-phase transformer

- Example of Dyn 11 connection:

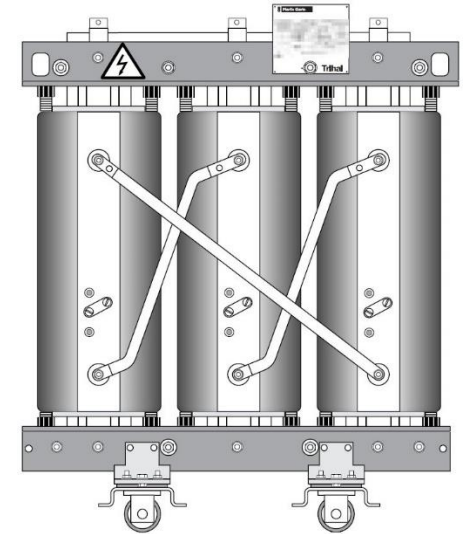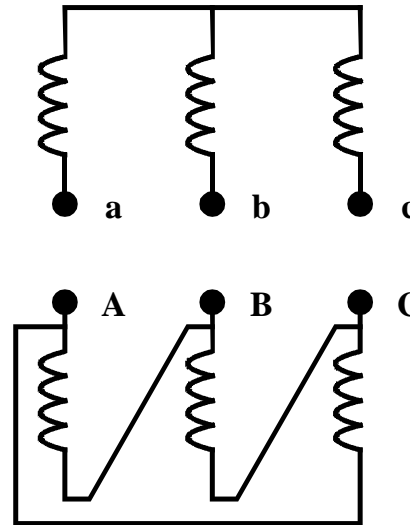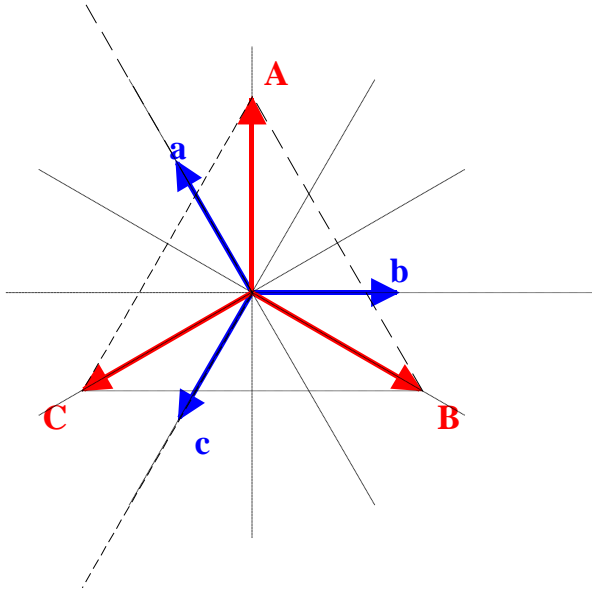


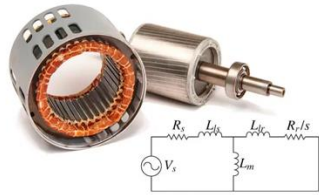
- High-voltage side => delta coupling.
- Low-voltage side => Y connection with neutral out.
- 330° phase shift (11x30) between primary and secondary.




III - Transformers

Three-phase transformer

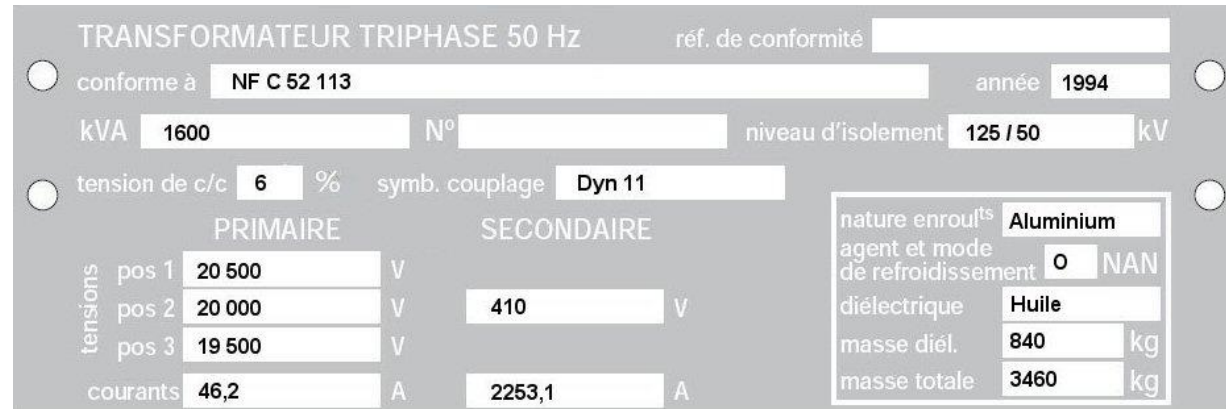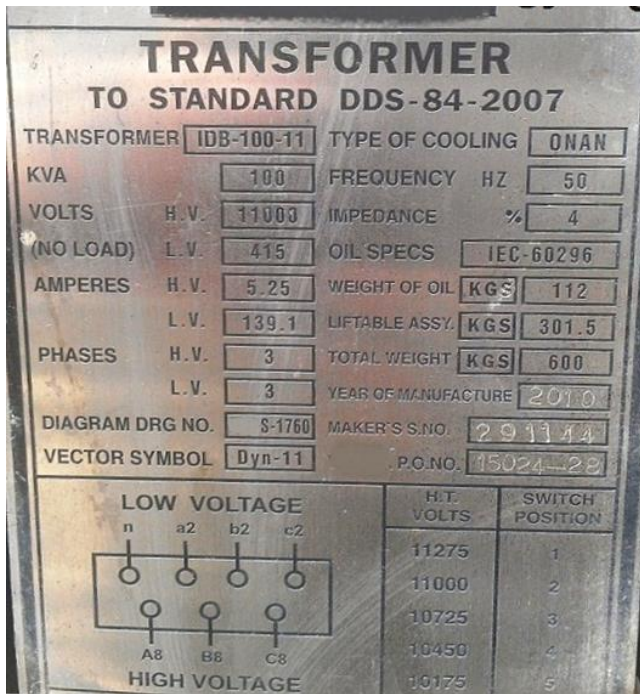- Transformer name plate: gives all the rating



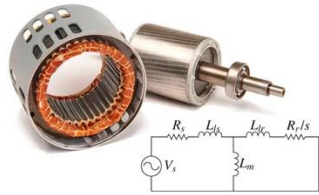

III - Transformers


Three-phase transformer

- Equivalent model of the real transformer:
- Each transformer column can be modeled separately by a single-phase equivalent diagram at the secondary (see before)
- Each element of the secondary model can be determined by the same tests as those of the single-phase transformer
- Test at no load:

$$R_F = \frac{3V_N^2}{P_0} \quad X_P = L_P \cdot \omega = \frac{3V_N^2}{Q_0} \quad \text{with } Q_0 = \sqrt{(V_N \cdot I_0)^2 - P_0^2} \quad m = \frac{V'_N}{V_N}$$

- Short-circuit test: (short circuit at the secondary side)

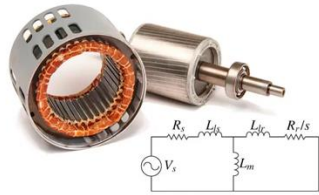
$$R_S = \frac{P_{CC}}{3I_{CC}^2} \quad X_S = L_S \cdot \omega = \frac{Q_{CC}}{3I_{CC}^2} \quad \text{with } Q_{CC} = \sqrt{(V_{CC} \cdot I_{CC})^2 - P_{CC}^2}$$




III - Transformers

Three-phase transformer

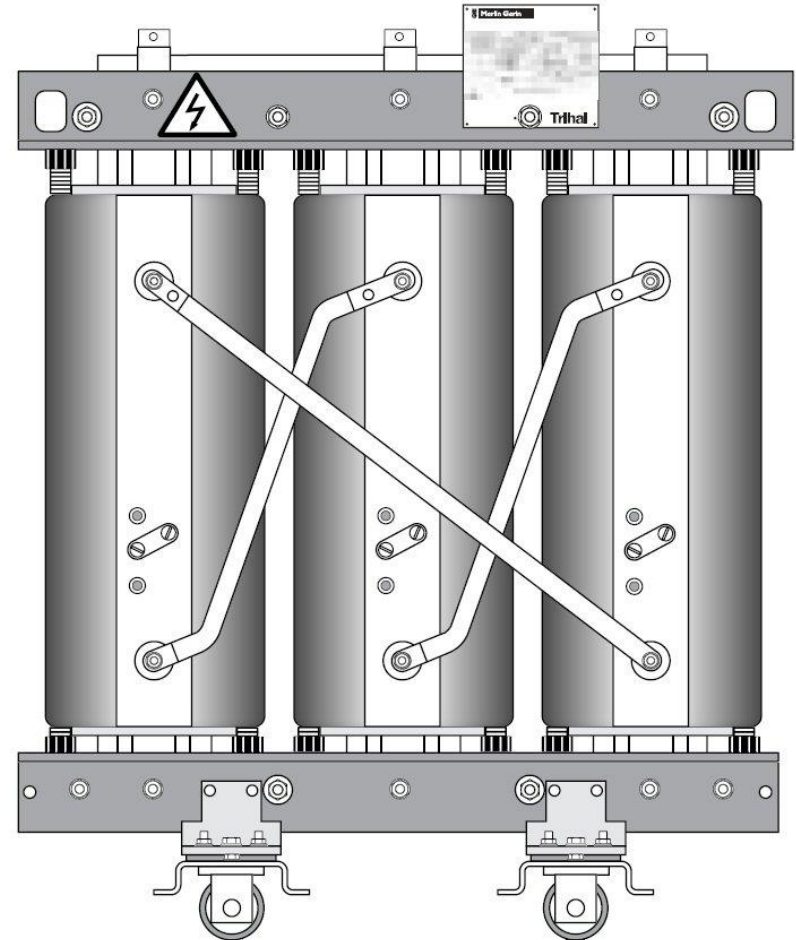- HTA/BT distribution transformers: Dry transformer
- Active parts coated in protective resins (often epoxies) and mounted on a support frame in the open air.
- Good ventilation of the device and the room is required
- Dust removal from ambient air recommended





III - Transformers

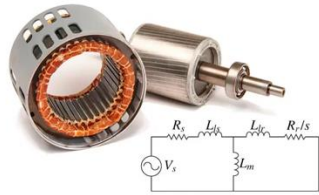

Three-phase transformer

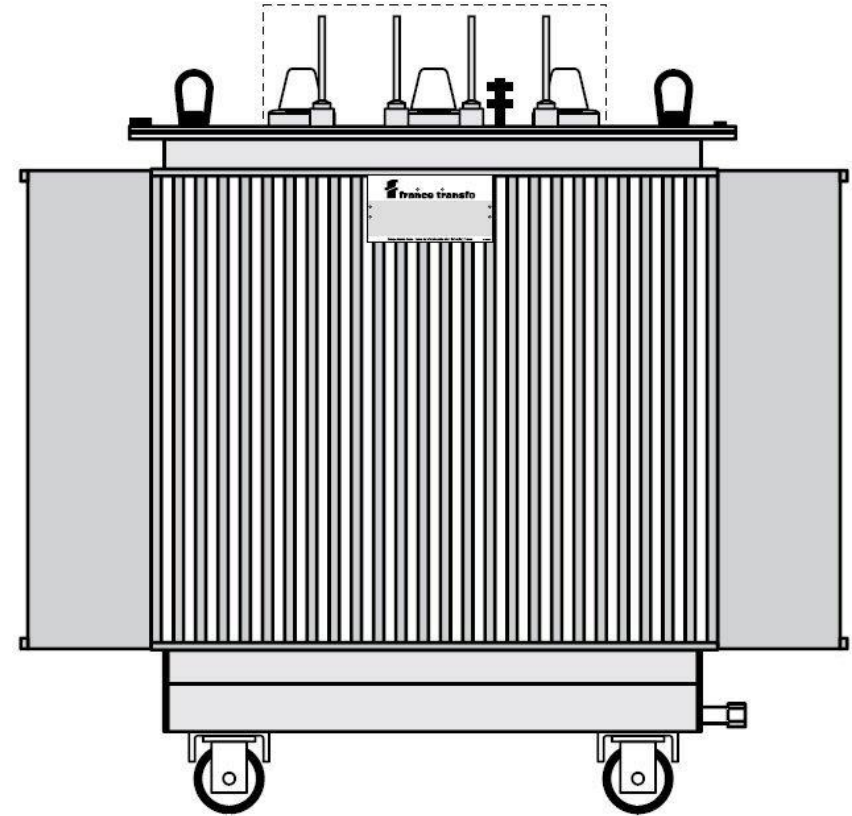- HTA/BT distribution transformers: Immersed transformer
- Sealed with Total/Integral filling
- Hermetically sealed transformer
- Flexible tank
- Flexible tank
- Accordion-folded walls to absorb changes in dielectric volume as it heats up



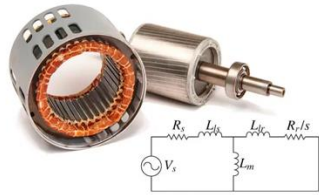

III - Transformers

Three-phase transformer

- HTA/BT distribution transformers: Dry and Immersed transformers



Transformateur de type enrobé sous enveloppe



Transformateur 400 kVA avec accessoires de protection