

3-phase motors


- Synchronous machine: => limited to the study of the synchronous alternator

- Construction:


=> 3-phase stator generating a rotating magnetic field (see before)

=> DC rotor : different configurations


Permanent magnet rotor

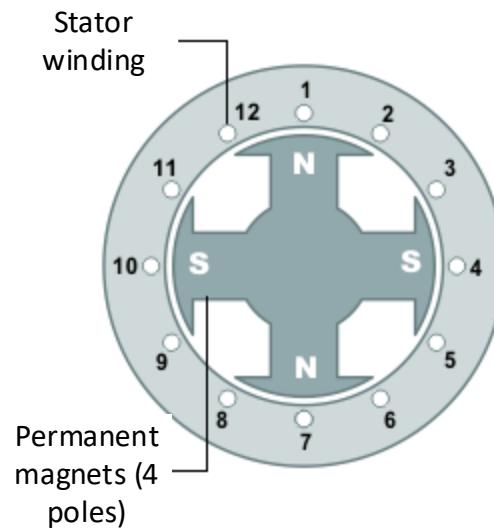

Wound rotor (DC current)

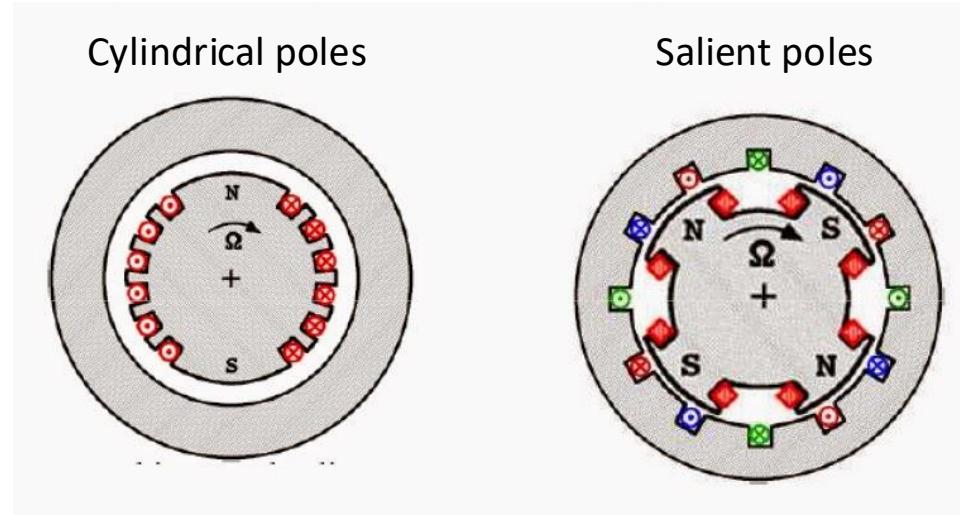

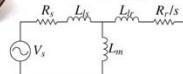Synchronous machine: The rotor rotates at the same speed as that of the rotation magnetic field



IV - Motors

3-phase motors

- Synchronous machine:

- Equivalent circuit in the linear domain:


=> The **armature circuit** (stator for the alternator) can be represented, for each phase, by the series connection of a **no-load emf**, a **resistor** (winding), a **self-inductance** and a **mutual inductance** with the two other phases.


=> With the no-load electromotive force:

$$E_v = K\Omega_S I_e$$

- Ω_S : rotation speed (rad/s)

- I_e : rotor excitation current

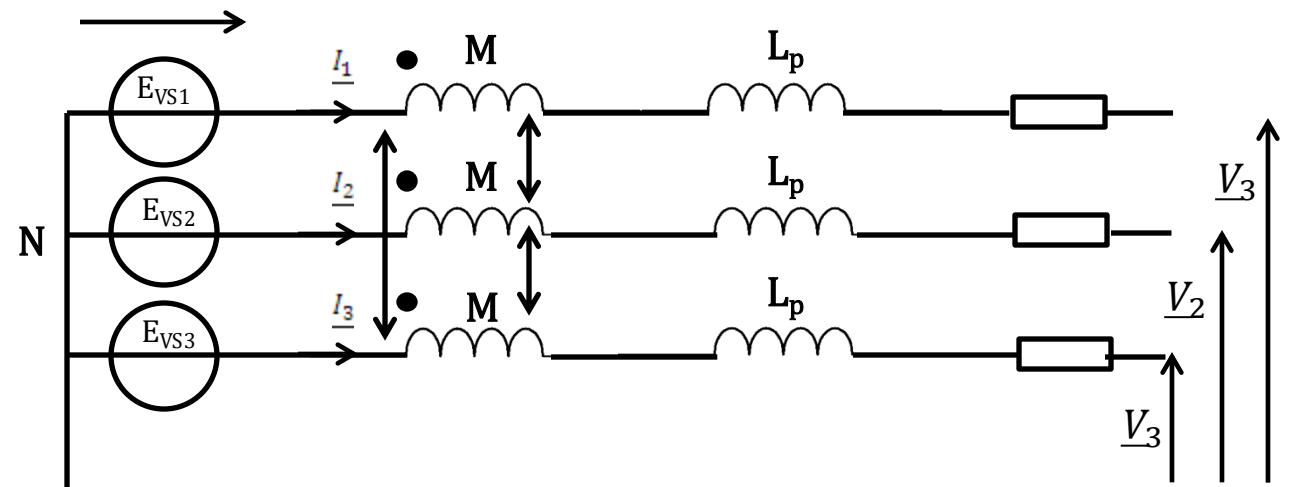


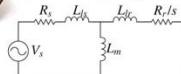

3-phase motors

- Synchronous machine:

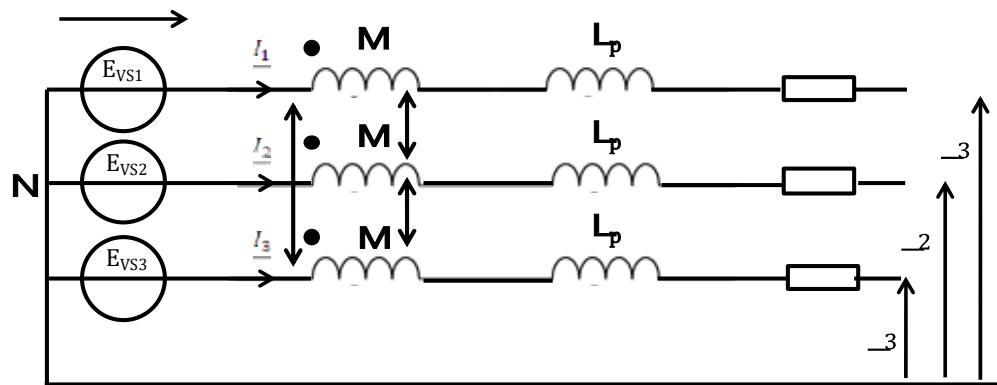- Equivalent circuit in the linear domain:




- With:

$$\underline{I_1} + \underline{I_2} + \underline{I_3} = 0$$


$$\begin{cases} \underline{E_{v1}} = j \cdot M \cdot \omega \cdot \underline{I_2} + j \cdot M \cdot \omega \cdot \underline{I_3} + j \cdot L_p \cdot \omega \cdot \underline{I_1} + R \cdot \underline{I_1} + \underline{V_1} \\ \underline{E_{v2}} = j \cdot M \cdot \omega \cdot \underline{I_1} + j \cdot M \cdot \omega \cdot \underline{I_3} + j \cdot L_p \cdot \omega \cdot \underline{I_2} + R \cdot \underline{I_2} + \underline{V_2} \\ \underline{E_{v3}} = j \cdot M \cdot \omega \cdot \underline{I_1} + j \cdot M \cdot \omega \cdot \underline{I_2} + j \cdot L_p \cdot \omega \cdot \underline{I_3} + R \cdot \underline{I_3} + \underline{V_3} \end{cases} \rightarrow \begin{cases} \underline{E_{v1}} = j \cdot (L_p - M) \cdot \omega \cdot \underline{I_1} + R \cdot \underline{I_1} + \underline{V_1} \\ \underline{E_{v2}} = j \cdot (L_p - M) \cdot \omega \cdot \underline{I_2} + R \cdot \underline{I_2} + \underline{V_2} \\ \underline{E_{v3}} = j \cdot (L_p - M) \cdot \omega \cdot \underline{I_3} + R \cdot \underline{I_3} + \underline{V_3} \end{cases}$$

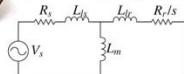With $L_s = L_p - M$ the **cyclic inductance**, each phase can be decoupled



3-phase motors

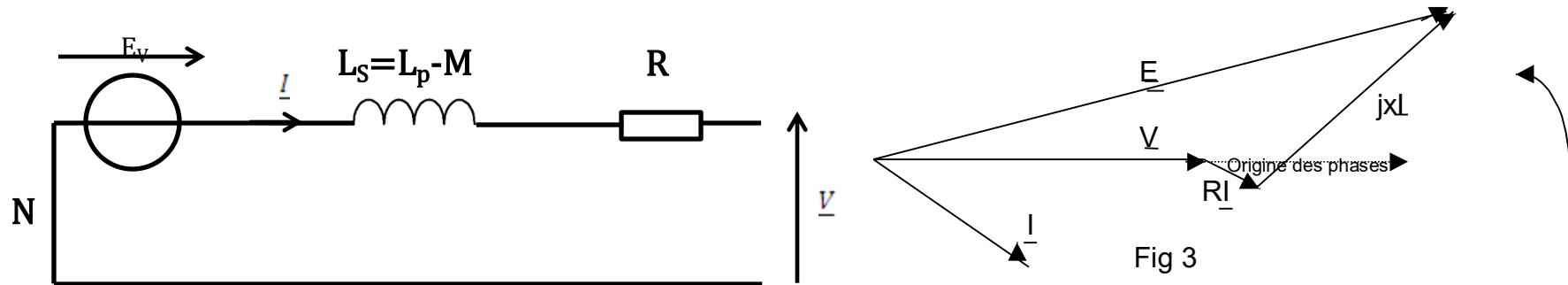
- Synchronous machine:
- Each phase can be modelled with an equivalent single-phase circuit
=> Behn-Eschenburg's model



$$\underline{V} = \underline{E_v} - jL_s \cdot \omega \cdot \underline{I} - R \cdot \underline{I}$$

- L_s : synchronous inductance
- X_s : synchronous reactance

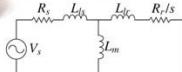- R : winding resistance
- E_v : no-load electromotive force



3-phase motors

- Synchronous machine:

- Determining the elements of the equivalent circuit diagram


=> E_v is measured as a function of the excitation current I_e - $E_v(I_e)$: **No-load characteristic** of the SM

=> **No-load** test = the SM is driven at nominal speed by an auxiliary motor (e. g. a DC motor)

=> R is directly calculated from imposed current and voltage (voltamperometric method)


=> X_s is obtained from a short-circuit test performed at nominal speed with reduced excitation (I_e)

=> Plot of I_{cc} as a function of I_e

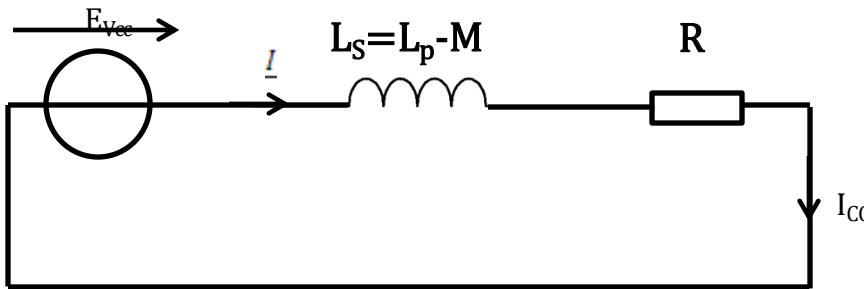

$$E_{vcc} = jL_s \cdot \omega \cdot I_{cc} - R \cdot I_{cc}$$
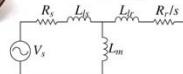
$$X_s = L_s \omega = \sqrt{\left(\frac{E_{vcc}}{I_{cc}}\right)^2 - R^2}$$




IV - Motors


3-phase motors

- Synchronous machine:

- Power balance

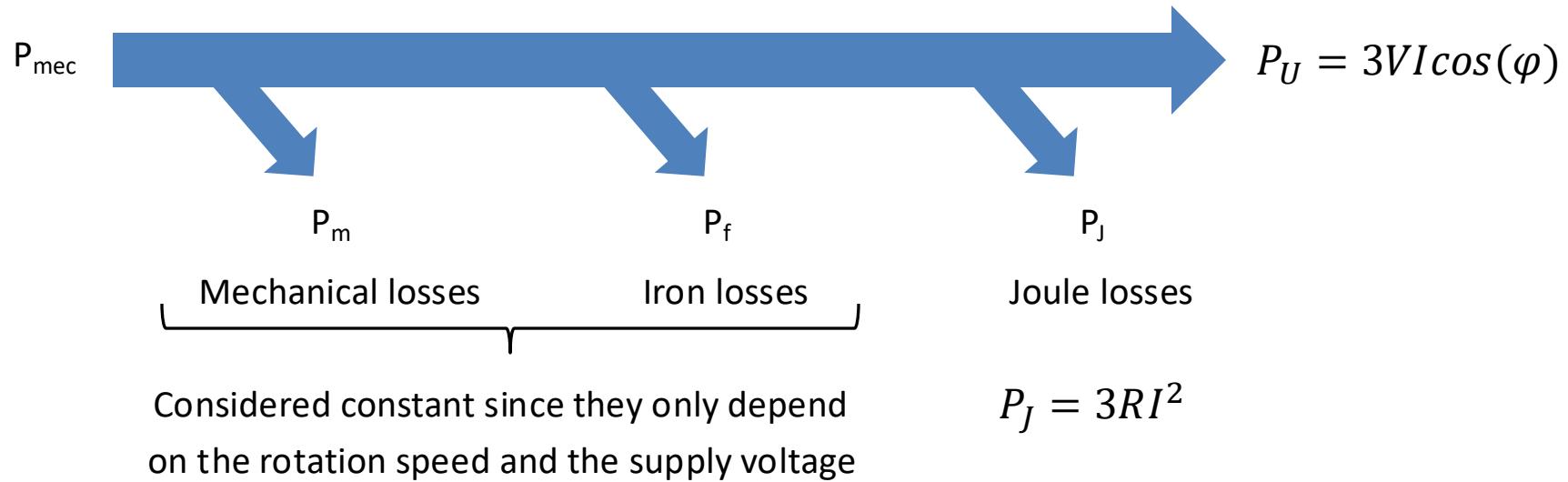

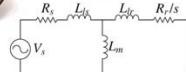- Therefore, the efficiency: $\eta = \frac{P_U}{P_U + P_m + P_f + P_J}$



3-phase motors

- [Induction motor/ Asynchronous motor:](#)

- Construction:


=> 3-phase stator generating a rotating magnetic field (see before)


=> 3-phase rotor : different configurations

Squirrel cage rotor



3-phase wound rotor

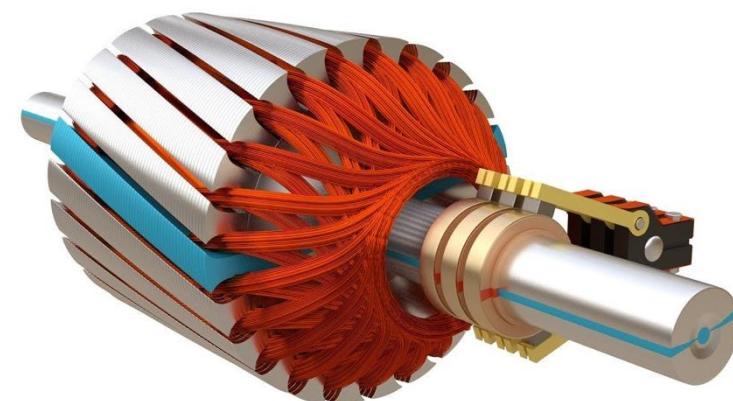

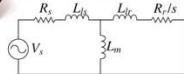

3-phase motors

- [Induction motor/ Asynchronous motor:](#)

- **Squirrel cage rotor:**


=> Aluminum conductors or bars are placed in the cylinder slots and [short-circuited](#) at each end




© DWTMA 1998

- **3-phase wound rotor or Slip-ring rotor:**

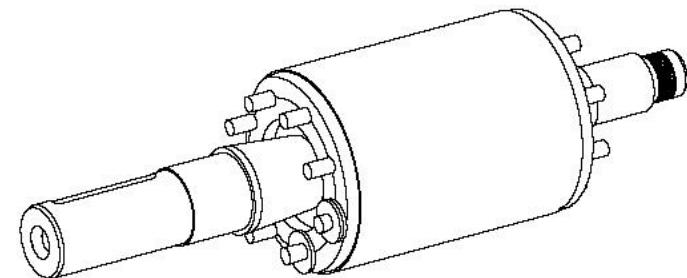- ⇒ Windings identical to those of the stator are housed in the slots on the periphery of the rotor
- ⇒ The rotor is three-phase and [wye-coupled \(short-circuit\)](#)
- ⇒ The ends of the windings are connected to three copper rings, insulated and fixed to the rotor



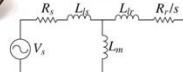[Short-cut necessary at the rotor to generate induced currents](#)



3-phase motors

- [Induction motor/ Asynchronous motor:](#)

- Working principle:


=> The 3-phase stator generates a rotating magnetic field


=> The rotating field induces [eddy currents](#) in the rotor windings

=> According to [Lenz's law](#), these currents oppose the cause that gave rise to them and generate a magneto-motive force that makes the rotor rotate

=> Therefore, the rotor moves with the stator field at speed Ω_R tending towards Ω_S , but never reaches it

$$\Omega_R < \Omega_S$$

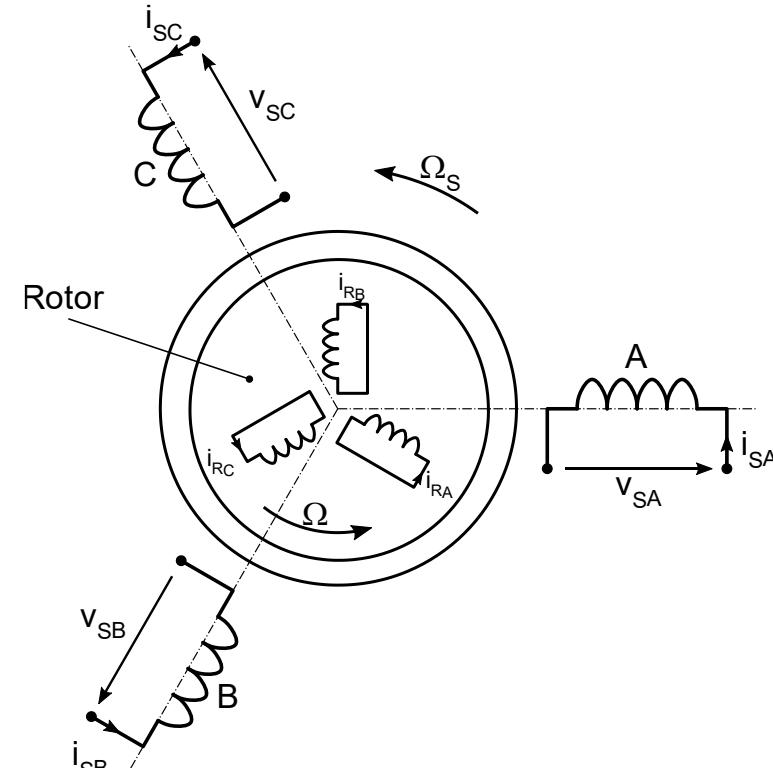

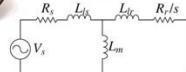

3-phase motors

- [Induction motor/ Asynchronous motor:](#)

- The slip g :

=> The rotor slip with respect to the stator field is defined as the relative deviation of the rotor rotation speed from synchronous speed


$$g = \frac{\Omega_S - \Omega_R}{\Omega_S}$$

=> At synchronous speed: $\Omega_R = \Omega_S, g = 0$

=> 0 induced current => deceleration of rotor

=> When stopped, and at starting-up: $\Omega_R = 0, g = 1$

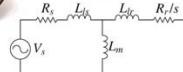=> Generator operation: $\Omega_R > \Omega_S, g < 0$




IV - Motors

3-phase motors

- [Induction motor/ Asynchronous motor:](#)
- [Equivalent circuit diagram of the induction motor](#)

=> [Ideal model: the perfect Asynchronous motor](#)

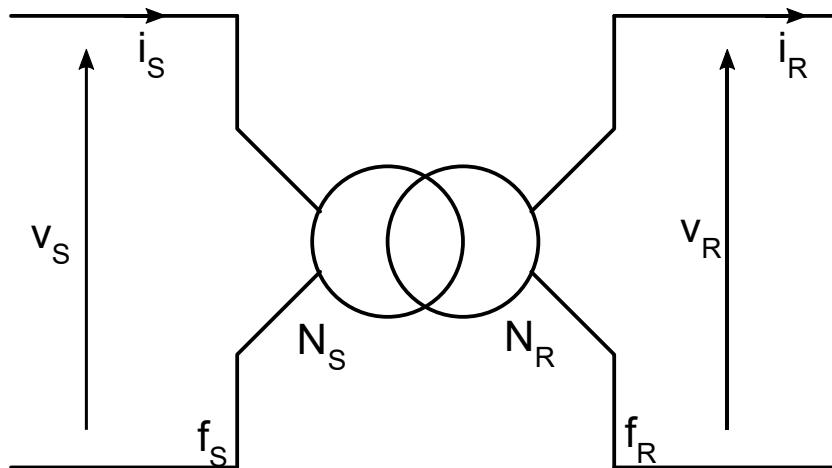=> Very similar to the transformer with short-circuited secondary side



V_s : RMS voltage across the stator winding

i_s : RMS current flowing in the stator winding


V_R : RMS voltage across the rotor winding

i_R : RMS current flowing in the rotor winding

f_s : frequency of stator or grid

f_R : frequency of rotor currents

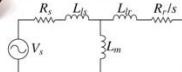m : number-of-turns ratio between rotor and stator: $m=N_R/N_S$




3-phase motors

- Induction motor/ Asynchronous motor:
- Equivalent circuit diagram of the induction motor for each phase

=> Ideal model: the perfect Asynchronous motor

- At the stator, frequency of the grid f_S :

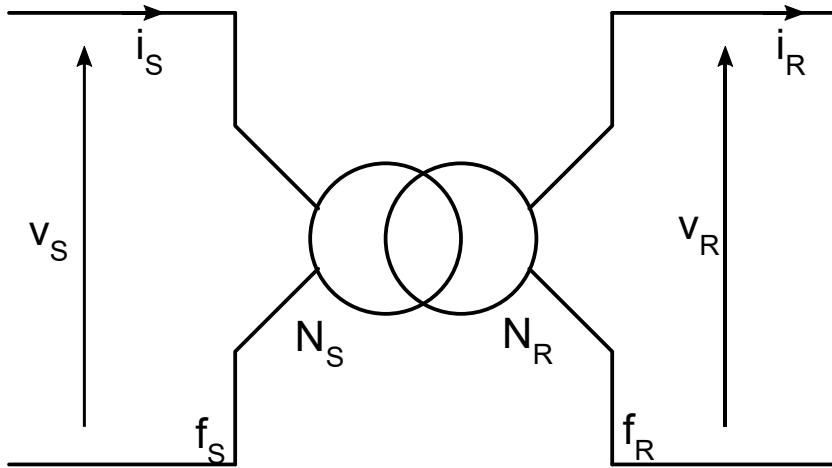- Frequency of currents induced at the rotor: f_R



$$f_S = \frac{\Omega_S}{2\pi} \text{ for } p = 1$$


$$g = \frac{\Omega_S - \Omega_R}{\Omega_S}$$

$$g\Omega_S = \Omega_S - \Omega_R$$

$$f_R = \frac{\Omega_S - \Omega_R}{2\pi} = \frac{g\Omega_S}{2\pi}$$

=> Frequency transformation ratio

$$f_R = g f_S$$

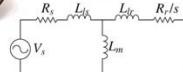

IV - Motors

3-phase motors

- Induction motor/ Asynchronous motor:

- Equivalent circuit diagram of the induction motor

=> Ideal model: the perfect Asynchronous motor

$$V_R = 4,44 \cdot S \cdot N_R \cdot \hat{B} \cdot f_R$$

$$V_S = 4,44 \cdot S \cdot N_S \cdot \hat{B} \cdot f_S$$

- Voltage transformation ratio (from Boucherot's formula)


$$\frac{V_R}{V_S} = \frac{N_R}{N_S} \cdot \frac{f_R}{f_S} = m \cdot g$$


$$V_R = m \cdot g \cdot V_S$$

- Current transformation ratio

$$N_R \cdot I_R - N_S \cdot I_S = 0$$
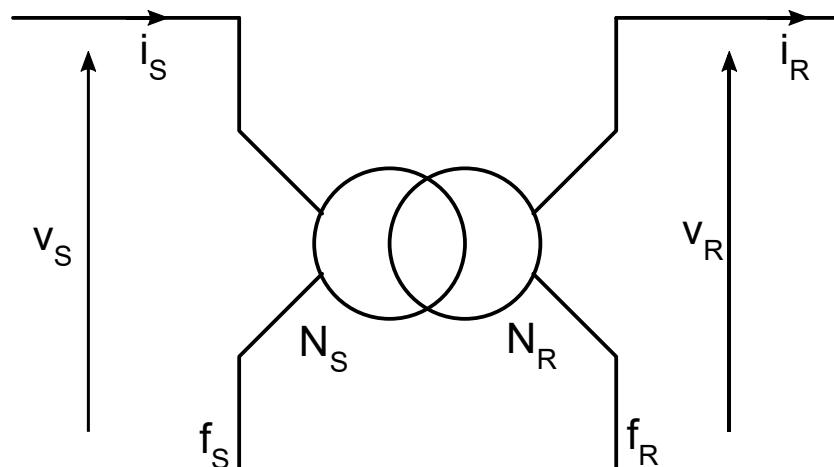
$$\frac{I_R}{I_S} = \frac{1}{m} = \frac{N_S}{N_R}$$



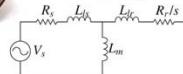


IV - Motors

3-phase motors

- [Induction motor/ Asynchronous motor:](#)
- [Equivalent circuit diagram of the induction motor](#)

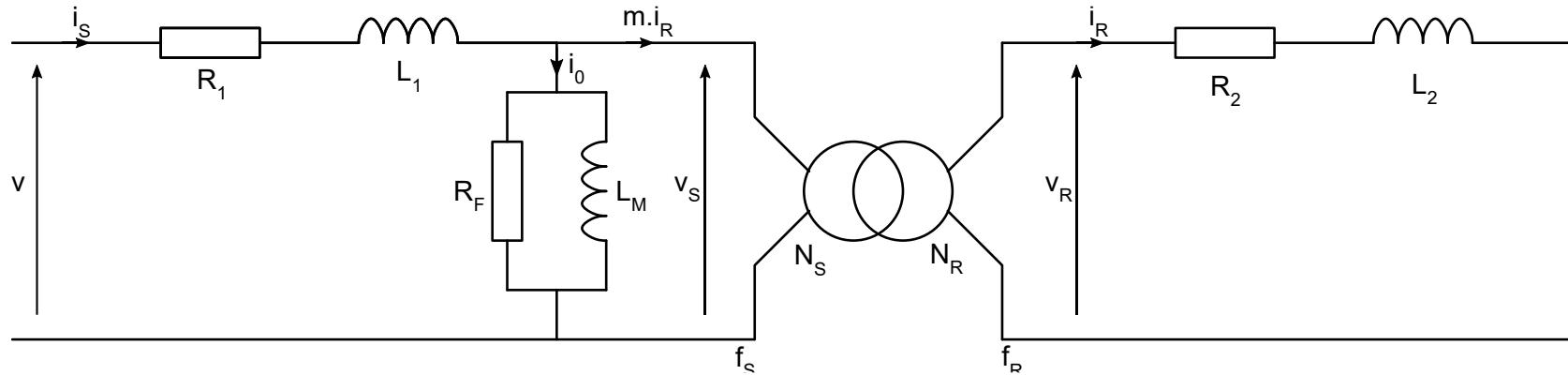=> [Intermediate model \(from the transformer\)](#)



R_1 : resistance of stator conductors


L_1 : stator winding leakage inductance

R_2 : resistance of rotor conductors

L_2 : rotor winding leakage inductance

R_F : resistance modelling iron losses

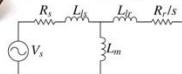
L_M : magnetizing inductance of the magnetic circuit



3-phase motors

- [Induction motor/ Asynchronous motor:](#)
- [Equivalent circuit diagram of the induction motor](#)

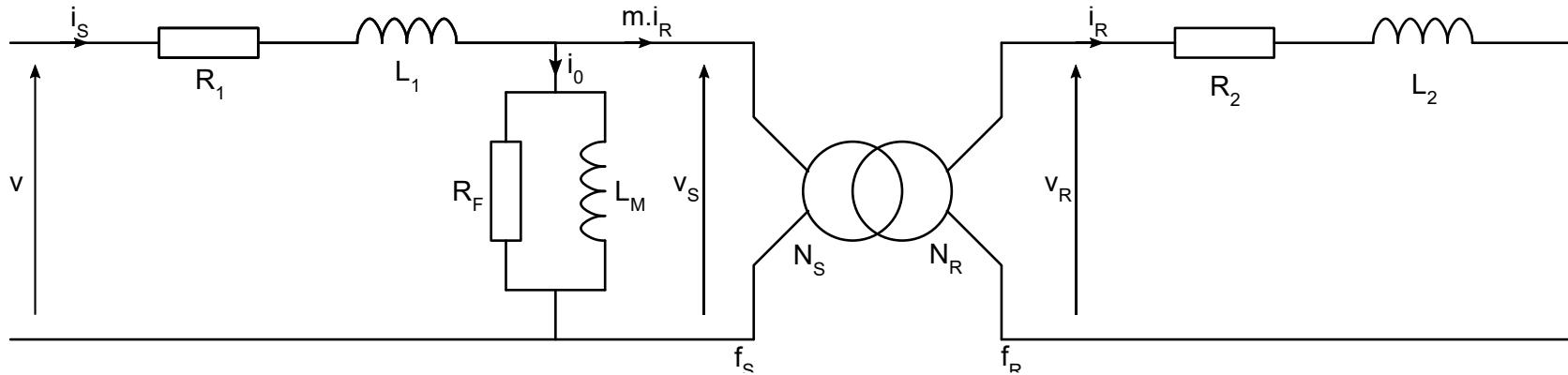=> [Intermediate model \(from the transformer\)](#)




- Voltages at the stator

$$\underline{V} = R_1 \cdot \underline{I_S} + j \cdot L_1 \cdot \omega_S \cdot \underline{I_S} + \underline{V_S}$$

- Voltages at the rotor

$$\underline{V_R} - R_2 \cdot \underline{I_R} - j \cdot L_2 \cdot g \cdot \omega_S \cdot \underline{I_R} = 0$$
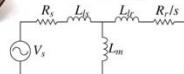
$$m \cdot \underline{V_S} - \frac{R_2}{g} \cdot \underline{I_R} - j \cdot L_2 \cdot \omega_S \cdot \underline{I_R} = 0$$




IV - Motors

3-phase motors

- Induction motor/ Asynchronous motor:
- Equivalent circuit diagram of the induction motor

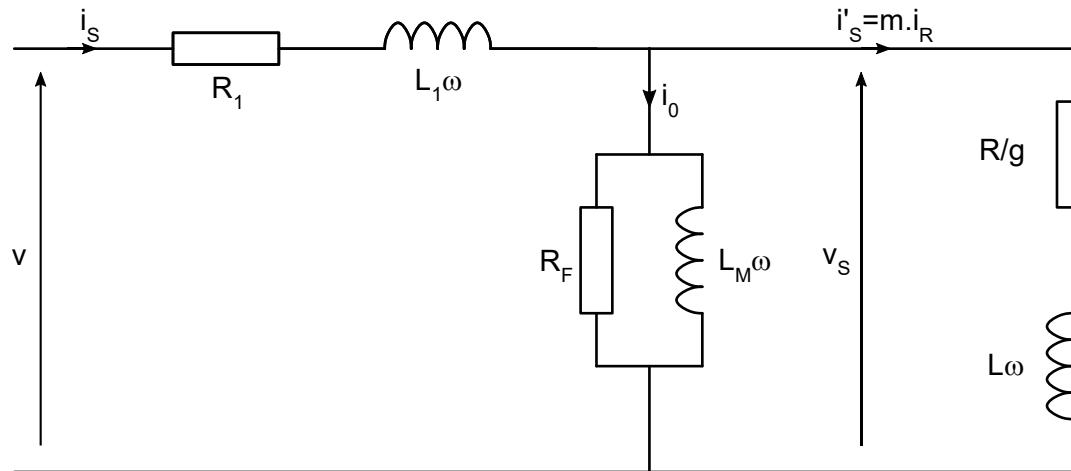=> The real model (equivalent primary model)




- Impedance transfer from rotor to stator: $m \cdot \underline{V_S} - \frac{R_2}{g} \cdot \underline{I_R} - j \cdot L_2 \cdot \omega_S \cdot \underline{I_R} = 0$

$$L = \frac{L_2}{m^2}$$

$$\frac{R}{g} = \frac{R_2}{g \cdot m^2}$$

$$\frac{I_R}{I_S} = \frac{1}{m}$$

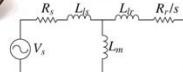


IV - Motors

3-phase motors

- [Induction motor/ Asynchronous motor:](#)
- [Equivalent circuit diagram of the induction motor](#)

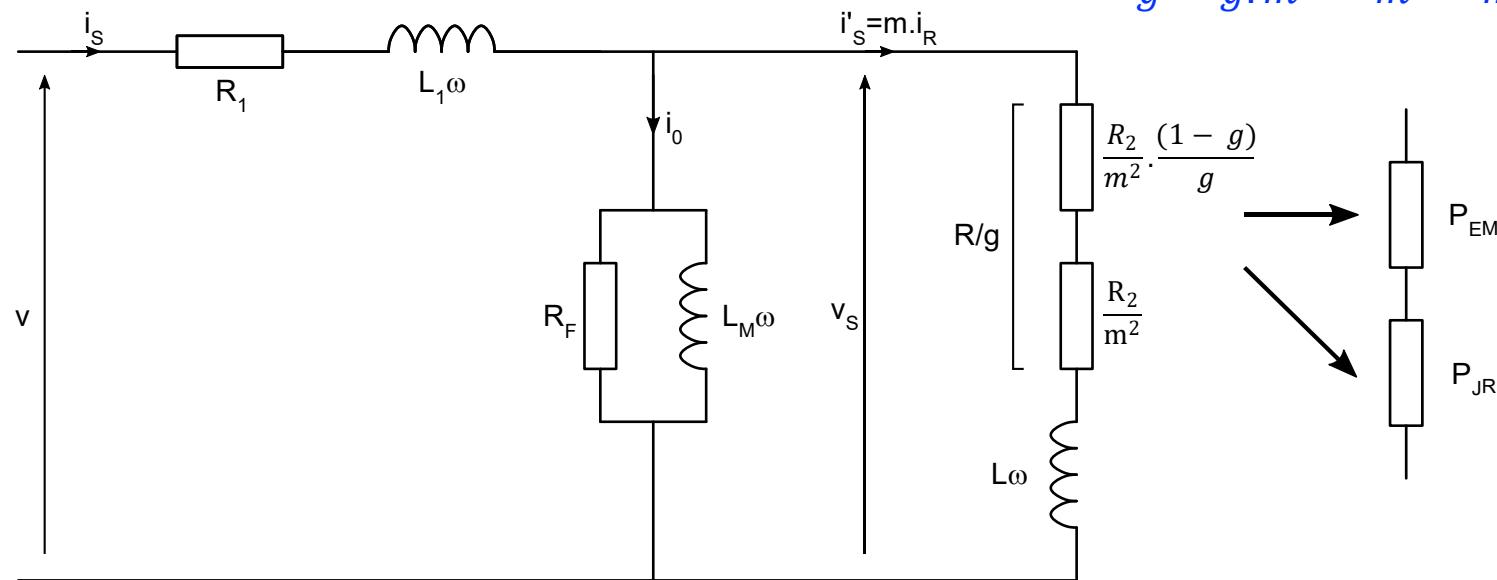
=> The real model (equivalent primary model)



$$\frac{R}{g} = \frac{R_2}{g \cdot m^2} = \frac{R_2}{m^2} + \frac{R_2 \cdot (1-g)}{m^2 \cdot g}$$

$\frac{R_2}{m^2}$ = related to Joule losses at the rotor

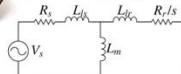$\frac{R_2 \cdot (1-g)}{m^2 \cdot g}$ = related to the power transferred to the rotor




IV - Motors

3-phase motors

- [Induction motor/ Asynchronous motor:](#)
- Equivalent circuit diagram of the induction motor
 => The real model (equivalent primary model)

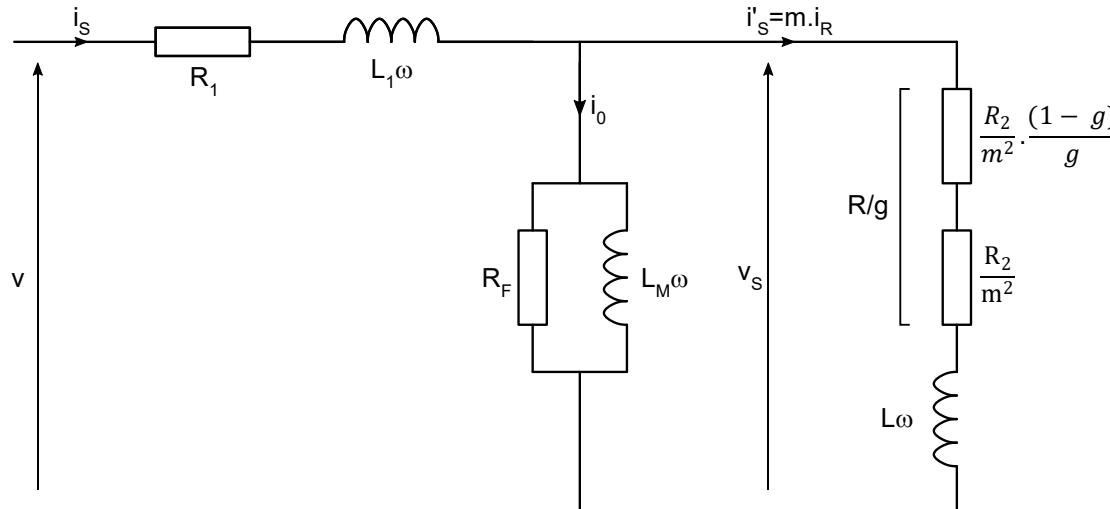Remark : inductances are cyclic inductances



R_F: resistance modeling iron losses

L_M: magnetizing inductance of the magnetic circuit

R₁: resistance of stator conductors/
Joule losses


L₁: stator winding leakage inductance

R/g: resistance of rotor conductors/motional resistance

R₂/m²: resistance of rotor conductors/
Joule losses

R₂/m² ((1-g)/g) resistance modelling
the electromagnetic power transferred
to the rotor

L: rotor winding leakage inductance

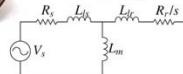


IV - Motors

3-phase motors

- Induction motor/ Asynchronous motor:

- Power balance:

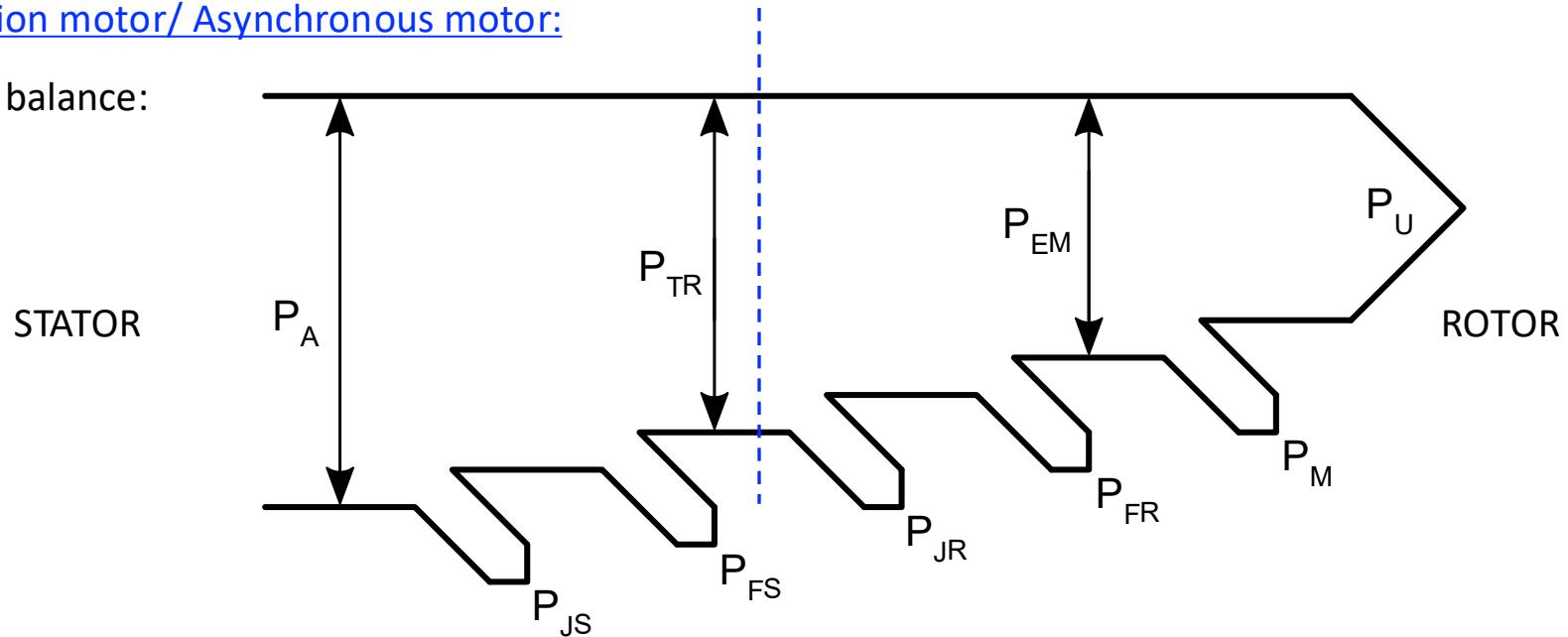

P_a : Active power absorbed at the stator

$$P_a = 3V_S I_S \cos\varphi_S$$

P_u : Useful power
(mechanical)

P_{JS} : Joule losses at the stator

$$P_{JS} = 3R_1 I_S^2$$

P_{FS} : Iron losses at the stator

$$P_{FS} = 3 \cdot \frac{V_S^2}{R_F}$$

P_{TR} : Power transmitted to the rotor


$$P_{TR} = C_{EM} \cdot \Omega_S$$



3-phase motors

- Induction motor/ Asynchronous motor:

- Power balance:

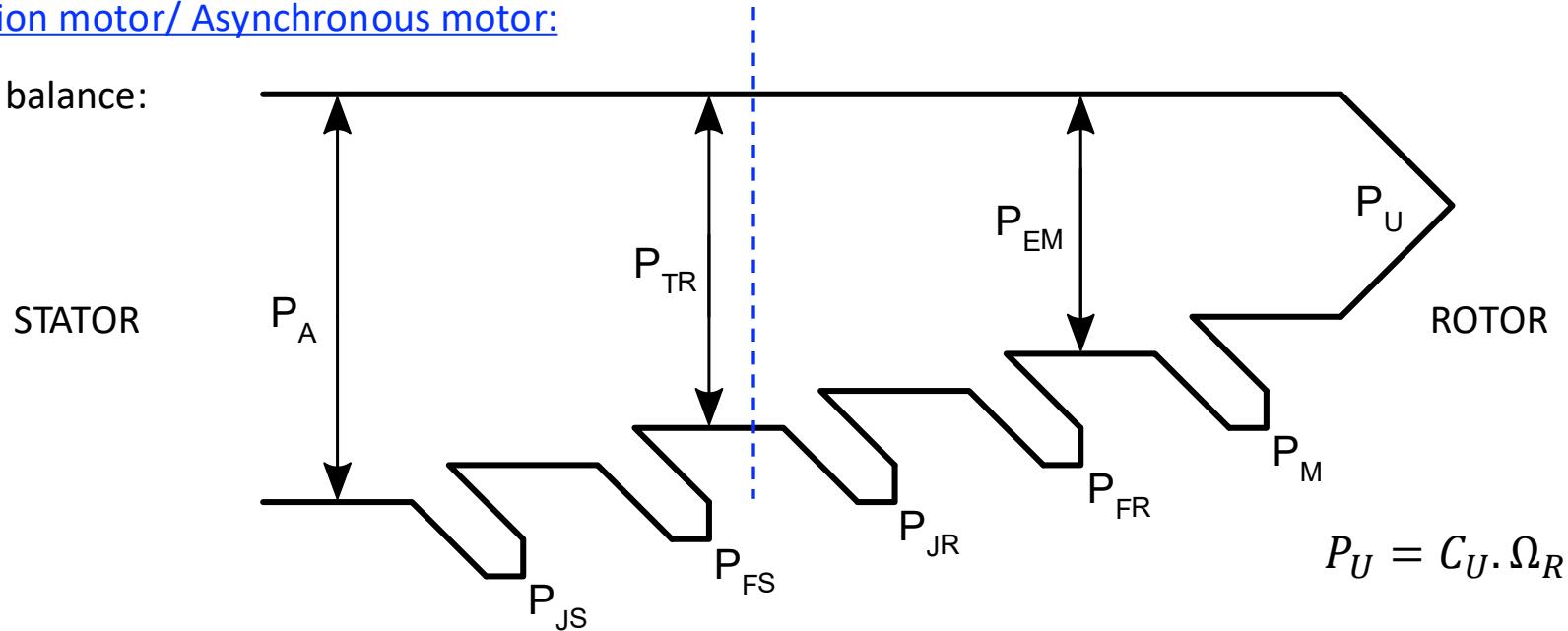



P_{JR} : Joule losses at the rotor $P_{JR} = 3 \cdot R_2 \cdot I_R^2$

P_{FR} : Iron losses at the stator (almost 0 usually, low f_R)

P_{EM} : Electromagnetic power $P_{EM} = C_{EM} \cdot \Omega_R$

p_M : Mechanical losses (bearing losses, aerodynamic friction of the fan...)
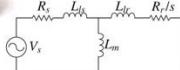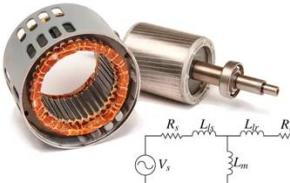
$$\eta = \frac{P_U}{P_U + P_{JS} + P_{FS} + P_{JR} + P_{FR} + p_M}$$



3-phase motors

- Induction motor/ Asynchronous motor:

- Determining the elements of the equivalent circuit diagram: **Test at $g = 0$**

=> Test at **nominal voltage**

=> The synchronous machine is driven at **synchronous speed** (Ω_s) by an auxiliary motor ($g=0$)


=> Under such conditions, $P_{EM} = 0$


- Measured quantities: V_{S0} , I_{S0} , P_{S0} , Q_{S0}

$$P_{S0} = P_{JS0} + P_{FS0} \cong P_{FS}$$

$$R_F = \frac{3V_{S0}^2}{P_{S0}}$$
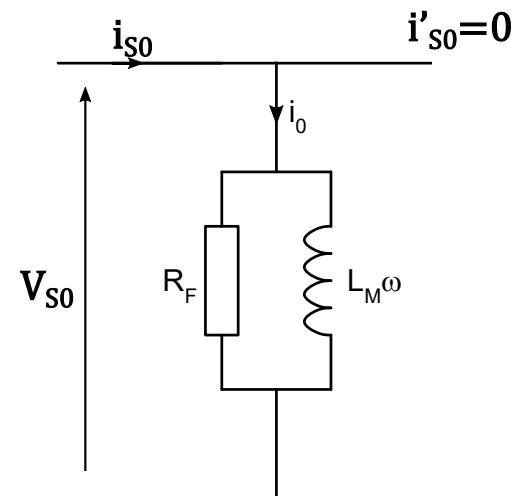
$$L_m \omega = \frac{3V_{S0}^2}{Q_{S0}}$$



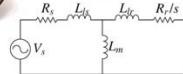


IV - Motors

3-phase motors


- [Induction motor/ Asynchronous motor:](#)
- Determining the elements of the equivalent circuit diagram: **Test at $g = 1$**
 - => Test at **reduced voltage**, close to the **nominal current**
 - => A brake blocks the rotor ($g=1$, $(\Omega_R=0)$)
 - => Iron losses are assumed to be negligible – Powers are all consumed at the rotor
- Measured quantities: V_{SR} , I_{SR} , P_{SR} , Q_{SR}

$$R = \frac{P_{SR}}{3I_{SR}^2} - R_1$$

$$L\omega = \frac{Q_{SR}}{3I_{SR}^2}$$

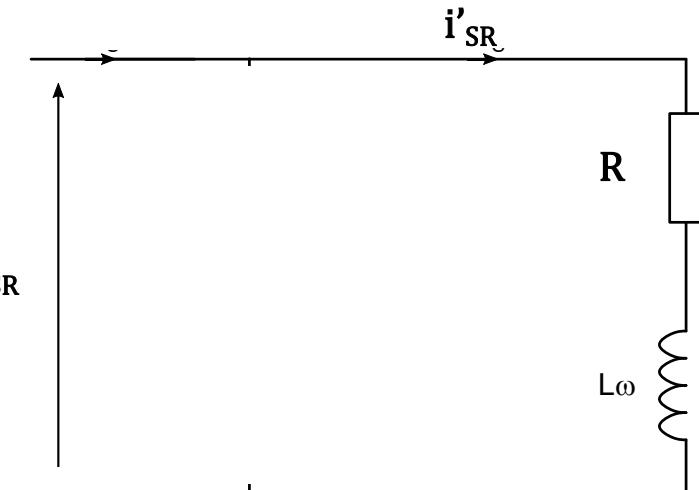

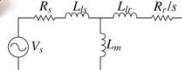- R_1 is measured by volt-amperemetric at the stator
- => Hot, continuous and nominal voltage and current



3-phase motors

- Induction motor/ Asynchronous motor:
- Expression of the electromagnetic torque


- R_1 and L_1 are neglected at $V = V_s$


$$I'_S = \frac{V}{\sqrt{\left(\frac{R}{g}\right)^2 + (L \cdot \omega)^2}}$$

$$P_{TR} = 3 \cdot \frac{R}{g} \cdot I'^2_S$$

$$P_{TR} = C_{EM} \cdot \Omega_S$$
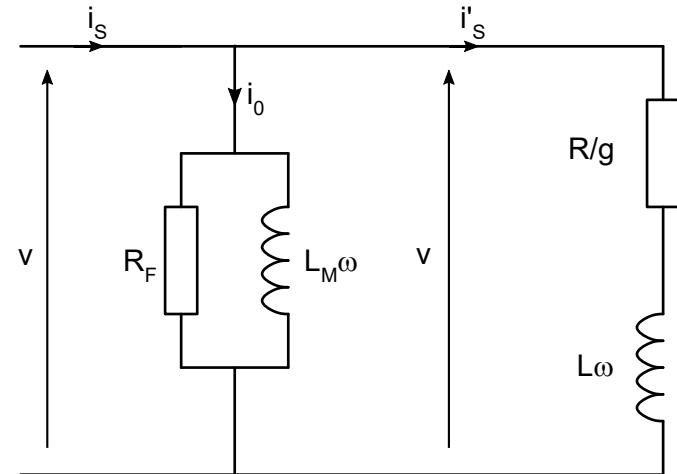
$$C_{EM} = 3 \cdot \frac{p}{\omega} \cdot \frac{V^2 \cdot R}{\frac{R^2}{g} + g \cdot (L \cdot \omega)^2}$$



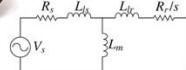

IV - Motors

3-phase motors

- [Induction motor/ Asynchronous motor:](#)
- Electromagnetic torque

$$C_{EM} = 3 \cdot \frac{p}{\omega} \cdot \frac{V^2 \cdot R}{\frac{R^2}{g} + g \cdot (L \cdot \omega)^2}$$

$$C_{MAX} = k \cdot \frac{V^2}{f^2} \quad g_{max} = \frac{R}{L \cdot \omega}$$

$$C_{DEM} = 3 \cdot \frac{p}{\omega} \cdot \frac{V^2 \cdot R}{R^2 + (L \cdot \omega)^2}$$

